

Go to **wooclap.com** and use the code **EYETQC**

Any questions? Send them in now by



- 1 Go to **wooclap.com**
- 2 Enter the event code in the top banner

Event code
EYETQC

Contact Information

Anupam Chattopadhyay

Email: anupam@ntu.edu.sg

Office: N4-02c-105

Writing complete Verilog code for a RISC-V CPU, including all the modules and their interconnections, is a complex and extensive task that would go beyond the scope of a single response. Implementing a full RISC-V CPU in Verilog is typically a project that requires significant time and expertise. However, I can provide a simplified example of Verilog code for a basic RISC-V core to give you a starting point.

Please note that this is a very basic example and may not cover all features and optimizations of a real-world RISC-V CPU. You would need to consult detailed CPU designs and possibly a CPU microarchitecture textbook for a more comprehensive implementation. Here's a basic structure of a 3-stage pipelined RV32I RISC-V core in Verilog:

```
verilog
Copy code

module RISC_V_CPU (
    input wire clk,
    input wire reset,
    input wire [31:0] instruction,
    output wire [31:0] result
);

// Define the registers
reg [31:0] pc;
reg [31:0] if_id_instruction;
reg [31:0] id_ex_instruction;
reg [31:0] ex_mem_instruction;

// Fetch stage
always @(posedge clk or posedge reset) begin
    if (reset) begin
        pc <= 32'h0;
        if_id_instruction <= 32'h0;
    end else begin
        pc <= pc + 4;
        if_id_instruction <= instruction;
    end
end
```

Plan for the 2nd half of the semester

■ Full-Time Course

Week	Pre-Recorded Lectures	Monday (LT19A) 830-920	Thursday (Zoom) 1630-1720	Tutorial	Lab
7	L13-L14				
Recess Week					
8	L15-L16	L13-L14 Summary	Online Consultation (Zoom)	Tutorial 6	+ quiz 3
9	L17-L18	L15-L16 Summary		Tutorial 7	Experiment 4 + quiz 4
10	L19-L20	L17-L18 Summary		Tutorial 8	
11	L21-L22	L19-L20 Summary (Zoom)		Tutorial 9	Experiment 5 + quiz 5
12	L23	L21-L22 Summary		Tutorial 10	
13		Public holiday			

Plan for the 2nd half of the semester (*contd.*)

■ Part-Time Course

Week	Pre-Recorded Lectures	Tuesday (LT11) 1830-2130		Lab
7	L13-L14			
Recess Week				
8	L15-L16	L13-L14 Summary	Tutorial 6	
9	L17-L18	L15-L16 Summary	Tutorial 7, 8	
10	L19-L20	L17-L19 Summary	Tutorial 9	
11	L21-L22			Experiment 4 + quiz 4
12	L23	L20-L22 Summary	Tutorial 10	
13				Experiment 5 + quiz 5

Plan for the 2nd half of the semester (*contd.*)



- Online Tasks for L13 to L22
 - Will not be graded

- Discussion lectures (Monday, 8:30-9:20 AM, LT19A)
 - You are required to view the pre-recorded lectures
 - Recap and discussion (slides to be uploaded afterwards)
 - Additional examples and exercises
 - Polls through **Wooclap** (QR code in respective slides)

Plan for the 2nd half of the semester (contd.)

■ Participation in Course

- Use NTULearn Discussion Forum to ask follow-up questions

Discussion Board
Discussions are a good way to encourage students to think critically about your coursework and interact with each others' ideas. You can create discussions around indi

Create Forum Remove Sorting

FORUM	DESCRIPTION	TOTAL POSTS	UNREAD POSTS
<input type="checkbox"/> Q&A Lecture 21-22		0	0
<input type="checkbox"/> Q&A Lecture 19-20		0	0
<input type="checkbox"/> Q&A Lecture 17-18		0	0
<input type="checkbox"/> Q&A Lecture 15-16		0	0
<input type="checkbox"/> Q&A Lecture 13-14		0	0

■ Consultation Slots on (Thursday, 4:30-5:20 PM, Zoom)

- Limit yourself to 3 questions
- Avoid the clarification on tutorial
- <https://ntu-sg.zoom.us/j/81954891824>
Meeting ID: 819 5489 1824
Passcode: 364003



SC1005

Digital Logic

Recap and Discussion




Lecture 19

Sequential Circuits in Verilog

Summary of Lecture 19

- Sequential Circuits in Verilog
 - Registers in Verilog
 - Clock and Reset
 - Synchronous always block
 - Counters

Recap: Registers in Verilog

   

```
module simplereg (input d, clk,  
                  output reg q);
```

```
    always@(posedge clk)  
        q <= d;
```



```
endmodule
```

```
module simplereg (input [7:0] d, input clk,  
                  output reg [7:0] q);
```

```
    always@(posedge clk)  
        q <= d;
```

```
endmodule
```


Recap: Synchronous vs Asynchronous Reset

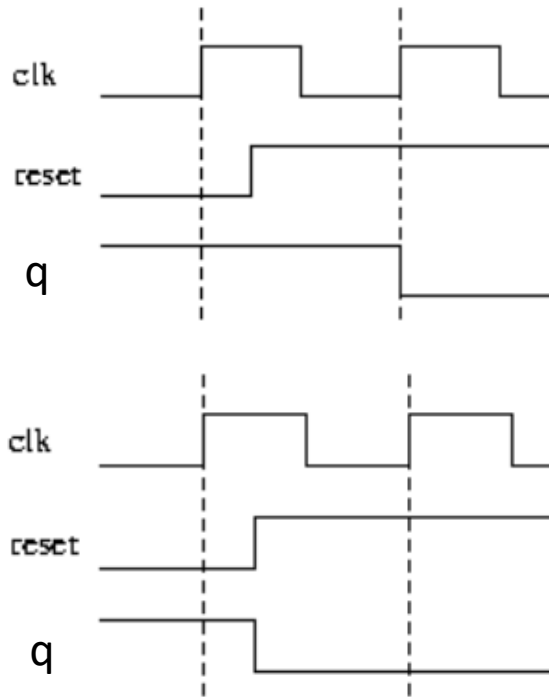 

```
module simplereg (input [7:0] d,
                  input clk, rst,
                  output reg [7:0] q);

always@(posedge clk)
begin
    if(rst) // same as (rst==1'b1)
        q <= 8'b0000_0000;
    else
        q <= d;
end

endmodule
```


```
module simplereg (input [7:0] d,
                  input clk, rst,
                  output reg [7:0] q);

always@(posedge clk or posedge rst)
begin
    if(rst)
        q <= 8'b0000_0000;
    else
        q <= d;
end

endmodule
```

Registers in Verilog

 - Each *assignment* in a synchronous always block results in a *register*




```
module multireg (input [7:0] a, b, c,  
                 input clk, rst,  
                 output reg [7:0] q, r, s);  
  
    always@(posedge clk)  
    begin  
        if(!rst) begin  
            q <= 8'b0000_0000;  
            r <= 8'b0000_0000;  
            s <= 8'b0000_0000;  
        end else begin  
            q <= a;  
            r <= b;  
            s <= c;  
        end  
    end  
end  
  
endmodule
```

Recap: Assignments in Always Blocks

- For *combinational* always blocks, we *always* use a blocking assignment (`=`), and **order matters**
- For *synchronous* always blocks, we *always* use non-blocking assignments (`<=`), and **order does not matter**

Combinational always block

 
```
reg x, y;  
  
always @ *  
begin  
    x = a & b;  
    y = x ^ c;  
end
```



Synchronous always block

```
reg x, y;  
  
always@(posedge clk)  
begin  
    x <= a;  
    y <= x;  
end
```

Each *assignment* in a synchronous always block results in a *register*

 

Exercise 1


For the Verilog code shown, if the current state of the circuit is $ABC = 001$, what is the next state?

```
module Ex1 (input Clk, Rst,
            output reg A, B, C);

    always@(posedge Clk)
    begin
        if (Rst) begin
            C <= 1'b1;
            B <= 1'b0;
            A <= 1'b0;
        end
        else begin
            C <= B;
            B <= A;
            A <= A ^ B ^ C;
        end
    end
endmodule
```



111
001
100
010

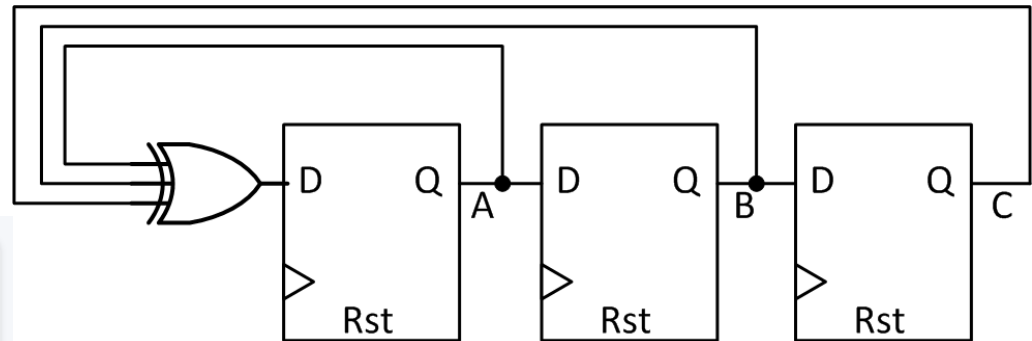

1 Go to wooclap.com



2 Enter the event code in the top banner

Event code
EYETQC

- There are a number of other basic sequential blocks we can use within our designs.
- Generally *edge-triggered components* are used.
 - Counters
 - Shift Registers
 - Serial-to-Parallel and Parallel-to-Serial Converters
 - Memories
 - FIFO buffer
- Synthesis tools will convert designs to D-type flip-flops/registers

Synchronous Counters

- Timing diagram helps:

  

- At each clock edge, the incremented value, *inc*, derived from the current output, is passed to *q*

Recap: Binary Counters

- At each rising edge, we pass through the incremented value of the current output

0 0 0

0 0 1

0 1 0

0 1 1

1 0 0

1 0 1

1 1 0

1 1 1


```

module simplecnt (input clk, rst,
                  output reg [3:0] q);

    always@(posedge clk)
    begin
        if(rst)
            q <= 4'b0000;
        else
            q <= q + 1'b1;
    end

endmodule

```



 


Synchronous Counters in Verilog


```
module simplecnt (input clk, rst,
                  input down, load,
                  input [3:0] cnt_in,
                  output reg [3:0] q);

always@(posedge clk)
begin
    if(rst)
        q <= 4'b0000;
    else
        if(load)
            q <= cnt_in;
        else
            q <= q + 1'b1;
end
endmodule
```


1-bit 2x1 mux

   


Exercise 2

 


W

 

X

 

Y

 

Z

- Using an up-counter with load capability, which circuit will generate a counting sequence of 1, 2, 3, 4, 5, 6? You can assume that the initial state of the counter is 001_2 .

W

X

Y

Z

None of the above



1

Go to wooclap.com

2


Enter the event code in the top banner

Event code


EYETQC



Synchronous Circuit Design

 

Synchronous Circuit Design

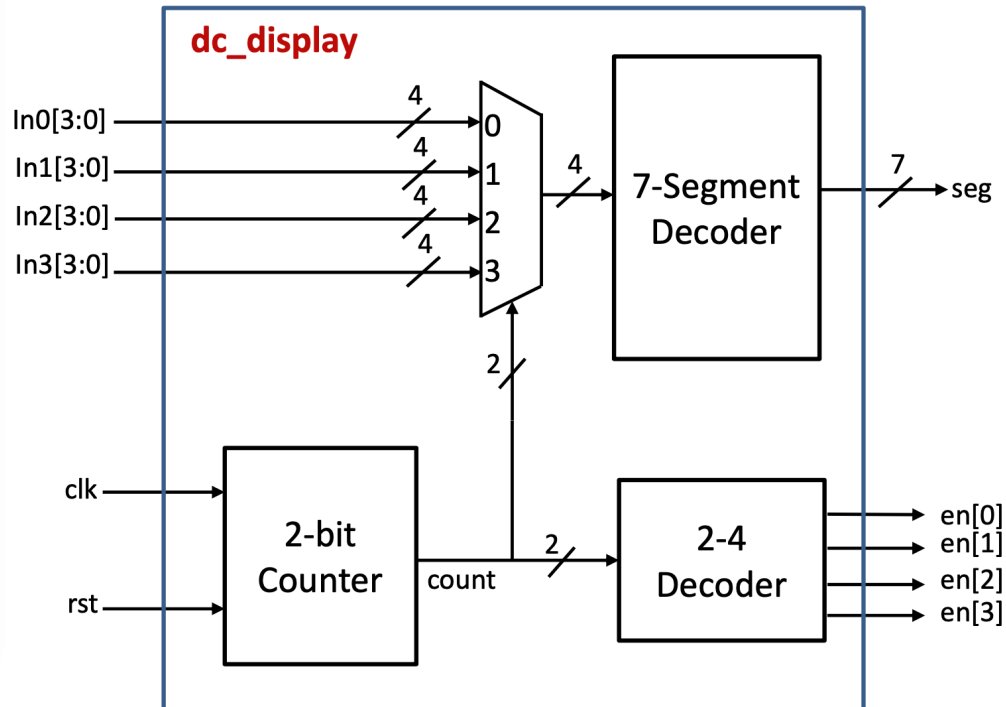

```
module dc_display (...) ...
```

```
// 2-bit counter
always@(posedge clk)
begin
    if(rst)
        count <= 2'b00;
    else
        count <= count + 1'b1;
end
```

```
// 2-to-4 decoder
always @ *
case (count)
    2'b00 : en = 2'b0001;
    2'b01 : en = 2'b0010;
    2'b10 : en = 2'b0100;
    2'b11 : en = 2'b1000;
endcase

// 4-bit 4x1 multiplexer
always @ *
case (count)
    2'b00 : mx_o = In0;
    2'b01 : mx_o = In1;
    2'b10 : mx_o = In2;
    2'b11 : mx_o = In3;
endcase


// 7-segment decoder
always @ *
case (mx_o)
    4'b0000 : seg = ...;
    4'b0001 : seg = ...;
    ...
    4'b1111 : seg = ...;
endcase
```

```
... endmodule
```

Summary of Lecture 20

- Sequential Circuits in Verilog
 - Shift Registers
 - Serial Data Transfer
 - Memory
 - What gets synthesized

Recap: Shift Registers in Verilog

 

```
module shiftreg (input clk, y,  
                 output reg q);
```

```
    reg q1, q2, q3;
```

```
    always@(posedge clk)  
    begin
```

```
        q1 <= y;  
        q2 <= q1;  
        q3 <= q2;  
        q  <= q3;
```

```
    end
```

```
endmodule
```

```
module shiftreg (input clk, y,  
                 output reg q);
```

```
    reg q1, q2, q3;
```

```
    always@(posedge clk)  
    begin
```

```
        q2 <= q1;  
        q1 <= y;  
        q  <= q3;  
        q3 <= q2;
```

```
    end
```

```
endmodule
```

Order does
not matter

First-In-First-Out Buffers

- FIFOs (First-In-First-Out) are useful for managing dataflow
- The structure is identical to shift registers, but now each register is multi-bit
- The input, output, and internal signal widths should match


```

module fifo4 (input clk, input [3:0] y,
              output reg [3:0] q);



    reg [3:0] q1, q2, q3;

    always@(posedge clk)
    begin
        q1 <= y;
        q2 <= q1;
        q3 <= q2;
        q  <= q3;
    end

endmodule
    
```

 

Serial to Parallel; Parallel to Serial

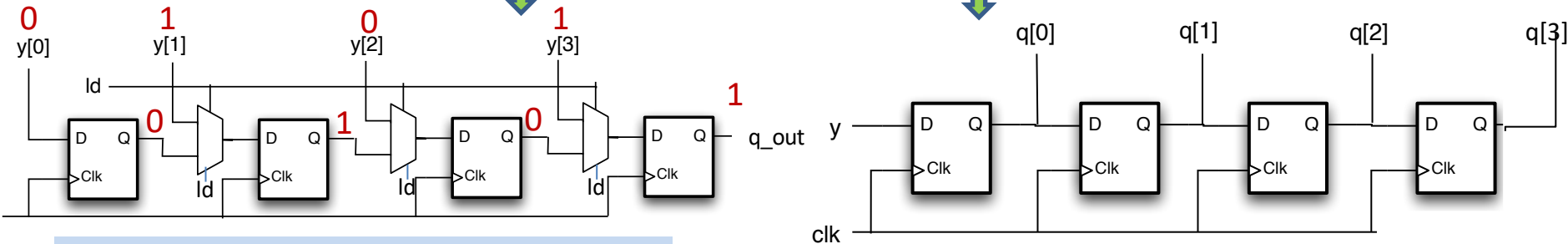 


```
module piso4 (input clk, ld,
              input [3:0] y,
              output q_out);
    reg [3:0] q;

    always@(posedge clk)
    begin
        if (ld) q <= y;
        else begin
            q[0] <= y[0];
            q[3:1] <= q[2:0];
        end
    end
    assign q_out = q[3];
endmodule
```


```
module sipo4 (input clk, y,
              output reg [3:0] q);
    always@(posedge clk)
    begin
        q[0] <= y;
        q[3:1] <= q[2:0];
    end
endmodule
```

 Exercise 3

Which of the following is the correct Verilog description of the circuit?



X

 

Y



1 Go to wooclap.com

2 Enter the event code in the top banner

Event code
EYETQC


Z

```
always@(posedge Clk)
begin
  if (rst) begin
    Q1 <= 1'b0;
    Q0 <= 1'b0;
  end
  else begin
    Q1 <= ~(Q1);
    Q0 <= ~(Q0) ^ Q1;
  end
end
endmodule
```

```
always@(posedge Clk)
begin
  if (rst) begin
    Q1 <= 1'b0;
    Q0 <= 1'b0;
  end
  else begin
    Q1 <= ~(Q1);
    Q0 <= ~(Q1) ^ Q0;
  end
end
endmodule
```


```
always@(posedge Clk)
begin
  if (rst) begin
    Q1 <= 1'b0;
    Q0 <= 1'b0;
  end
  else begin
    Q1 <= ~(Q0);
    Q0 <= ~(Q0) ^ Q1;
  end
end
endmodule
```


Memories

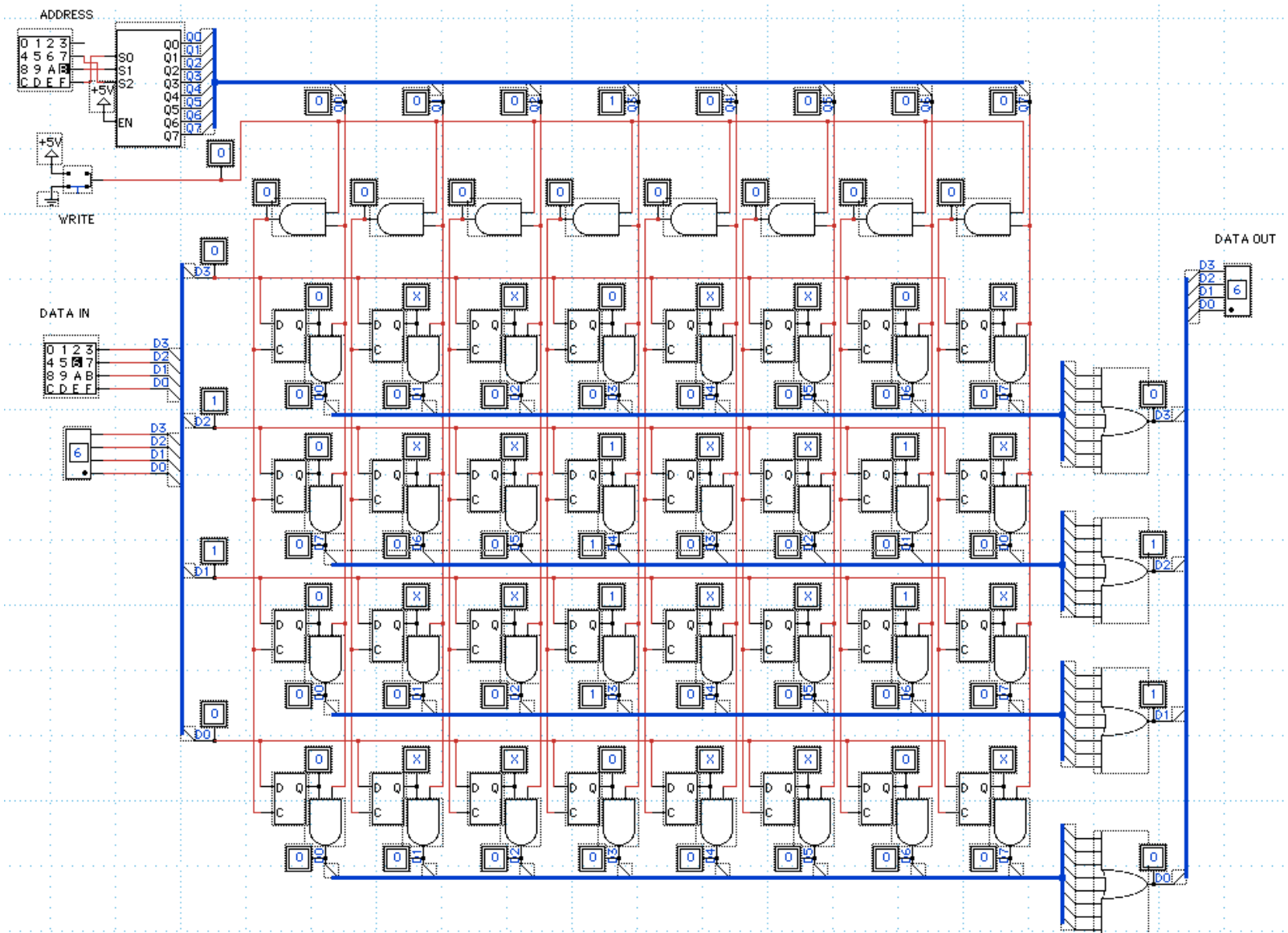


Memories

 - In order to **store** a value, we must assert *we* (write enable) and provide an address
- For **reading**, a mux connects the corresponding register to the *d_out* output




Recap: What Gets Synthesized?
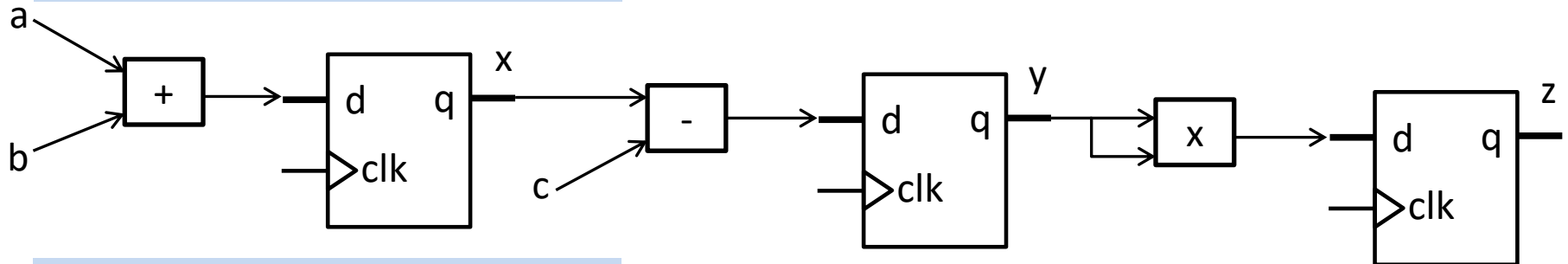
```
always@(posedge clk)
begin
    x <= a + b;
    y <= x - c;
    z <= y * y;
end
```





```
always@ *
begin
    x = a + b;
    y = x - c;
    z = y * y;
end
```

 

  Exercise 4

What is the correct output sequence of Q1 and Q0 observed at the **dash-red** lines?



Q1: 1010; Q0: 0011
Q1: 0101; Q0: 1010
Q1: 1010; Q0: 1100
None of the above



1

Go to wooclap.com

2

Enter the event code in the top banner

Event code
EYETQC



END OF L19,L20 SUMMARY