

SC1005

Digital Logic

Recap and Discussion

Lecture 17 and 18

Sequential Circuits

Summary of Lecture 17


- Intro to Sequential Circuits
- Latches
- Timing

Summary of Lecture 18

- Sequential Circuits
 - Gated/Enabled SR Latch
 - Transparent D-Latch
 - Edge-Triggered Flip-Flop
 - Registers

Review of Combinational Circuits

 
- So far, we have investigated *combinational* circuits
- The output of a combinational circuit is purely a function of the inputs to it
 - *output = f(input)*
- When the inputs are changed, the output will change to that determined by those inputs (after a short propagation delay)
- Knowing only the *current* inputs, we can always determine the output



- *Sequential* circuits introduce the idea of *state*
 - The state of a circuit encodes information about the past to determine how it will react with the inputs to produce an output
- The output of a sequential circuit depends on **both** the *current* inputs and what has previously happened (the *previous* inputs determine the “state”)
- In this sense, *sequential circuits have memory*, whereas combinational circuits have no memory.

 Exercise 2

- Consider two styles of fan speed control:
 - Dial-based (Off, Lo, Med, Hi)
 - Button-based (+, -)
- Which of the following correctly define the type of circuit used for implementing the fan control for L and R?




- | | |
|---|--|
| A. L – Combinational
R – Combinational | C. L – Sequential
R – Combinational |
| B. L – Combinational
R – Sequential | D. L – Sequential
R – Sequential |

Ans: B. For the first, the fan speed depends on which input is selected. For the second, the fan speed depends on the input and the current fan speed

Set-Reset (SR) Latch

 - The most basic circuit for storing a bit is the **Set-Reset (SR) Latch**




S	R	Q+	Function
0	0	Q	Store
0	1	0	Reset
1	0	1	Set

Note: $S = R = 1$ is not defined







The SR latch allows us to build a flight attendant call system

 - Connect “call” to S, and “cancel” to R
- Q stays at 1 even after “call” is released




Set-Reset (SR) Latch

■ Operation:

      

Set-Reset (SR) Latch

 
- There is, though, a problem with the SR Latch
- What happens when both S and R are asserted?



- When both S and R is then de-asserted at the same time, we may get oscillation at the output:
 - Constant swapping from 0 to 1 to 0 ...
- Normally, one gate is a little faster so the output will eventually stabilize, but which?
 - Impossible to know


Recap: Latches

Set-Reset (SR) Latch

 


S	R	Q+	Function
0	0	Q	Store
0	1	0	Reset
1	0	1	Set
1	1	?	Undefined

Enabled SR Latch

 


E	S	R	Q+	Function
0	X	X	Q	Store
1	0	0	Q	Store
1	0	1	0	Reset
1	1	0	1	Set
1	1	1	?	Undefined

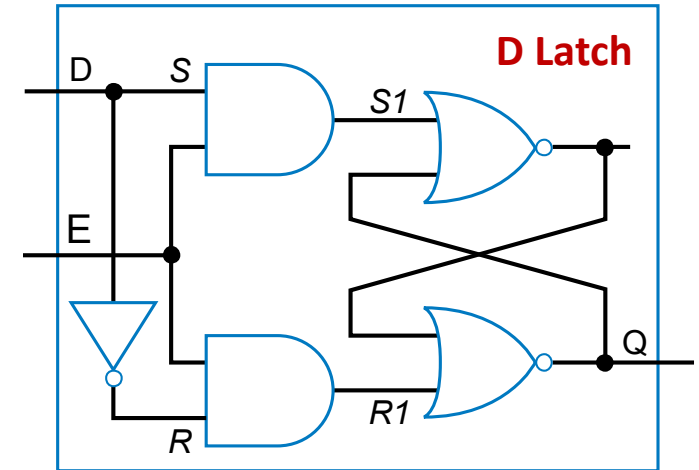

E	D	Q+	Function
0	X	Q	Store
1	0	0	Transparent
1	1	1	Transparent

The Clock

 
- In digital systems, sequential components are connected to what we call a “clock”
- The clock is a signal that continuously toggles between 0 and 1 at a fixed rate:



- The **period** of the clock is the time it takes to complete **one complete cycle** – we call this a cycle
- The **frequency** is the inverse of the period:
 - A 10ns (10×10^{-9} s) period gives a frequency of $1/10 \times 10^{-9} = 10^8 \text{Hz} = 100 \text{MHz}$
 - This is where the MHz and GHz numbers for chips come from – how fast the clock oscillates




Timing in Circuits

 - Assume an **and** gate has a delay of 4ns and an **inverter** has a delay of 2ns:



- The propagation delay, t_p , may differ between different inputs and outputs in the same circuit
- If we report a single number, we always use the worst (i.e. longest path)



Timing of Latches

  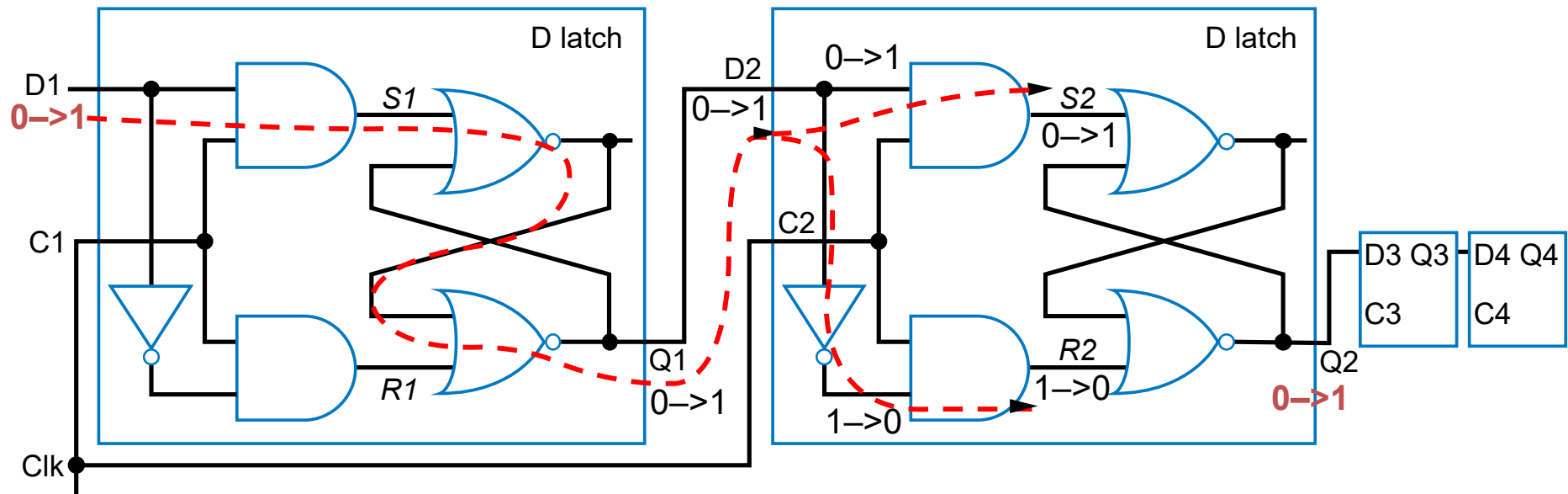


Transparent (level-sensitive) latches are problematic!!

Recap: Edge-Triggered Flip-Flops

- Use an edge triggered flip-flop to overcome the limitation of D latches
- We build edge-triggered flip-flops using two D-latches in a master-slave arrangement.
- A **flip-flop** is a circuit that changes its outputs only at the **control signal's edges**
 - **Positive edge-triggered**: output changes when control goes from 0 to 1
 - **Negative edge-triggered**: output changes when control goes from 1 to 0

 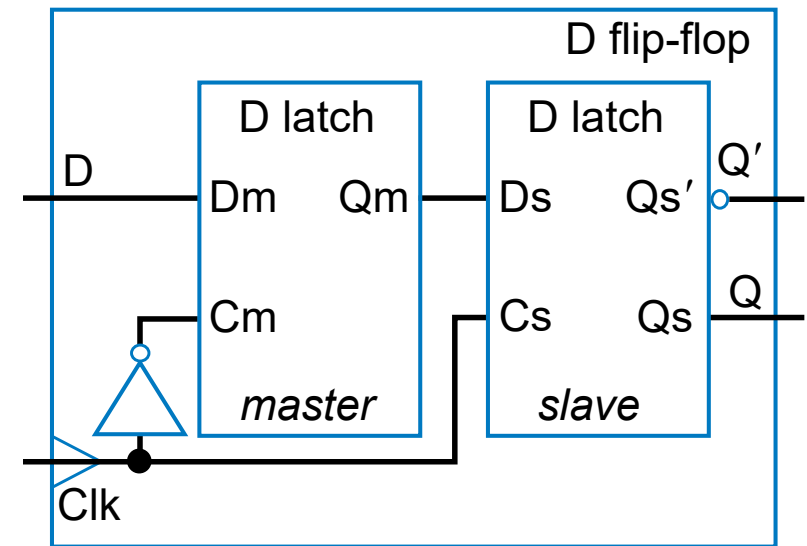


The Internals are not important

 


Recap: Edge Triggered Flip-Flops

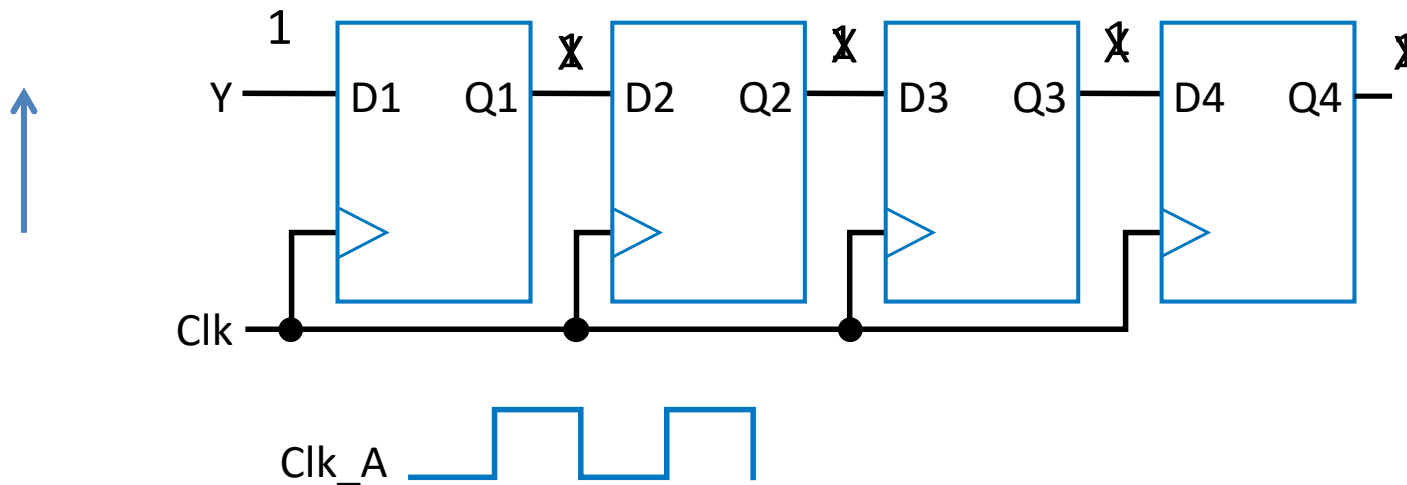- Use edge triggered flip-flops to overcome the limitation of D latches
 - Apply a 1 to the input. The current state of the FFs is unknown (X)




Recap: Edge Triggered Flip-Flops

 - Use edge triggered flip-flops to overcome the limitation of D latches



The duty cycle of the clock has no impact on the FF operation.

Exercise 3

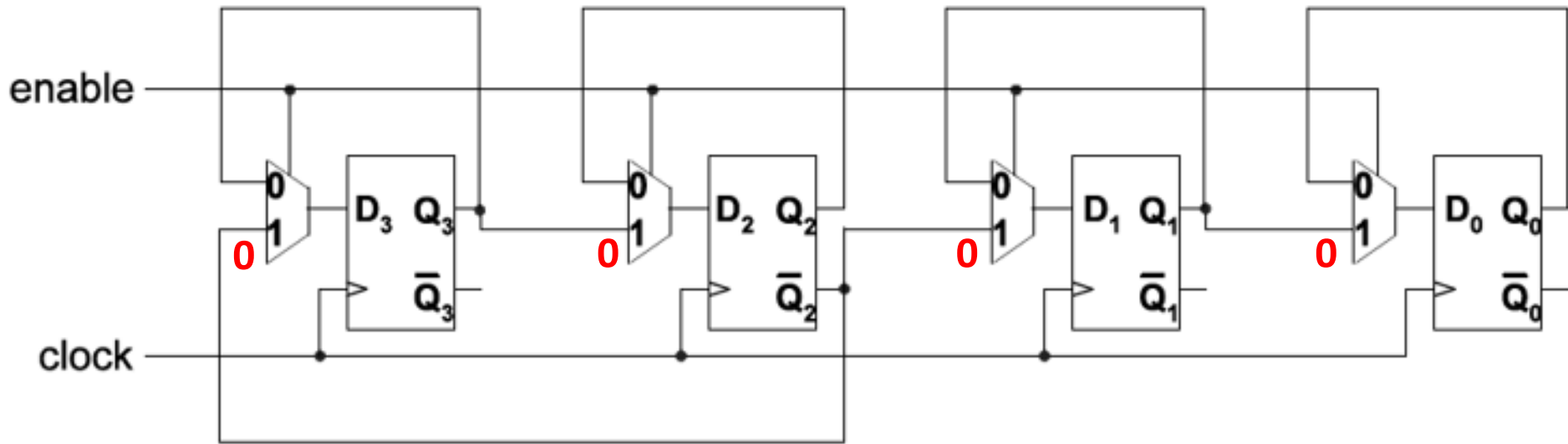

If $enable = 1$ and the current state of the circuit is $Q_3Q_2Q_1Q_0 = 0101$, what is the next state?

- A. 1111
B. 1010
C. 1100
D. 0011
E. 0000

Ans: E = 0000


Q_2 is '1', so $Q_2' = '0'$. Q_3 and Q_1 will be '0' at the next rising edge. The other outputs will just propagate through.

What is the next state if enable=0 and $Q_3Q_2Q_1Q_0 = 0101$?


Ans: $Q_3Q_2Q_1Q_0 = 0101$ (No change)

Edge-Triggered Flip-Flops

 
- We've seen the D flip-flop:
 - Q takes the value on D at the rising edge of C
- There's also a J-K flip-flop:
 - At the rising edge, Q becomes 1 if J is asserted and 0 if K is asserted
 - If both J and K are asserted, the output toggles at the rising edge
- And a T flip-flop:
 - Q toggles at the rising edge if T=1



clk	D	Q+
↑	0	0
↑	1	1
	X	Q

 

clk	J	K	Q+
↑	0	0	Q
↑	0	1	0
↑	1	0	1
↑	1	1	Q'
	X	X	Q

 


clk	T	Q+
↑	0	Q
↑	1	Q'
	X	Q

- (Also a lesser seen SR flip-flop)



Registers

- A **flip-flop** is a circuit that changes its outputs only at the **control signal's edges**

 - Positive edge-triggered
- Negative edge-triggered




  - The D-type flip-flop is the fundamental building block in synchronous design
- But we often deal with multi-bit signals
- When we combine multiple D flip-flops together to store multiple bits, we call this a **register**:



Registers

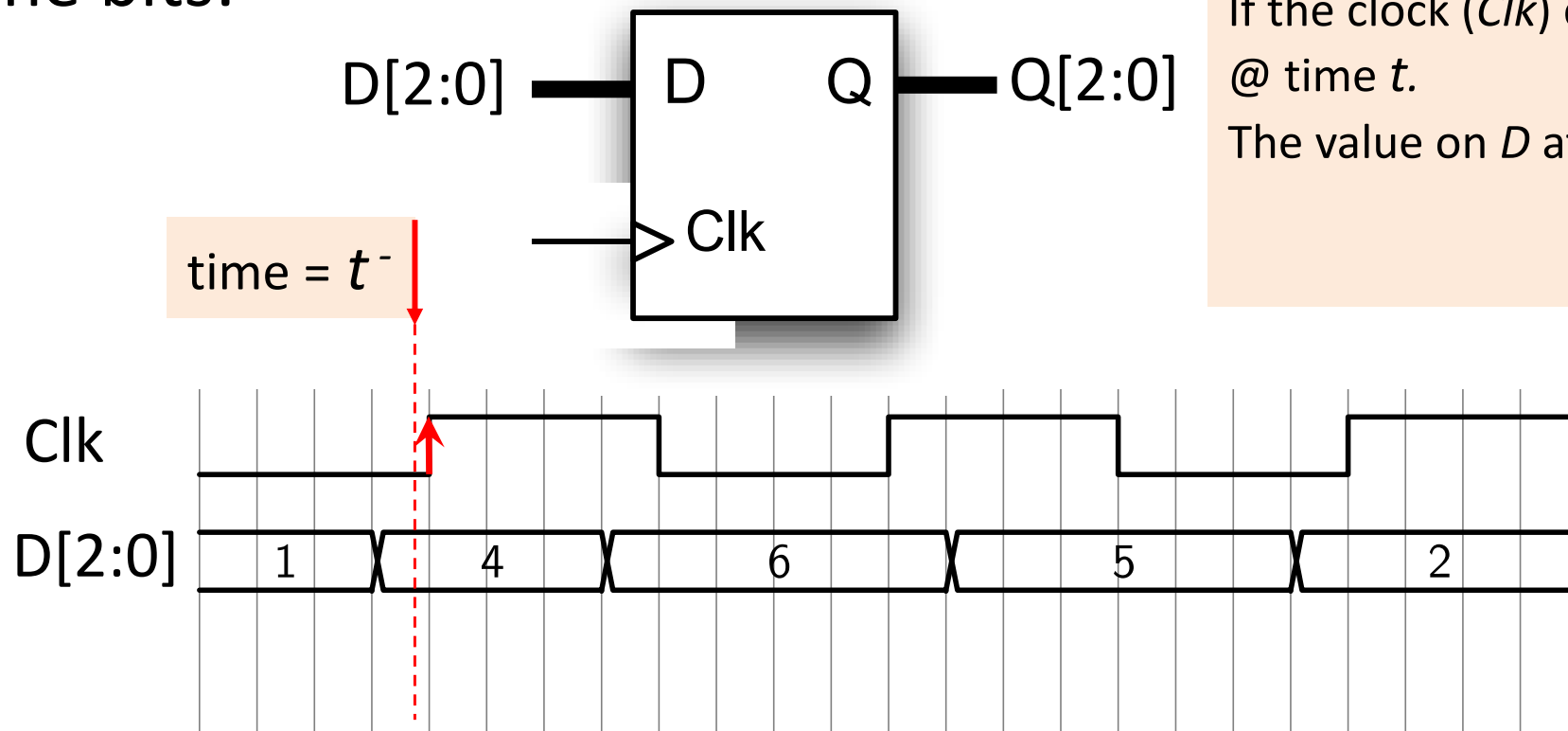
- When dealing with multi-bit registers, we can show these values in a timing diagram without splitting up the bits:



If the clock (Clk) changes @ time t .
The value on D at time t^-

Registers

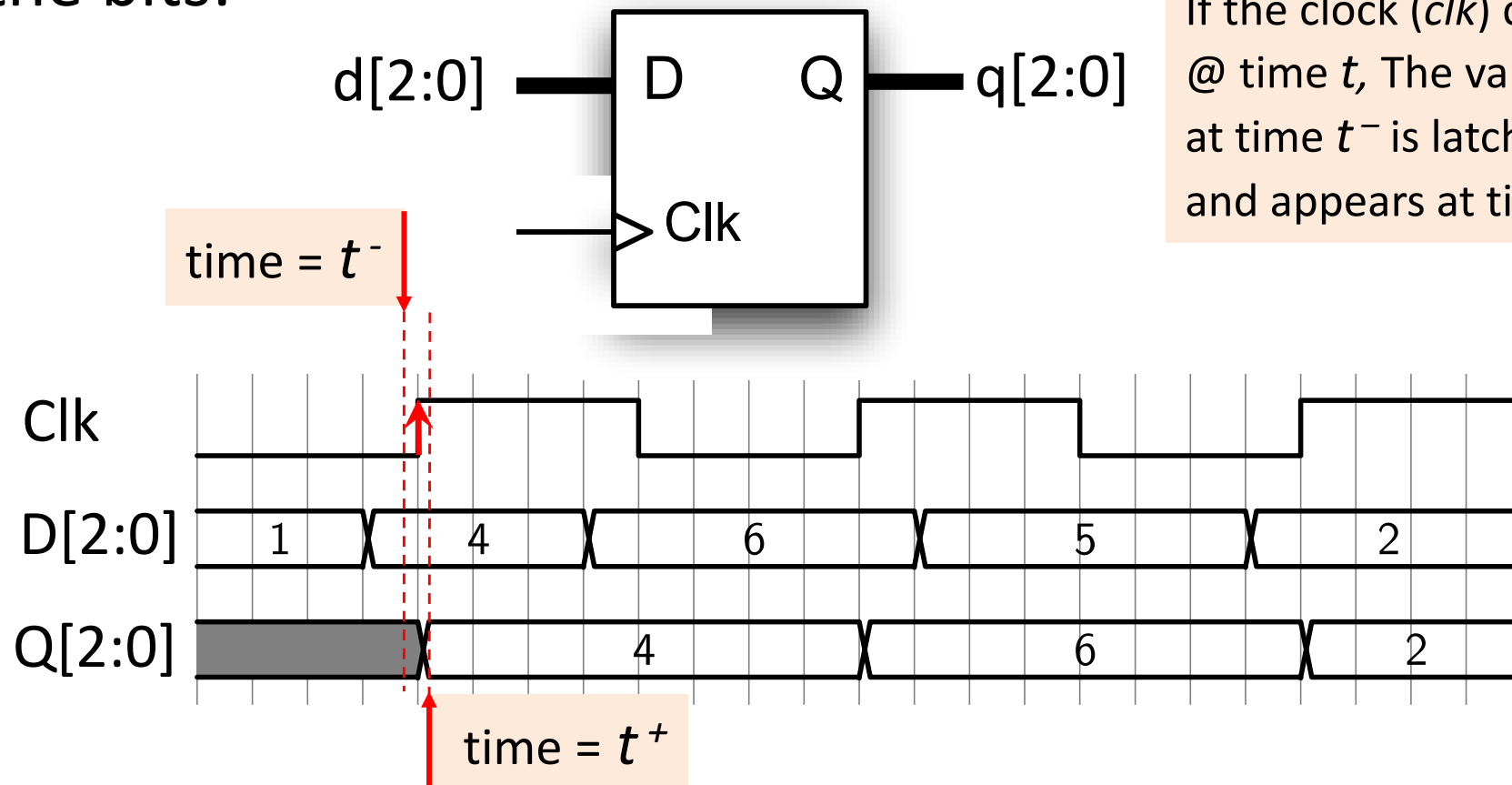
- When dealing with multi-bit registers, we can show these values in a timing diagram without splitting up the bits:



- We can use decimal or hex (or even binary), but make it clear
- Again, transitions only happen at the rising edge


Lecture 18 (Task 1)

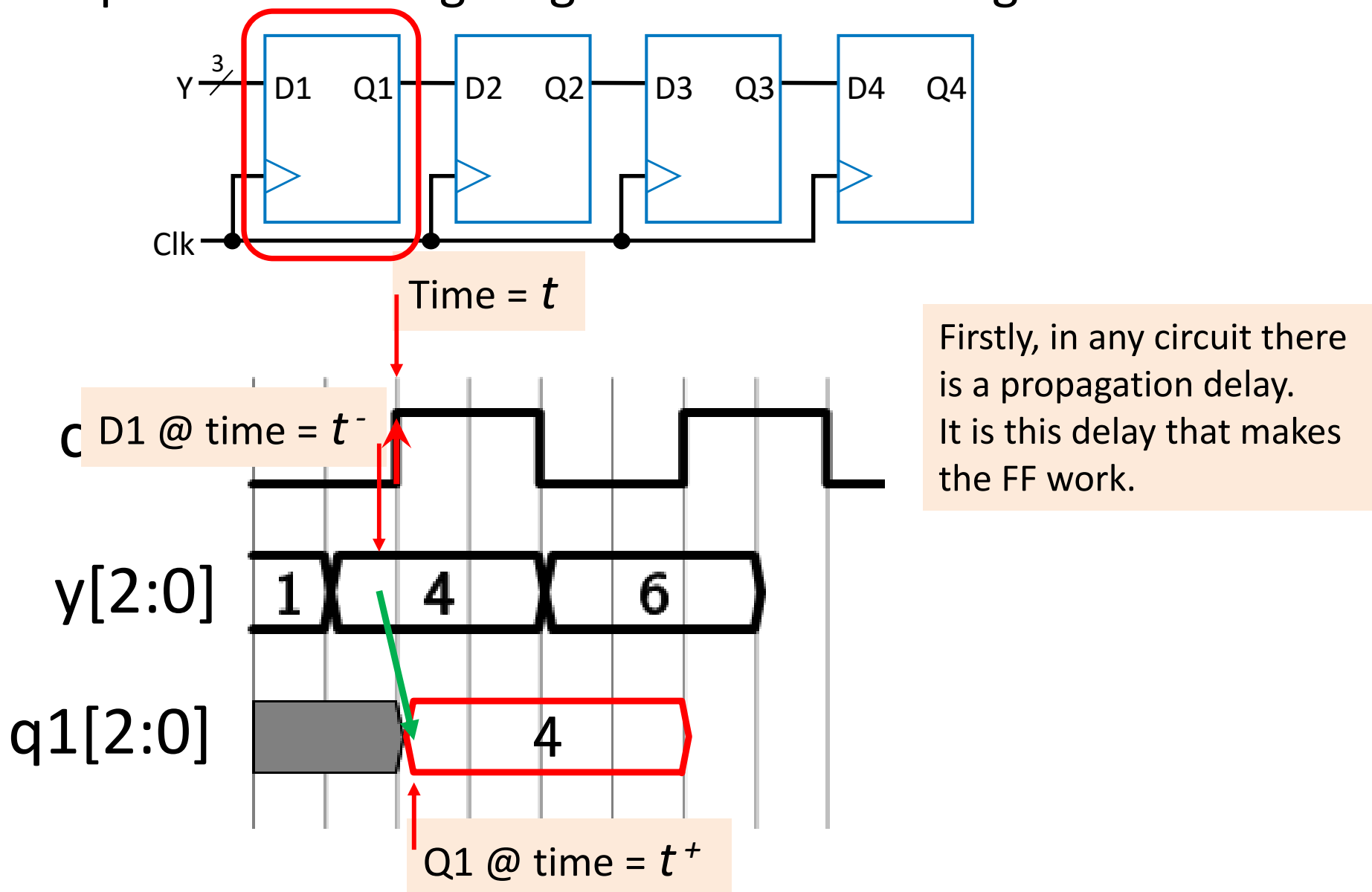- Complete the timing diagram of the shift register




Lecture 18 (Task 1)

 - Complete the timing diagram of the shift register



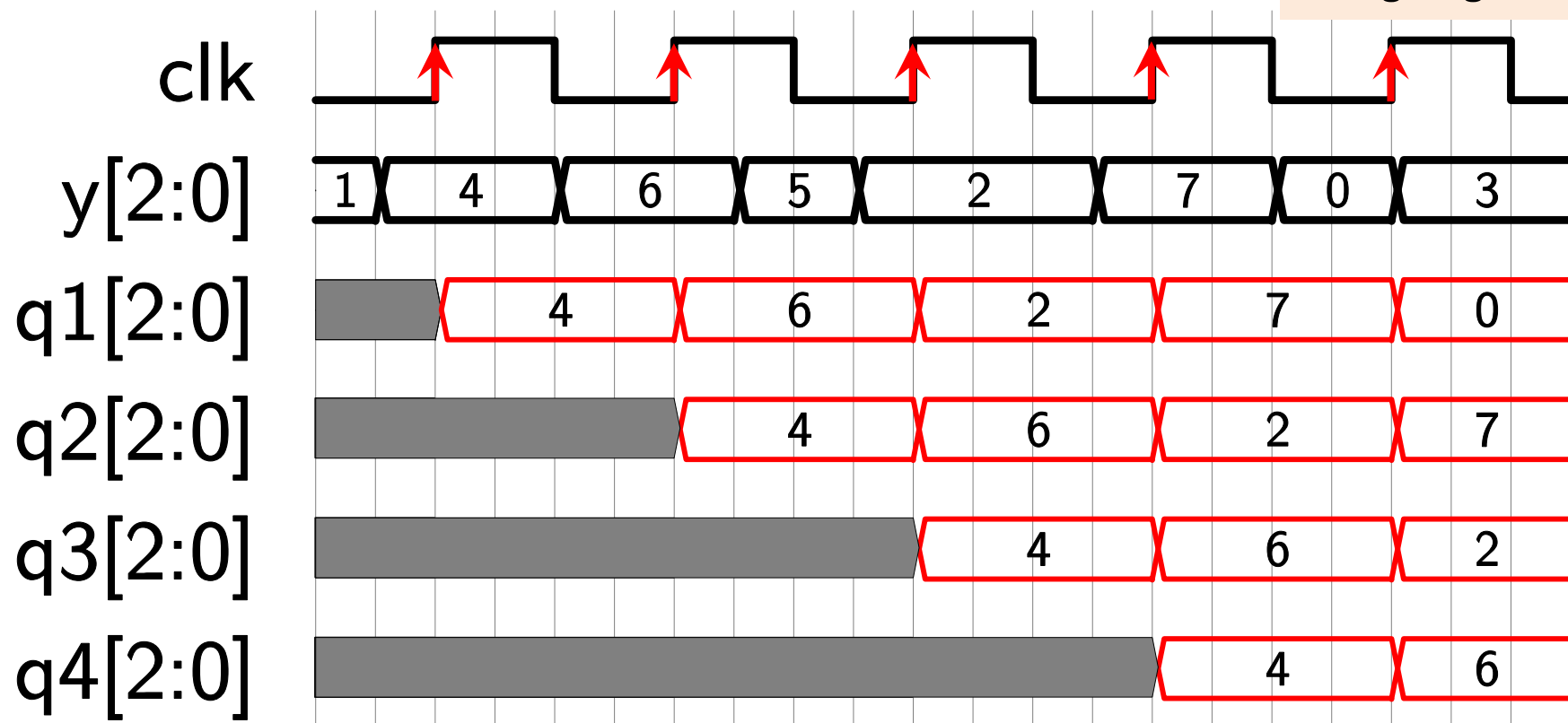Note all four 3-bit registers produce an output at the same time. Just after each clk rising edge.



Selected Past Exam Questions



CE/CZ1005 2017-2018 Semester 2 (Apr/May 2018)

Q4(a) Differentiate between a level-sensitive D-latch and edge-triggered D-flip-flop with the help of a timing diagram.

(5 marks)

ANS: A level sensitive D-latch will propagate signals through the latch when the enable signal is high. An edge triggered D-FF uses a master-slave arrangement so that the signals move through the FF only during the clock transition period.

Consider:

  


Selected Past Exam Questions

CE/CZ1005 2017-2018 Semester 1 (Nov/Dec 2017)

 Q4(a) What is a SR latch? Briefly describe how it works.

(6 marks)

ANS: A latch has 2 stable states, $Q=1$ and $Q=0$. A SR latch sets Q to 1 when $S=1$ and resets Q to 0 when $R=1$. When $S=R=0$ the latch holds its value. The output is undefined when $S=R=1$. The simplest SR latch is constructed using cross-coupled NOR gates. It is defined by:



S	R	Q+	Function
0	0	Q	Store
0	1	0	Reset
1	0	1	Set

