

L7 (5.1 – 5.23)

- Minterm and maxterm
- Canonical Boolean expressions
- SOP and POS expressions
- Active-high and active-low logic signals

5. Combinational Logic Circuits

- The most common type of digital logic circuits
- Made up of combinations of logic gates
- At any point in time, the output logic level only depends on the present combination of logic levels at the N inputs
 - $O(t) = f [I_1(t), I_2(t), I_3(t), \dots, I_N(t)]$
- It has no memory characteristics, unlike sequential circuits
- Relatively easy to analyse and design compared to sequential circuits

Designing and Implementing a Combinational Logic Circuit

- The function of a required logic circuit can be fully described by a truth table
- To design the circuit, we obtain the Boolean expression from the truth table
- The Boolean expression can then be implemented using a proper choice of logic gates

A Boolean expression is also known as

- **a Boolean equation**
- **a logic function**

**It fully describes, algebraically,
the logic circuit's output in response
to every possible input condition.**

**For simple circuits, the expression can
usually be obtained by observation.**

Forms of Boolean Expressions

- **Canonical Form**
 - Sum of minterms expression (SOM)
 - Product of maxterms expression (POM)
- **Standard Form**
 - Sum of products expression (SOP)
 - Product of sums expression (POS)

- **minterms:**

- All possible combinations of a given set of Boolean variables formed by the **AND** operation

- **maxterms:**

- All possible combinations of a given set of Boolean variables formed by the **OR** operation

A logic circuit with 2 inputs X and Y will have these 4 minterms and maxterms:

| inputs | | minterms | | maxterms | |
|--------|---|---------------|----|-----------|----|
| X | Y | | | | |
| 0 | 0 | $X' \cdot Y'$ | m0 | $X + Y$ | M0 |
| 0 | 1 | $X' \cdot Y$ | m1 | $X + Y'$ | M1 |
| 1 | 0 | $X \cdot Y'$ | m2 | $X' + Y$ | M2 |
| 1 | 1 | $X \cdot Y$ | m3 | $X' + Y'$ | M3 |

A minterm or maxterm uniquely describes the input combination at a given time instant

A logic circuit with 3 inputs X, Y and Z will have these 8 minterms and maxterms:

| inputs | | | minterms | | maxterms | |
|--------|---|---|------------------------|----|----------------|----|
| X | Y | Z | | | | |
| 0 | 0 | 0 | $X' \cdot Y' \cdot Z'$ | m0 | $X + Y + Z$ | M0 |
| 0 | 0 | 1 | $X' \cdot Y' \cdot Z$ | m1 | $X + Y + Z'$ | M1 |
| 0 | 1 | 0 | $X' \cdot Y \cdot Z'$ | m2 | $X + Y' + Z$ | M2 |
| 0 | 1 | 1 | $X' \cdot Y \cdot Z$ | m3 | $X + Y' + Z'$ | M3 |
| 1 | 0 | 0 | $X \cdot Y' \cdot Z'$ | m4 | $X' + Y + Z$ | M4 |
| 1 | 0 | 1 | $X \cdot Y' \cdot Z$ | m5 | $X' + Y + Z'$ | M5 |
| 1 | 1 | 0 | $X \cdot Y \cdot Z'$ | m6 | $X' + Y' + Z$ | M6 |
| 1 | 1 | 1 | $X \cdot Y \cdot Z$ | m7 | $X' + Y' + Z'$ | M7 |

For N-inputs, there will be 2^N minterms

e.g. 4 inputs: a, b, c, d

- 13 in decimal = 1101 in binary
- Then **minterm m13** = a b c' d
- **maxterm M13** = a' + b' + c + d'
- 2 in decimal = 0010 in binary
- Then **minterm m2** = a' b' c d'
- **maxterm M2** = a + b + c' + d

- **Minterms** are formed such that given a set of input conditions, only the corresponding minterm (but not the other minterms) will **yield a logic 1**.
- Eg. $x=0, y=1, z=1$ the corresponding minterm is m_3 , i.e. $x'yz$
- Substituting the values of x, y and z will result in $m_3 = x'yz = 0' \cdot 1 \cdot 1 = 1$
- Notice that by arranging x, y, z together to form a 3-bit binary number (MSB= x , LSB= z), the decimal equivalent is used to denote the minterm number ($011_2 = 3_{10}$ in this example)

- **Maxterms** are formed such that given a set of input conditions, only the corresponding maxterm (but not the other maxterms) will **yield a logic 0**.
- eg. $x=1, y=0, z=1$ the corresponding maxterm is M_5 , i.e. $x' + y + z'$
- Substituting the values of x, y and z will result in $M_5 = x' + y + z' = 1' + 0 + 1' = 0$
- Notice that arranging x, y, z together to form a 3-bit binary number (MSB= x , LSB= z), the decimal equivalent is used to denote the maxterm number ($101_2 = 5_{10}$ in this example)

The Sum of minterms expression

To write the sum-of-minterms

Boolean expression from a truth table:

- **For each combination of the input variables that produces a logic 1 in the output, collect the corresponding minterms and **OR** them together**

The Product of maxterms Expression

- For each combination of the input variables that produces a logic 0 in the output, collect the corresponding maxterms and **AND** them together
- Conversion between the two forms is easy.
- Sum of minterms expression is associated with **active HIGH** output.
- Product of maxterms expression is associated with **active LOW** output.

Example: given the truth table, obtain the SOM and POM expressions for output F

| inputs | | | Output F |
|--------|---|---|-------------|
| X | Y | Z | |
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

| inputs | | | minterms | | maxterms | | F |
|--------|---|---|------------------------|----|----------------|----|---|
| X | Y | Z | | | | | |
| 0 | 0 | 0 | $X' \cdot Y' \cdot Z'$ | m0 | $X + Y + Z$ | M0 | 0 |
| 0 | 0 | 1 | $X' \cdot Y' \cdot Z$ | m1 | $X + Y + Z'$ | M1 | 1 |
| 0 | 1 | 0 | $X' \cdot Y \cdot Z'$ | m2 | $X + Y' + Z$ | M2 | 1 |
| 0 | 1 | 1 | $X' \cdot Y \cdot Z$ | m3 | $X + Y' + Z'$ | M3 | 0 |
| 1 | 0 | 0 | $X \cdot Y' \cdot Z'$ | m4 | $X' + Y + Z$ | M4 | 1 |
| 1 | 0 | 1 | $X \cdot Y' \cdot Z$ | m5 | $X' + Y + Z'$ | M5 | 0 |
| 1 | 1 | 0 | $X \cdot Y \cdot Z'$ | m6 | $X' + Y' + Z$ | M6 | 0 |
| 1 | 1 | 1 | $X \cdot Y \cdot Z$ | m7 | $X' + Y' + Z'$ | M7 | 1 |

$$F = X'Y'Z + X'YZ' + XY'Z' + XYZ$$

$$= \Sigma_{XYZ} (1, 2, 4, 7)$$

SOM

$$F = (X+Y+Z) (X+Y'+Z') (X'+Y+Z') (X'+Y'+Z)$$

$$= \Pi_{XYZ} (0, 3, 5, 6)$$

POM

Other ways of writing canonical expressions:

$$F = \sum_{XYZ} (1, 2, 4, 7)$$

SOM

$$F(X, Y, Z) = \sum m (1, 2, 4, 7)$$

$$F(X, Y, Z) = m_1 + m_2 + m_4 + m_7$$

$$F = \prod_{XYZ} (0, 3, 5, 6)$$

POM

$$F(X, Y, Z) = \prod M (0, 3, 5, 6)$$

$$F(X, Y, Z) = M_0 \cdot M_3 \cdot M_5 \cdot M_6$$

Interpretation of **active High** and **active Low** for the above example:

| Value of Output F | Interpretation of output F | |
|-------------------|---|--|
| | There is an <u>odd</u> number of 1's among the 3 inputs X, Y, Z | There is an <u>even</u> number of 1's among the 3 inputs X, Y, Z |
| 1 (High) | TRUE | FALSE |
| 0 (Low) | FALSE | TRUE |

- E.g. rename F as **ODD**, which is **active High** (usually write Som expression)
- E.g. rename F as **EVEN***, which is **active Low** (usually write PoM expression)

Standard Form of Boolean Expressions

- **SOP and POS**
- **Simplified expressions from the canonical forms**
- **Leads to simpler logic circuits**
- **Known as combinational circuit minimisation**
- **Minimise the number of gates (minimum number of product terms or sum terms)**
- **Minimise the number of inputs on each gate (minimum number of input variables in each product term and sum term)**

Sum of products (SOP) expression

example:

This is a sum-of-minterms expression:

$$f(x, y, z) = xyz' + xyz + x'y'z + xy'z$$


Simplifying, we get

$$\begin{aligned} f(x, y, z) &= xy(z' + z) + (x' + x)y'z \\ &= xy + y'z \end{aligned}$$

This is now a sum-of-products expression.

A **product term** need not contain all the input variables, unlike a **minterm**.

Product of sums (POS) expression

example:

This is a product-of-maxterms expression:

$$f(x, y, z) = (x+y'+z')(x+y'+z)(x'+y'+z)(x'+y+z)$$


Simplifying, we get

$$f(x, y, z) = (x + y')(x' + z)$$

This is now a product-of-sums expression.

A **sum term** need not contain all the input variables, unlike a **maxterm**.

These are **neither SOP nor POS** expressions:

$$f = (xy)'z + xz'$$

not a product term

$$f = xy(x' + z)'$$

not a sum term

$$f = (xy + z)(x' + y)$$

not a sum term

Use the standard form (i.e. SOP or POS) wherever possible.

Obtaining Simplified Standard Expressions from the Canonical Form

- **Different methods for Boolean expression simplification**
 - Algebraic method
 - Karnaugh map (K-map)
 - Quine-McCluskey method (Q-M method or tabulation method)
 - Heuristic methods, e.g. Espresso-II

Simplified Boolean expressions yield

- **Simpler circuits with fewer logic gates**
- **Fewer connections**
- **Lower cost**
- **Improved reliability**

Algebraic method

- **Use Boolean theorems**
- **Requires experience and skills**

**Examples:
simplify**

$$Z = ABC + AB'(A'C')'$$



$$Z = AB' + AC$$

simplify

$$X = (A' + B)(A + B + D)D'$$



$$X = BD'$$

L8 (5.24 – 5.48)

- Karnaugh map to simplify Boolean expression
- What to do with “Don’t cares”
- How to enable or disable a circuit

Karnaugh Map

- Graphical method
- Easier to use than algebraic method
- Based on the Boolean theorems
$$AB + AB' = A(B + B') = A \text{ (for SOP)}$$
$$(A+B)(A+B') = A \text{ (for POS)}$$
- Truth table gives value of output X for each combination of input values. K-map gives the same info in a different format.

- K-map squares are labelled such that adjacent squares differ only in one variable.
- **SOP** expression for output X can be obtained by **OR**ing together those squares that contain a **1**.
- Can also obtain **POS** expression by **AND**ing together those squares that contain a **0**.
- Note the correspondence with **SOM** (think **1**) and **POM** (think **0**).

Truth Table to K-Map Conversion [2 Inputs]

$$X = A'B' + AB$$

| A | B | X |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

K-map

| X | B=0 | B=1 |
|-----|-----|-----|
| A=0 | 1 | 0 |
| A=1 | 0 | 1 |

Truth Table to K-Map Conversion [3 Inputs]

$$X = A'B'C' + A'B'C + A'BC' + ABC'$$

| A | B | C | X |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

K-map

| X | C=0 | C=1 |
|---------|-----|-----|
| A=0,B=0 | 1 | 1 |
| A=0,B=1 | 1 | 0 |
| A=1,B=1 | 1 | 0 |
| A=1,B=0 | 0 | 0 |

Truth Table to K Map Conversion [4 Inputs]

| A | B | C | D | X |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

$$X = A'B'C'D + A'BC'D + ABC'D + ABCD$$


| | | | | | |
|------|-----|------|-----|-----|-----|
| | | C, D | | | |
| | | | | | |
| A, B | X | 0 0 | 0 1 | 1 1 | 1 0 |
| | 0 0 | 0 | 1 | 0 | 0 |
| | 0 1 | 0 | 1 | 0 | 0 |
| | 1 1 | 0 | 1 | 1 | 0 |
| | 1 0 | 0 | 0 | 0 | 0 |

Truth Table to K Map Conversion [4 Inputs]


| A | B | C | D | dec |
|---|---|---|---|-----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 2 |
| 0 | 0 | 1 | 1 | 3 |
| 0 | 1 | 0 | 0 | 4 |
| 0 | 1 | 0 | 1 | 5 |
| 0 | 1 | 1 | 0 | 6 |
| 0 | 1 | 1 | 1 | 7 |
| 1 | 0 | 0 | 0 | 8 |
| 1 | 0 | 0 | 1 | 9 |
| 1 | 0 | 1 | 0 | 10 |
| 1 | 0 | 1 | 1 | 11 |
| 1 | 1 | 0 | 0 | 12 |
| 1 | 1 | 0 | 1 | 13 |
| 1 | 1 | 1 | 0 | 14 |
| 1 | 1 | 1 | 1 | 15 |

| | | | | | |
|------|-----|------|-----|-----|-----|
| | | C, D | | | |
| | | X | | | |
| | | 0 0 | 0 1 | 1 1 | 1 0 |
| A, B | 0 0 | 0 | 1 | 3 | 2 |
| | 0 1 | 4 | 5 | 7 | 6 |
| | 1 1 | 12 | 13 | 15 | 14 |
| | 1 0 | 8 | 9 | 11 | 10 |

Kmap: Looping 2 “neighbouring” 1’s

 

Kmap: Looping 4 “neighbouring” 1’s

 

Kmap: Looping 8 “neighbouring” 1’s

A, B

| | | | | |
|------------|-------------|------------|------------|------------|
| X | C, D | | | |
| | 0 0 | 0 1 | 1 1 | 1 0 |
| 0 0 | 0 | 1 | 1 | 0 |
| 0 1 | 0 | 1 | 1 | 0 |
| 1 1 | 0 | 1 | 1 | 0 |
| 1 0 | 0 | 1 | 1 | 0 |

A red circle highlights the 8 '1's in the central 4x2 area of the Kmap. A red arrow points from the top-right corner of this circle to a red **D**.

Note these rules on Kmap for simplification:

- Loop **1**'s to obtain **SOP** expression.
 - Only 2^N number of “neighbouring” 1's can be looped together.
 - No looping along diagonal.
 - All **1**'s must be looped.
 - Use the biggest loops and the fewest loops.
 - A square(s) may be looped more than once.
 - **Each loop of 1's will yield a product term.**
-
- **0**'s can also be looped in a similar manner to obtain **POS** expression.
 - **Each loop of 0's will yield a sum term.**

Example: Simplify the Boolean expression for output Z using K-map

| A | B | C | D | Z |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

Example (cont)

Step 1 : Convert truth table to K-map

Step 2 : Loop adjacent 1's to get SOP

| | CD | | | |
|----|----|----|----|----|
| Z | 00 | 01 | 11 | 10 |
| 00 | 0 | 0 | 0 | 0 |
| 01 | 0 | 0 | 1 | 0 |
| 11 | 1 | 1 | 1 | 1 |
| 10 | 1 | 1 | 1 | 1 |

AB

BCD


A

$$Z = A + BCD$$

Example (cont)

Alternatively

Step 2 : Loop adjacent 0's to get POS

 

$$Z = (A + B)(A+C)(A+D)$$

Don't care conditions

- **Some logic circuits can be designed such that there are certain input conditions for which there are **no specified output levels**.**
- **This is possible because**
 - **These input conditions will not occur**
 - **It does not matter whether the output is 0 or 1**
- **The designer is free to make the output for any “don't care” condition to be 0 or 1 in order to produce the simplest output expression.**

Example: Design a logic circuit whose input is a BCD digit, and whose output goes HIGH if the input is smaller than 6_{10}

| A | B | C | D | Z |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | X |
| 1 | 0 | 1 | 1 | X |
| 1 | 1 | 0 | 0 | X |
| 1 | 1 | 0 | 1 | X |
| 1 | 1 | 1 | 0 | X |
| 1 | 1 | 1 | 1 | X |

X denotes “don’t care”

Example (cont):

Design 1: SOP

$$Z = A'B' + A'C'$$

| | | CD | | | |
|----|---|----|----|----|----|
| Z | | 00 | 01 | 11 | 10 |
| 00 | 1 | 1 | 1 | 1 | 1 |
| 01 | 1 | 1 | 0 | 0 | 0 |
| 11 | X | X | X | X | X |
| 10 | 0 | 0 | X | X | X |

AB

X denotes “don’t care”

Example (cont):

Design 2: SOP

$$Z = A'B' + BC'$$

| | | CD | | | |
|----|---|----|----|----|----|
| Z | | 00 | 01 | 11 | 10 |
| 00 | 1 | 1 | 1 | 1 | 1 |
| 01 | 1 | 1 | 0 | 0 | 0 |
| 11 | X | X | X | X | X |
| 10 | 0 | 0 | X | X | X |

AB

X denotes “don’t care”

Example (cont):

Design 3: SOP

$$Z = B'C + A'C'$$

| | CD | | | |
|----|----|----|----|----|
| Z | 00 | 01 | 11 | 10 |
| 00 | 1 | 1 | 1 | 1 |
| 01 | 1 | 1 | 0 | 0 |
| 11 | X | X | X | X |
| 10 | 0 | 0 | X | X |

AB

X denotes “don’t care”

Example (cont):

Design 4: POS

$$Z = (A' + B + C)(A + B' + C')$$

| | CD | | | |
|----|----|----|----|----|
| Z | 00 | 01 | 11 | 10 |
| 00 | 1 | 1 | 1 | 1 |
| 01 | 1 | 1 | 0 | 0 |
| 11 | X | X | X | X |
| 10 | 0 | 0 | X | X |

AB

X denotes “don’t care”

Example (cont):

Design 5: POS

$$Z = A' (B' + C')$$

| | CD | | | |
|----|----|----|----|----|
| Z | 00 | 01 | 11 | 10 |
| 00 | 1 | 1 | 1 | 1 |
| 01 | 1 | 1 | 0 | 0 |
| 11 | X | X | X | X |
| 10 | 0 | 0 | X | X |

AB

X denotes “don’t care”

Don't cares

- “Don't cares” can be looped in a similar way on the Karnaugh map.
- When looped with **1**'s to write **SOP** expression, the “don't care” is treated as **1**. Those “don't cares” not looped are treated as **0**.
- Conversely, when looped with **0**'s to write **POS** expression, the “don't care” is treated as **0**. Those “don't cares” not looped are treated as **1**.
- “Don't cares” should only be looped if it helps to simplify a Boolean expression (i.e. helps to form a bigger loop).

Summary: Designing a Combinational Logic Circuit

- 1 From problem specifications, derive the relationship between the output(s) and the inputs. This can be expressed in the form of a truth table.**
- 2 Obtain the Boolean expression that relates the desired output to the inputs. It can either be in SOP or POS form, although SOP is usually used.**
- 3 Simplify the expression using either algebraic, K-map or QM method.**
- 4 Implement the circuit from the simplified expression. Certain restrictions may need to be taken into account, eg. use only 2-input NAND gates.**

Enable/Disable Circuits

Enable

A logic circuit is said to be enabled if the **output is allowed to change** in response to changes in the inputs.

Disable/Inhibit

A logic circuit is said to be disabled/inhibited if the **output is not allowed to change** in response to changes in the inputs.

The output is either fixed at 0 (typically for active High output) or 1 (typically for active Low output).

 
 
 
 
 
 
 
 


Fig. 4-26 (Tocci 10th ed.)

Enable/Disable Example

| Inputs | | Output | Effect of output |
|------------|--------|--------|------------------|
| Child Safe | Unlock | Open | |
| 0 | X | 0 | Door closed |
| 1 | 0 | 0 | Door closed |
| 1 | 1 | 1 | Door opened |

X: “don’t care”, i.e. can be 0 or 1

- **Circuit is enabled when ChildSafe=1; the output Open changes with input Unlock.**
- **Circuit is disabled when ChildSafe=0; Open is stuck at 0.**