

SC1005

Tut 8

CE/CZ1005 Digital Logic

Tutorial 8

Q1. Using a behavioral description, write a Verilog module that has three 8-bit inputs, *a*, *b*, and *c*, and outputs the largest (max) and smallest (min) of them. Add a third output (*diff*) that outputs the difference between the two. Use if statement(s). You can ignore equal inputs.

Q2. The *clk* input in the timing diagram is connected to the control/enable/clock input of the following circuits:

SR-latch (no enable/control)

Enabled SR-latch


Enabled D-type latch

JK flip-flop



D flip-flop

For the D-type latch and D flip-flop, the *in1* input is connected to the D input, and *in2* is left disconnected. For the SR-latches, *in1* is connected to the S input and *in2* is connected to the R input. For the JK flip-flop, *in1* is connected to the J input and *in2* is connected to the K input.

 Complete the timing diagram showing the outputs of the four sequential circuits. Indicate any undefined output by shading the relevant area.



  Q3. A bank of 4-bit registers is arranged as per below, to form a FIFO, with a bitwise inversion in the middle. The input shown in the diagram is applied to the leftmost register. All registers share the same clock. Show a timing diagram for the rightmost register output. Write the resulting hexadecimal number sequence at the output.



Q1

```
module minmax(input [7:0] a, b, c,  
              output reg [7:0] max, min,  
              output [7:0] diff);  
    assign diff = max - min;  
    always @ *  
    begin  
        if (a>b)  
            begin  
                if (c>a)  
                    begin  
                        min = b;  
                        max = c;  
                    end  
                else  
                    begin  
                        max = a;  
                        if (c>b) min = b;  
                        else min = c;  
                    end  
            end  
    end  
end
```

```
    else // a<b  
        begin  
            if (c>b) begin  
                min = a;  
                max = c;  
            end  
            else  
                begin  
                    max = b;  
                    if (c>a) min = a;  
                    else min = c;  
                end  
            end  
        end  
    end  
endmodule
```

But, is this easy to read and understand?
Note: it is very easy to make syntax errors
when using nested conditional if statements.

An alternative Q1, which is much easier to read and understand.

```
module minmax(input [7:0] a, b, c,  
              output reg [7:0] max, min,  
              output [7:0] diff);  
  
    assign diff = max - min;  
  
    always @ *  
    begin  
        max = a;  
        if (b>max) max = b;  
        if (c>max) max = c;  
    end  
  
    always @ *  
    begin  
        min = a;  
        if (b<min) min = b;  
        if (c<min) min = c;  
    end  
endmodule
```


Q2 The rules:

SR-latch: ignore clk, when S (in1) is high, latch is set to 1, when R (in2) is high, latch is reset to 0, when both are high, the output is undefined, and may go metastable on de-assertion.

Enabled SR-latch: as above, but only consider inputs when E (clk) is high.

Enabled D-latch: when E (clk) is high, D (in1) should pass to the output.

 JK-flip-flop: the output only changes at the clock edge. J (in1)=1 sets the output high, K (in2)=1 sets the output low. Both J=1 & K=1 toggles the output. But all are only considered at the rising edge of clk.



S	R	Q+
0	0	Q
0	1	0
1	0	1
1	1	undef

Q2 The rules:


SR-latch: ignore clk, when S (in1) is high, latch is set to 1, when R (in2) is high, latch is reset to 0, when both are high, the output is undefined, and may go metastable on de-assertion.

Enabled SR-latch: as above, but only consider inputs when E (clk) is high.


Enabled D-latch: when E (clk) is high, D (in1) should pass to the output.

JK-flip-flop: the output only changes at the clock edge. J (in1)=1 sets the output high, K (in2)=1 sets the output low. Both J=1 & K=1 toggles the output. But all are only considered at the rising edge of clk.

 
D-flip-flop: the output will follow the D (in1) input at that the instance of the rising edge of clk.




S	R	Q+
0	0	Q
0	1	0
1	0	1
1	1	undef

 


E	S	R	Q+
0	X	X	Q
1	0	0	Q
1	0	1	0
1	1	0	1
1	1	1	undef

 


E	D	Q+
0	X	Q
1	0	0
1	1	1

 


clk	J	K	Q+
↑	0	0	Q
↑	0	1	0
↑	1	0	1
↑	1	1	Q'
	X	X	Q

 

clk	D	Q+
↑	0	0
↑	1	1
	X	Q

 

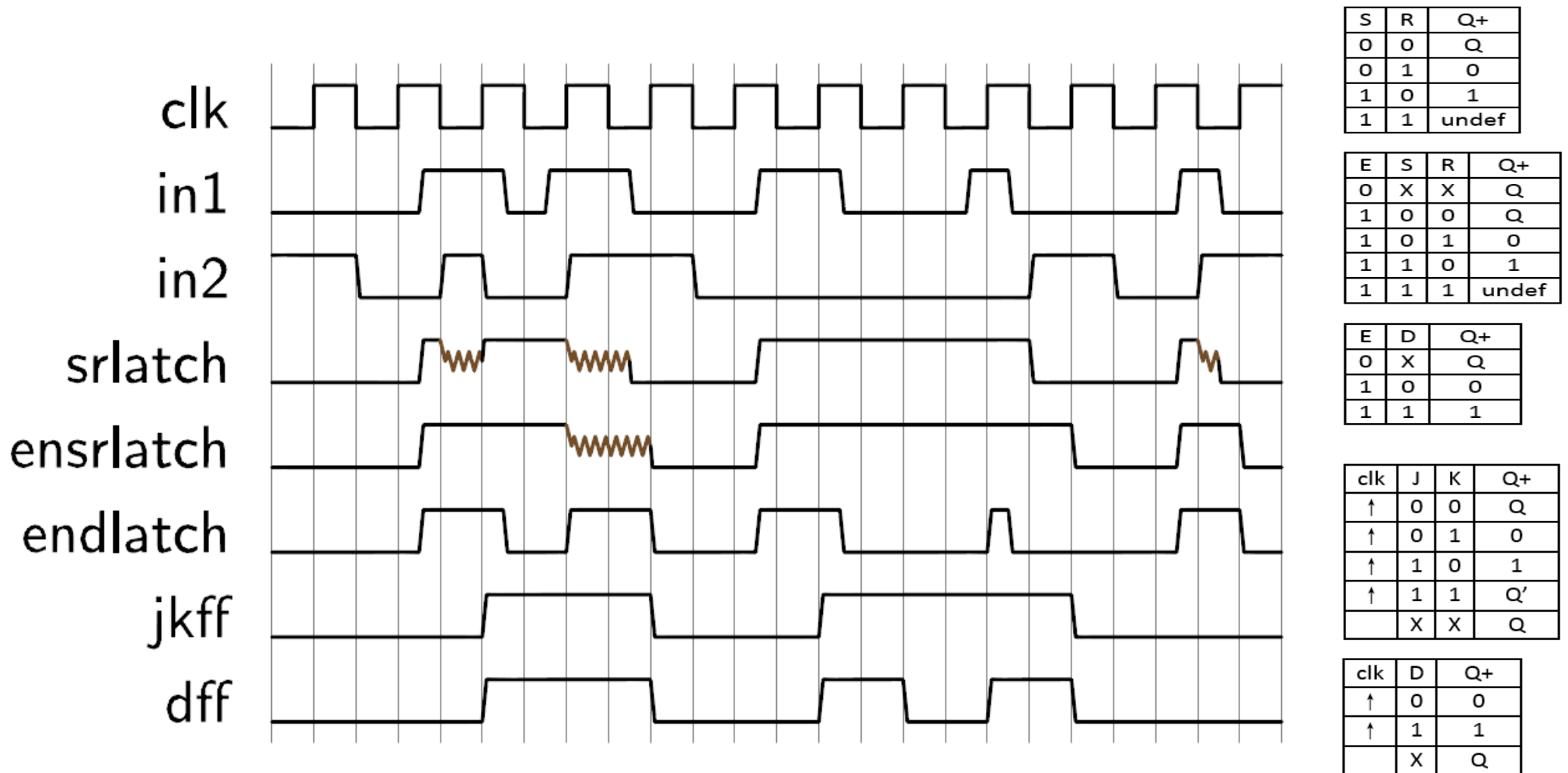Note: the output of an SR latch is undefined if the S and R inputs are both 1.



Note: the output of an SR latch is undefined if the S and R inputs are both 1.

- **Q3.** The extra signals in the timing diagram should give a hint as to how to do this. i.e. one step at a time. So, first annotate the diagram.
 - Remember, each register's output only changes at the rising edge. Hence, some inputs are missed. It is important to remember that the input value passed to the output is the one **just** before the rising edge.

