


Both active-high x and active-low y^* are asserted. Which one below is true?


 **A. $x=1, y^*=0$**

B. $x=0, y^*=1$

C. $x=1, y^*=1$

D. $x=0, y^*=0$

Both active-high x and active-low y^* are negated. Which one below is true?

- A. $x=1, y^*=0$
-  B. $x=0, y^*=1$
- C. $x=1, y^*=1$
- D. $x=0, y^*=0$

Interpretation of logic expressions

Example 1: all signals active high

$$F = A' B (C+D)$$

$F=1$
F is asserted iff

- A is asserted / negated, and
- B is asserted / negated, and
- either C or D is asserted / negated

$A=0$

$B=1$

$C+D=1$

Interpretation of logic expressions

Example 2: all signals active low

$$G^* = 0$$

$$G^* = A^{*'} B^* (C^* + D^*)$$

G^* is asserted iff

• A^* is asserted / **negated**, or

• B^* is **asserted** / **negated**, or

• C^* and D^* are both **asserted** / **negated**

$$A^* = 1$$

$$B^* = 0$$

$$C^* + D^* = 0$$

Interpretation of logic expressions

Example 3: mixed signals

$$W = A^* \cdot B' (C + D^*)$$

$W=1$
 W is asserted iff

- A^* is asserted / negated, and
- B is asserted / negated, and
- either C is asserted / negated or D^* is asserted / negated

$$A^* = 0$$

$$B = 0$$

$$C + D^* = 1$$

Interpretation of logic expressions

Example 4: mixed signals

$$V^* = 0$$

$$V^* = A^{*'} B' + C + D^*$$

V^* is asserted iff

• A^* is asserted / **negated** or B is

asserted / **negated**, and

• C is asserted / **negated**, and

• D^* is **asserted** / **negated**


$$A^* = 1$$

$$B = 1$$


$$C = 0$$

$$D^* = 0$$

 Enable input EN: active high or active low?



 
Enable input EN: active high or active low?



**Inputs A, B, C*, D* and output F.
F is only asserted when either A or C*
is asserted (but not both), and either B
or D* is negated (but not both).**

$$F(A,B,C^*,D^*)=$$

A. $\sum m(0, 2, 8, 12)$

 B. $\sum m(0, 5, 10, 15)$

C. $\sum m(0, 6, 12, 15)$

A
asserted

or

C*
asserted

but not both

and

B
negated


or

D*
negated

but not both

A	B	C*	D*	F	
0	0	0	0		m0
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		m5
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		m10
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		m15


 
How many parallel paths and serial paths are formed by the resistors?




- A. 2 parallel, 1 serial**
- B. 3 parallel, 2 serial**
- ✓ C. 3 parallel, 1 serial**

For a logic output to go high, current must flow from:

  
- A. V_{cc} to Gnd**
- ✓ B. V_{cc} to output**
- C. Output to Gnd**
- D. Output to V_{cc}**





Which circuit does it implement?

 


A.

 

B.

  


C.

 

D.



 

For $Z=0$

Both Q3 & Q1 must be ON, or

Both Q5 and Q7 must be ON

Q2, Q4, Q6, Q8 must be OFF
i.e. $A=B=1$, or $C=D=1$

For $Z=1$

Q2 or Q4 must be ON, and
Q6 or Q8 must be ON

Q1, Q3, Q5, Q7 must be OFF
i.e. $A=0$ or $B=0$, and
 $C=0$ or $D=0$

Fig. 3-20 Wakerly

Which circuit does it implement?

For $Z=0$

Both Q3 & Q1 must be ON, or

Both Q5 and Q7 must be ON

i.e. $A=B=1$, or $C=D=1$


For $Z=1$

Q2 or Q4 must be ON, and


Q6 or Q8 must be ON

i.e. $A=0$ or $B=0$, and $C=0$ or $D=0$


(A)

 


(B)

 

(C)

 

(D)

 


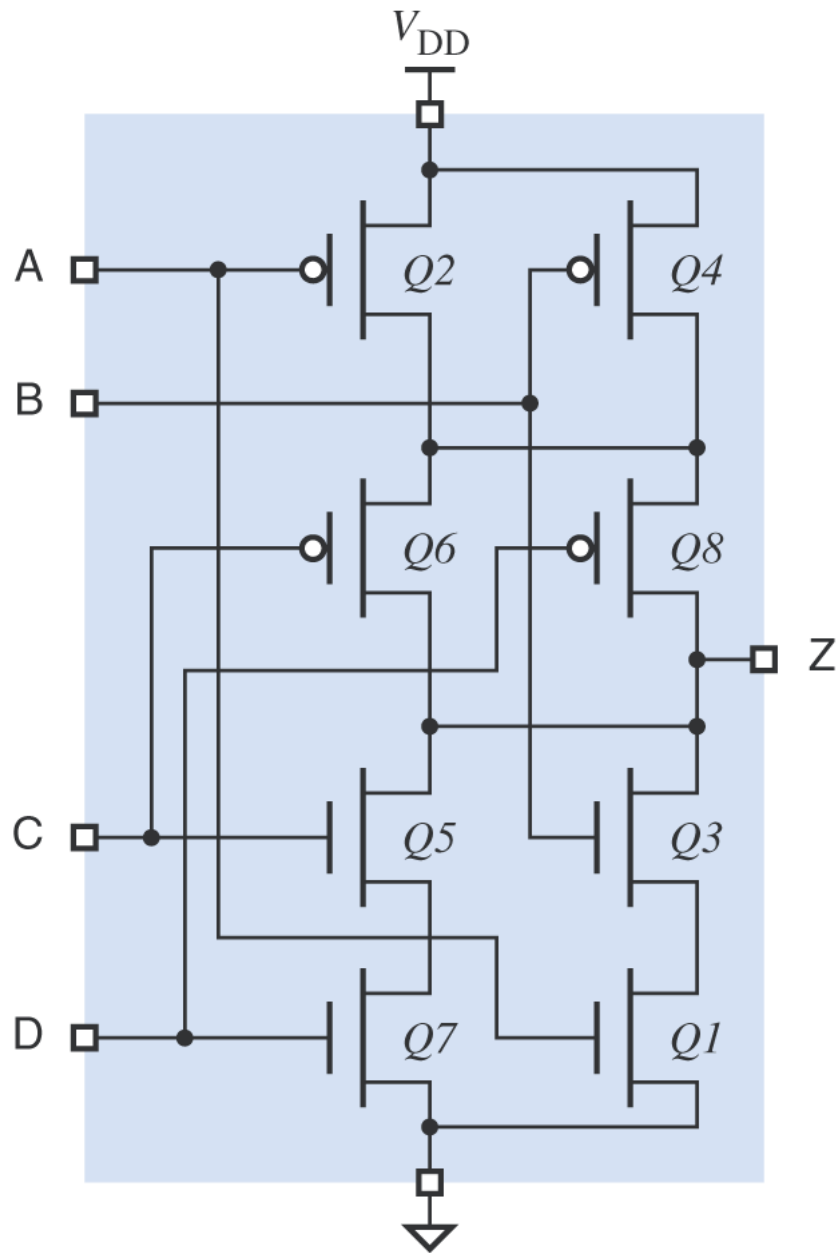


Fig. 3-20 Wakerly


**When A=B=1,
Q2 and Q4 OFF,
Q1 and Q3 ON
Z=0**

 **Similarly when C=D=1,
Q6 and Q8 OFF,
Q5 and Q7 ON
Z=0**



$$Z = (AB + CD)'$$

Which circuit does it implement?

 


A. $Z = (A+B)' (C+D)'$

B. $Z = (A'+B') (C'+D')$

C. $Z = (AB + CD)'$

✓ D. $Z = [(A+B) (C+D)]'$

 

For $Z=1$

**Both $Q2$ & $Q4$ must be ON,
or**

**Both $Q6$ and $Q8$ must be
ON**

**$Q1, Q3, Q5, Q7$ must be OFF
i.e. $A=B=0$, or $C=D=0$**

For $Z=0$

**$Q1$ or $Q3$ must be ON, and
 $Q5$ or $Q7$ must be ON**

**$Q2, Q4, Q6, Q8$ must be OFF
i.e. $A=1$ or $B=1$, and
 $C=1$ or $D=1$**

For $Z=1$

Both Q2 & Q4 must be ON, or

Both Q6 and Q8 must be ON

i.e. $A=B=0$, or $C=D=0$

For $Z=0$

Q1 or Q3 must be ON, and

Q5 or Q7 must be ON

i.e. $A=1$ or $B=1$, and $C=1$ or $D=1$

Which circuit does it implement?

(A) $Z = (A+B)' (C+D)'$

(B) $Z = (A'+B') (C'+D')$

(C) $Z = (AB + CD)'$

(D) $Z = [(A+B) (C+D)]'$


 


Fig. 3-22 Wakerly

**When A=B=0,
Q2 and Q4 ON,
Q1 and Q3 OFF
Z=1**

 **Similarly when C=D=0,
Q6 and Q8 ON,
Q5 and Q7 OFF
Z=1**



$$Z = [(A+B) (C+D)]'$$