


15-250X Faster than Software Implementation

Contact Information

Anupam Chattopadhyay

Email: anupam@ntu.edu.sg

Office: N4-02c-105

 

Attoseconds

Plan for the 2nd half of the semester

■ Full-Time Course

Week	Pre-Recorded Lectures	Monday (LT19A) 830-920	Thursday (Zoom) 1630-1720	Tutorial	Lab
7	L13-L14				
Recess Week					
8	L15-L16	L13-L14 Summary	Online Consultation (Zoom)	Tutorial 6	+ quiz 3
9	L17-L18	L15-L16 Summary		Tutorial 7	Experiment 4 + quiz 4
10	L19-L20	L17-L18 Summary		Tutorial 8	
11	L21-L22	L19-L20 Summary (Zoom)		Tutorial 9	Experiment 5 + quiz 5
12	L23	L21-L22 Summary		Tutorial 10	
13		Public holiday			

Plan for the 2nd half of the semester (*contd.*)

■ Part-Time Course

Week	Pre-Recorded Lectures	Tuesday (LT11) 1830-2130		Lab
7	L13-L14			
Recess Week				
8	L15-L16	L13-L14 Summary	Tutorial 6	
9	L17-L18	L15-L16 Summary	Tutorial 7, 8	
10	L19-L20	L17-L19 Summary	Tutorial 9	
11	L21-L22			Experiment 4 + quiz 4
12	L23	L20-L22 Summary	Tutorial 10	
13				Experiment 5 + quiz 5

Plan for the 2nd half of the semester (*contd.*)



- Online Tasks for L13 to L22
 - Will not be graded

- Discussion lectures (Monday, 8:30-9:20 AM, LT19A)
 - You are required to view the pre-recorded lectures
 - Recap and discussion (slides to be uploaded afterwards)
 - Additional examples and exercises
 - Polls through **Wooclap** (QR code in respective slides)

Plan for the 2nd half of the semester (contd.)

■ Participation in Course

- Use NTULearn Discussion Forum to ask follow-up questions

Discussion Board

Discussions are a good way to encourage students to think critically about your coursework and interact with each others' ideas. You can create discussions around indi

Create Forum Remove Sorting

FORUM	DESCRIPTION	TOTAL POSTS	UNREAD POSTS
<input type="checkbox"/> Q&A Lecture 21-22		0	0
<input type="checkbox"/> Q&A Lecture 19-20		0	0
<input type="checkbox"/> Q&A Lecture 17-18		0	0
<input type="checkbox"/> Q&A Lecture 15-16		0	0
<input type="checkbox"/> Q&A Lecture 13-14		0	0

■ Consultation Slots on (Thursday, 4:30-5:20 PM, Zoom)

- Limit yourself to 3 questions
- Avoid the clarification on tutorial
- <https://ntu-sg.zoom.us/j/81954891824>
Meeting ID: 819 5489 1824
Passcode: 364003



SC1005

Digital Logic

Recap and Discussion

Lecture 17

Sequential Circuits


Summary of Lecture 17

- Sequential Circuits
 - Set-Reset (SR) Latch
 - Transparent D-Latch
 - Clock and Timing


Recap: Combinational vs. Sequential Circuits

- The output of a combinational circuit is purely a function of the present inputs to it

- $output = f(input)$

 

- The output of a sequential circuit depends on both the *current* and *previous* inputs.

 

Exercise 1

- Consider two styles of fan speed control:
 - Dial-based (0,1,2,3,4,5)
 - Button-based (+,-)
- Which of the following correctly define the type of circuit used for implementing the fan control for L and R?



L – Combinational
R – Combinational

L – Combinational
R – Sequential

L – Sequential
R – Combinational

L – Sequential
R – Sequential



1

Go to [wooclap.com](https://www.wooclap.com)


2

Enter the event code in the top banner

Event code
CAOAZX


Recap: Latches

Set-Reset (SR) Latch

 


S	R	Q+	Function
0	0	Q	Store
0	1	0	Reset
1	0	1	Set
1	1	?	Undefined

Enabled SR Latch

 

E	S	R	Q+	Function
0	X	X	Q	Store
1	0	0	Q	Store
1	0	1	0	Reset
1	1	0	1	Set
1	1	1	?	Undefined

D Latch

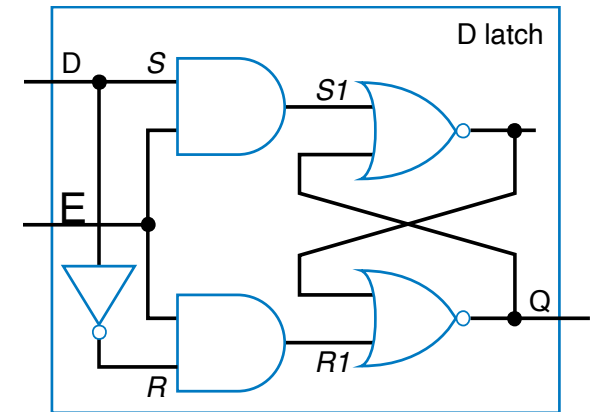


E	D	Q+
0	X	Q
1	0	0
1	1	1


Problem: When both S and R are asserted and then de-asserted at the same time, we may get output oscillation.

Recap: Transparent D Latch


Active-High D Latch

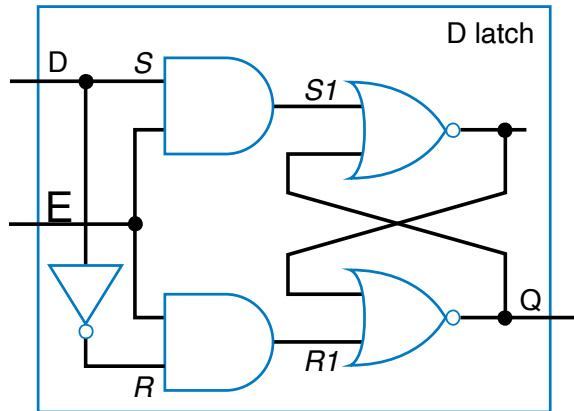


E	D	Q+	Function
0	X	Q	Store
1	0	0	Transparent
1	1	1	Transparent

 

Active-Low D Latch

 


E	D	Q+	Function
1	X	Q	Store
0	0	0	Transparent
0	1	1	Transparent

 

The Clock

 
- In digital systems, sequential components are connected to what we call a “clock”
- The clock is a signal that continuously toggles between 0 and 1 at a fixed rate:



- The **period** of the clock is the time it takes to complete **one complete cycle** – we call this a cycle
- The **frequency** is the inverse of the period:
 - 10ns period = $10 \times 10^{-9} \text{s}$, $1/10 \times 10^{-9} = 10^8 \text{Hz} = 100 \text{MHz}$
 - 1ns period = $1 \times 10^{-9} \text{s}$, $1/1 \times 10^{-9} = 10^9 \text{Hz} = 1 \text{GHz}$

Timing in Circuits

 - Assume an **and** gate has a delay of 4ns and an **inverter** has a delay of 2ns:



- The propagation delay, t_p , may differ between different inputs and outputs in the same circuit
- If we report a single number, we always use the worst (i.e. longest path)

SC1005

Digital Logic

Recap and Discussion

Lecture 18


Sequential Circuits

Summary of Lecture 18

- Introduction to Verilog HDL
 - Gated/Enabled S-R Latch
 - Transparent D-Latch
 - Edge-Triggered Flip-Flop

Timing of Latches

- Consider a chain of latches:



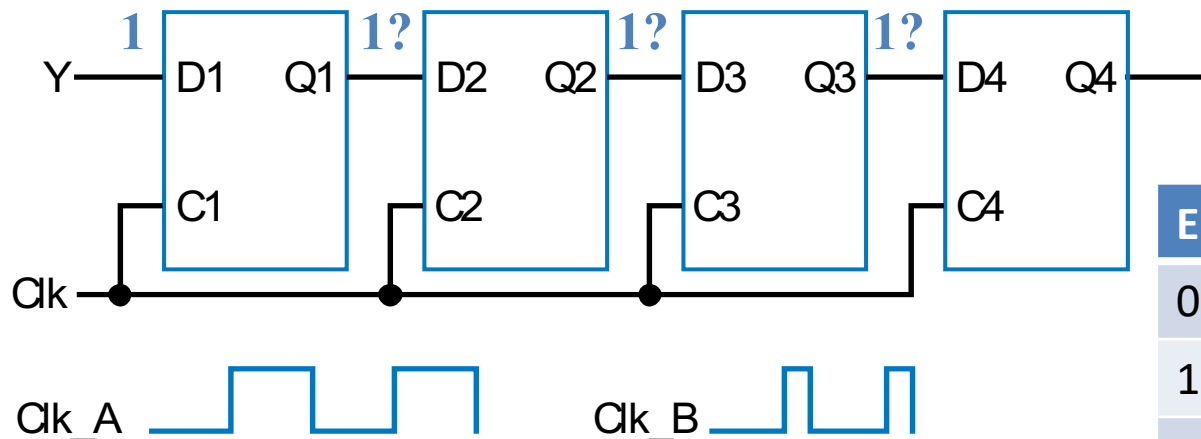


Truth table of a D Latch

E	D	Q+	Function
0	X	Q	Store
1	0	0	Transparent
1	1	1	Transparent



- When Clk_A is 1, how many latches will the input pass through?
- With Clk_A, it may be more, Clk_B, fewer

Timing of Latches

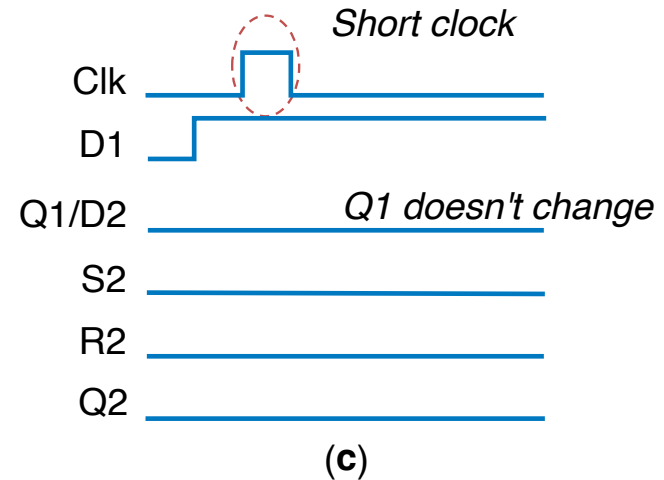 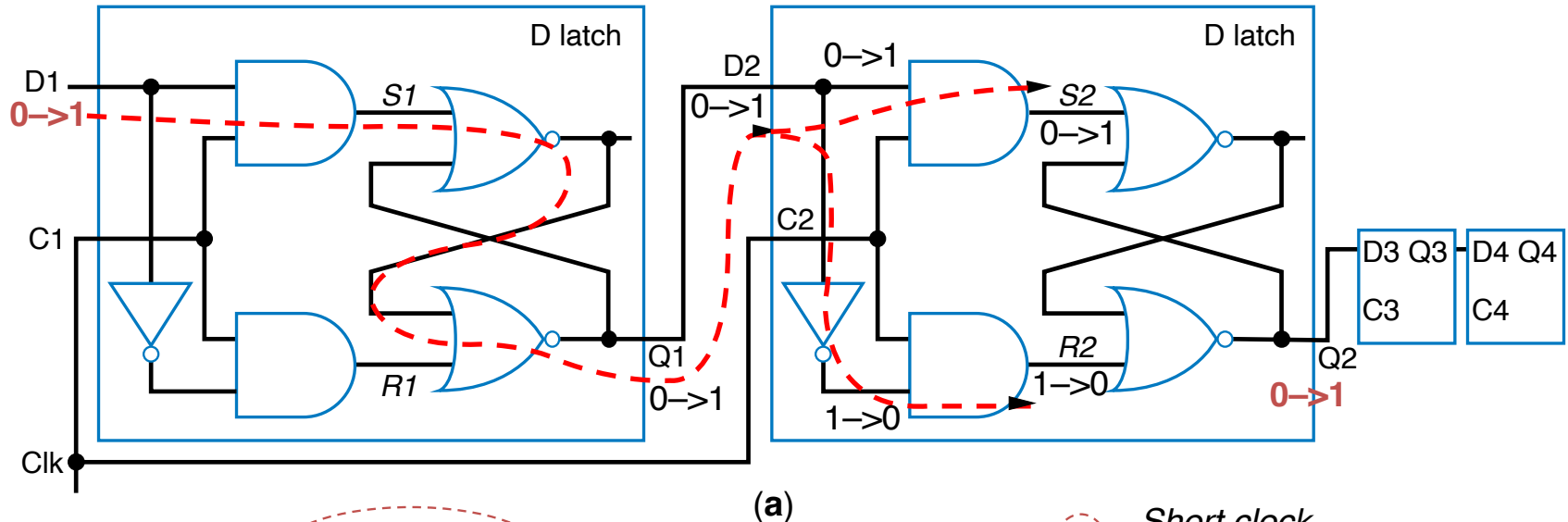


Recap: Edge Triggered Flip-Flops

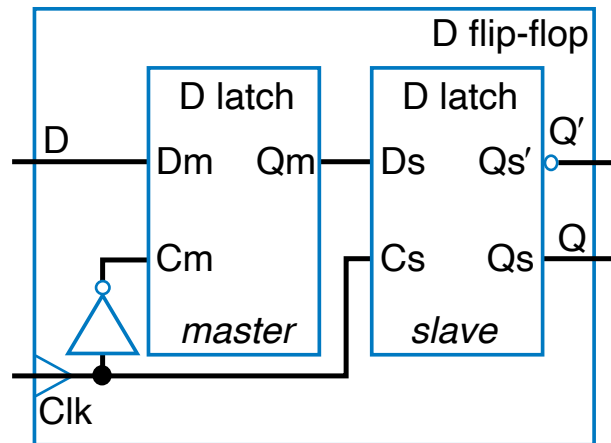 - Use edge triggered flip-flop to overcome the limitation of latches



Truth table of a D Latch


E	D	Q+	Function
0	X	Q	Store
1	0	0	Transparent
1	1	1	Transparent

 

- Master-Slave implies two latch stages:
 - Master stage is enabled when control is low, and samples the current input, while slave is disabled, locking it in the middle
 - When control goes high, the master is disabled, and the slave uses the value from the middle to determine its output
- Hence, the **only time an output will change is at the rising edge**
 - *For a negative-edge triggered setup, the master responds to high enable, and the slave to low enable*


Edge-Triggered Flip-Flops

 - The timing diagram for for a D-type flip-flop is as follows:



- Note transitions on the output only occur at the (rising) clock edge

Exercise 2

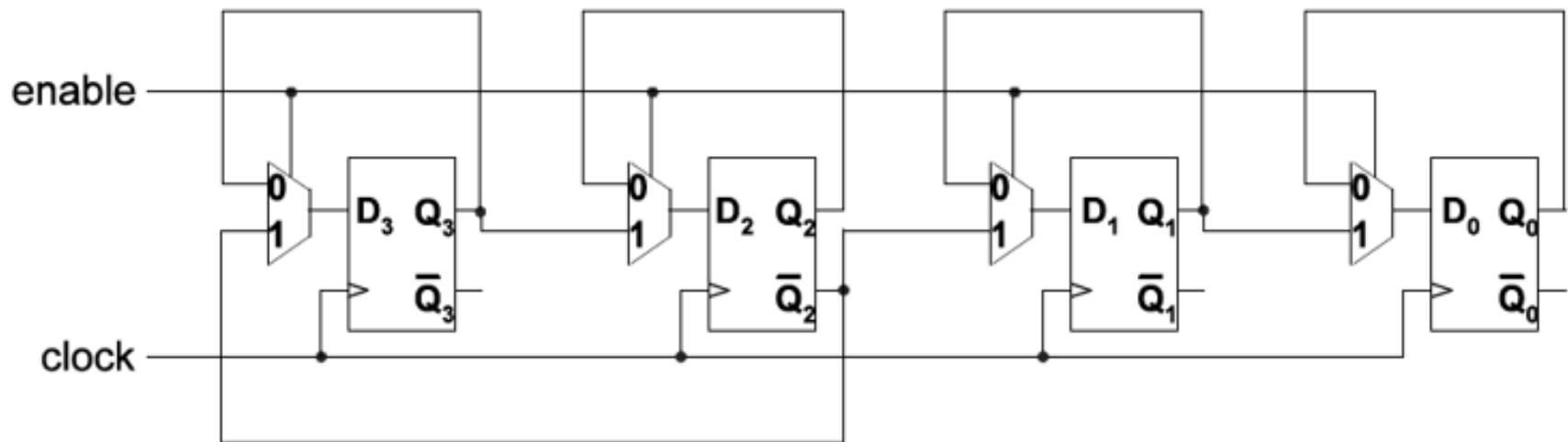

If $enable = 1$ and the current state of the circuit is $Q_3Q_2Q_1Q_0 = 0101$, what is the next state?

1111
1010
1100
0011
0000






- 1 Go to [wooclap.com](https://www.wooclap.com)
- 2 Enter the event code in the top banner

Event code
CAOAZX




Edge-Triggered Flip-Flops

- We've seen the D flip-flop:
 - Q takes the value on D at the rising edge of C
- There's also a J-K flip-flop:
 - Q becomes 1 if J is asserted at the rising edge and 0 if K is asserted
 - If both J and K are asserted, the output toggles at the rising edge
- And a T flip-flop:
 - Q toggles at the rising edge if T=1
- (Also a lesser seen SR flip-flop)

   

Exercise 3

 

1

Go to wooclap.com

2

Enter the event code in the top banner

Event code

CAOAZX

Initially both Q_0 and Q_1 are set to 1 (before the first clock cycle). The outputs

3rd clock cycle, $Q_1Q_0 = 11$; 4th clock cycle, $Q_1Q_0 = 00$;



3rd clock cycle, $Q_1Q_0 = 11$; 4th clock cycle, $Q_1Q_0 = 01$;

3rd clock cycle, $Q_1Q_0 = 00$; 4th clock cycle, $Q_1Q_0 = 11$;



3rd clock cycle, $Q_1Q_0 = 01$; 4th clock cycle, $Q_1Q_0 = 01$;

Registers

  - **Flip-flop** is a circuit that changes outputs only at the control signal's edges; **positive edge-triggered** or **negative edge-triggered**
- The D-type flip-flop is the fundamental building block in synchronous design
- But we often deal with multi-bit signals
- When we combine multiple D flip-flops together to store multiple bits, we call this a **register**:



Shift Register

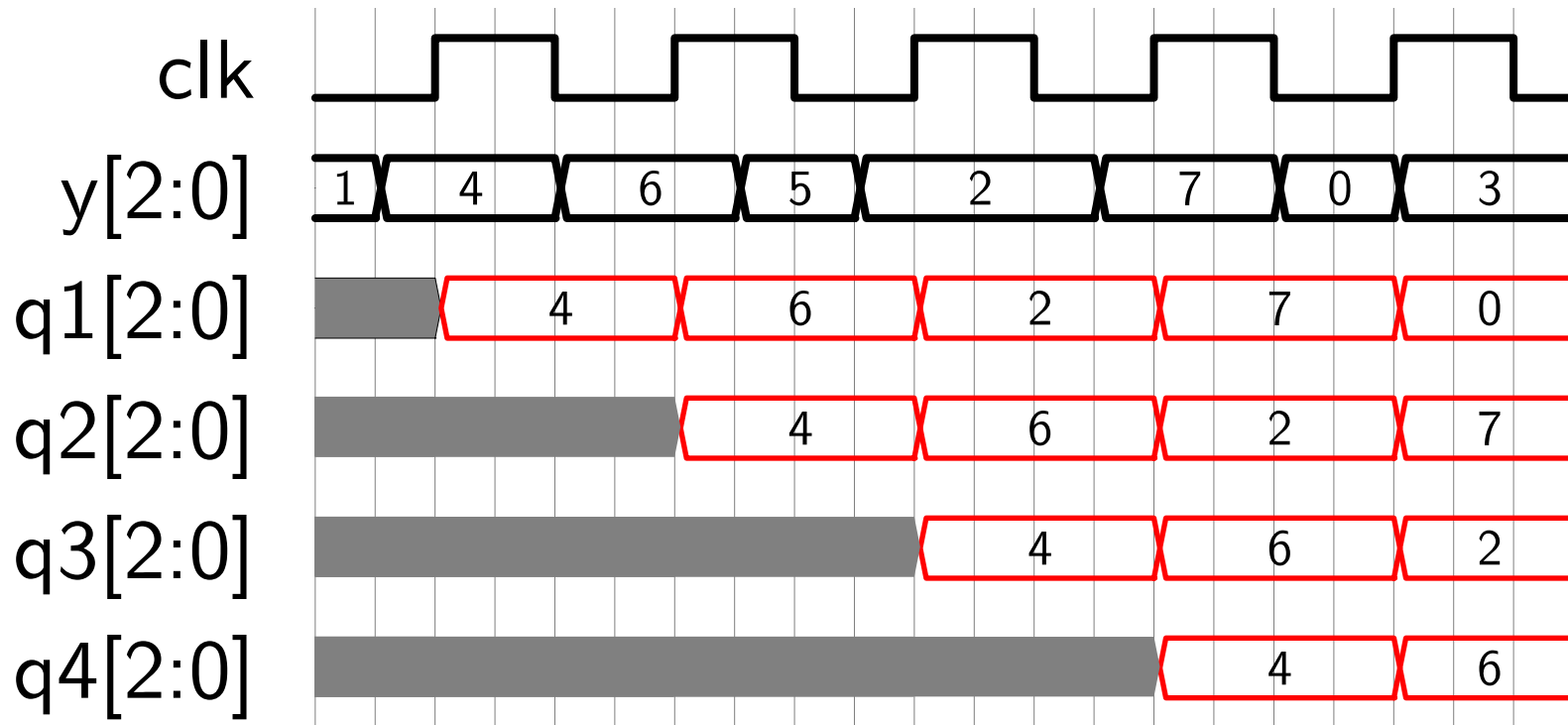 

END OF L17,L18 SUMMARY