

Contact Information



Anupam Chattopadhyay

Email: anupam@ntu.edu.sg

Office: N4-02c-105

Plan for the 2nd half of the semester

■ Full-Time Course

Week	Pre-Recorded Lectures	Monday (LT19A) 830-920	Thursday (Zoom) 1630-1720	Tutorial	Lab
7	L13-L14				
Recess Week					
8	L15-L16	L13-L14 Summary	Online Consultation (Zoom)	Tutorial 6	+ quiz 3
9	L17-L18	L15-L16 Summary		Tutorial 7	Experiment 4 + quiz 4
10	L19-L20	L17-L18 Summary		Tutorial 8	
11	L21-L22	L19-L20 Summary (Zoom)		Tutorial 9	Experiment 5 + quiz 5
12	L23	L21-L22 Summary		Tutorial 10	
13		Public holiday			

Plan for the 2nd half of the semester (*contd.*)



■ Part-Time Course

Week	Pre-Recorded Lectures	Tuesday (LT11) 1830-2130		Lab
7	L13-L14			
Recess Week				
8	L15-L16	L13-L14 Summary	Tutorial 6	
9	L17-L18	L15-L16 Summary	Tutorial 7, 8	
10	L19-L20	L17-L19 Summary	Tutorial 9	
11	L21-L22			Experiment 4 + quiz 4
12	L23	L20-L22 Summary	Tutorial 10	
13				Experiment 5 + quiz 5

Plan for the 2nd half of the semester *(contd.)*



- Online Tasks for L13 to L22
 - Will not be graded


- Discussion lectures (Monday, 8:30-9:30 AM, LT19A)
 - You are required to view the pre-recorded lectures
 - Recap and discussion (slides to be uploaded afterwards)
 - Additional examples and exercises
 - Polls through **Wooclap** (QR code in respective slides)

Plan for the 2nd half of the semester (contd.)



■ Participation in Course

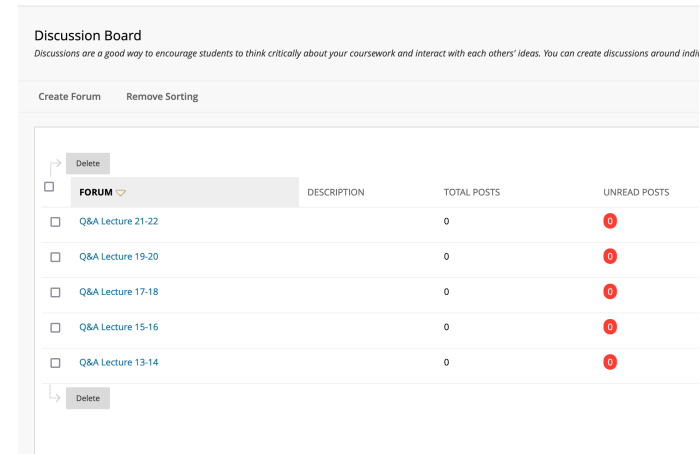- Use NTULearn Discussion Forum to ask follow-up questions



■ Consultation Slots on (Thursday, 4:30-5:20 PM, Zoom)

- Limit yourself to 3 questions
- Avoid the clarification on tutorial
- <https://ntu-sg.zoom.us/j/81954891824>
Meeting ID: 819 5489 1824
Passcode: 364003



SC1005

Digital Logic


Recap and Discussion

Lecture 13

Combinational Circuits

Summary of Lecture 13


 
- Combinational circuits are functions:
 - *Outputs depend solely on the **present combination** of input values*




- Combinational Circuits
 - Seven-Segment Decoder
 - Decoder (One-Hot)
 - Multiplexers
- Timing Diagrams

Combinational Circuits

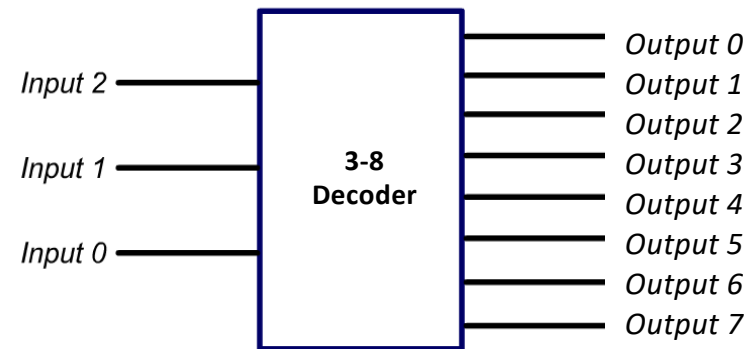 
- Examples:
 - Seven-Segment Decoder
 - Decoder (One-hot)
 - Multiplexer




1-bit 2x1 mux

 

1-bit 4x1 mux

 

8-bit 4x1 mux

 


DECODER

Decoder

- Decoders are an important basic circuit, similar to the 7-Segment Decoder
- Take a binary input number, and output a corresponding one-hot output
 - Only one bit of the output is high, its position corresponds to the input value
 - Output width is always 2 to the power of input width
 - N -input Decoder: 2^N outputs


Input	Output
00 →	0001
01 →	0010
10 →	0100
11 →	1000

 

 
Example: A two-input decoder will have four outputs (2-4 Decoder)

Decoder

- In general, decoders can be referred to n-m decoders



Input		Output			
1	0	D0	D1	D2	D3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

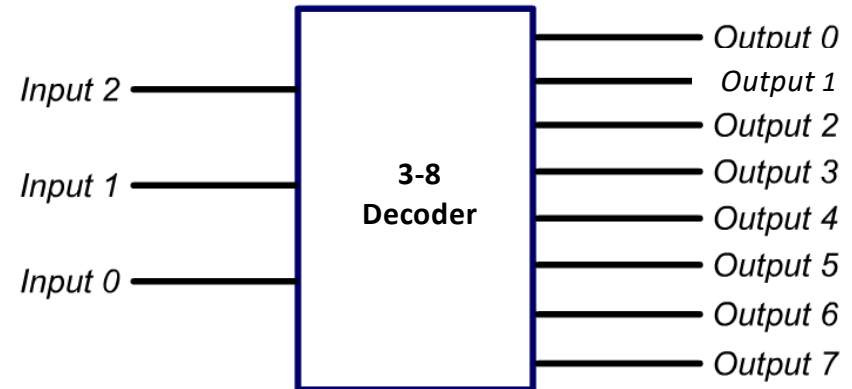

Input			Output							
2	1	0	D0	D1	D2	D3	D4	D5	D6	D7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Source: <https://filebox.ece.vt.edu/~jgtront/introcomp/decoder.swf>

Decoder: Example


■ Step 1: Capture function

- $d0 = a'b'c'e = 0001$
- $d1 = a'b'ce = 0011$
- $d2 = a'bc'e = 0101$
- $d3 = a'bce = 0111$
- $d4 = ab'c'e = 1001$
- $d5 = ab'ce = 1011$
- $d6 = abc'e = 1101$
- $d7 = abce = 1111$

■ Step 2: Implement Circuit


- Each term is a 4-input AND gate

This is a 3-8 Decoder.

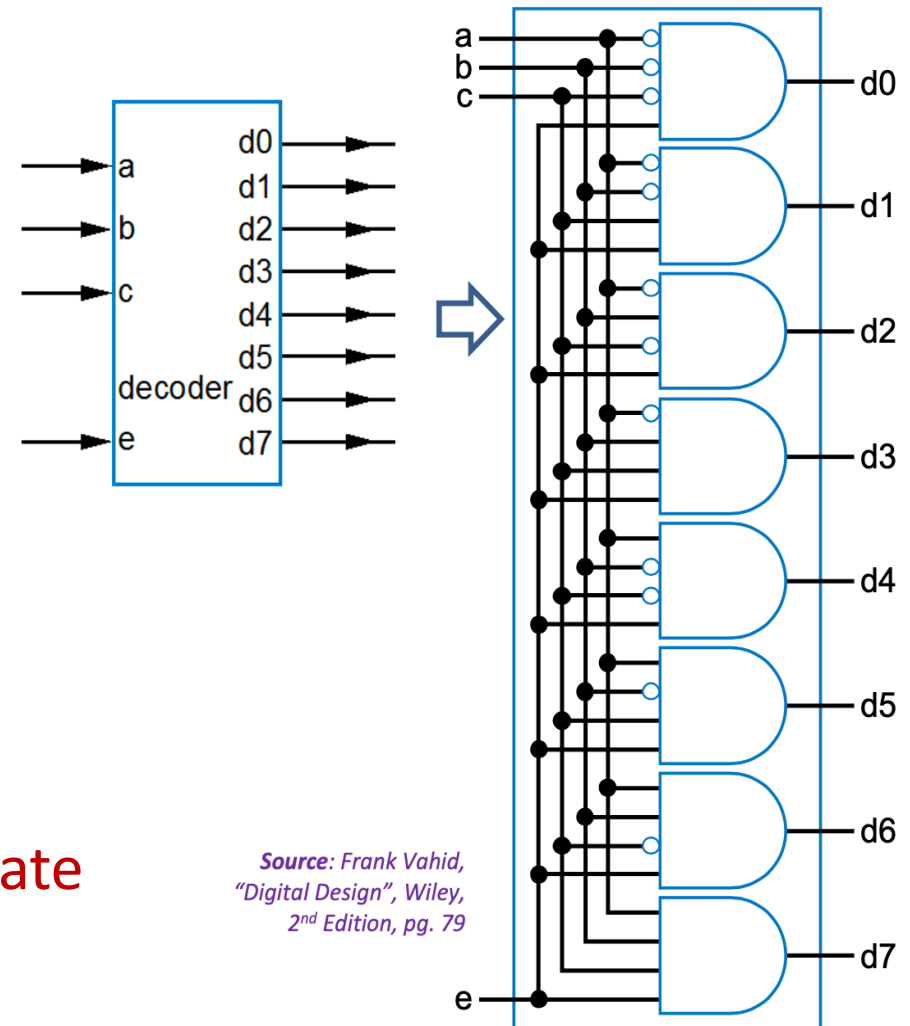

Exercise 1

- What is the Boolean expression of Q?

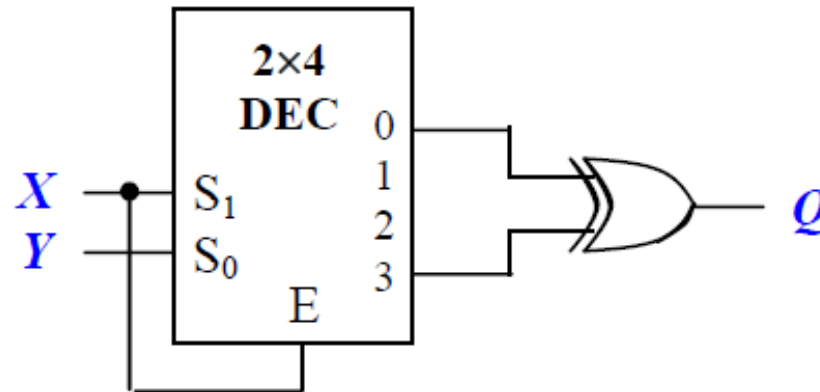

A. 1

B. X

✓ C. $X.Y$

D. $X' + Y'$

E. $X'Y + X.Y'$

$$\begin{aligned} Q &= X'Y'E \oplus XYE \\ &= X'Y'X \oplus XYX \quad (\text{since } X = E) \\ &= XY \end{aligned}$$



1

Go to wooclap.com

2


Enter the event code in the top banner

Event code
ZLXOFA

MULTIPLEXER


Multiplexer (Mux)

 - Consists of multiple inputs, and a single output
- A select input determines which input should be connected to the output
- 2-input MUX needs
 - 1-bit select input
- N -input MUX needs
 - $\log_2(N)$ bit select inputs




Source: Frank Vahid, "Digital Design", Wiley, 2nd Edition, pg. 87


1-bit 2x1 mux

 

1-bit 4x1 mux

 


8-bit 4x1 mux

 

 Exercise 2

- Find the SOP expression for function $T(A,B,C)$



A, B are the select signals of the 4x1 multiplexer.

$T = C$ when $AB = 00 \rightarrow A'B'C$

$T = C'$ when $AB = 10 \rightarrow AB'C'$



- ✓ A. $A'B'C + A.B'C'$
- B. $A'B'C' + A.B'C'$
- C. $A'B'C + A.B'C$
- D. $A'B'C' + A.B'C$
- E. None of the above



1 Go to wooclap.com

2 Enter the event code in the top banner

Event code
ZLXOFA

Exercise 3

- An $N \times 1$ multiplexer has N inputs

TRUE

✓ FALSE

N -input MUX needs $\log_2(N)$ bit select inputs
Hence, total $[N + \log_2(N)]$ inputs



1

Go to wooclap.com

2


Enter the event code in the top banner

Event code
ZLXOFA

TIMING DIAGRAMS


Timing Diagrams

- Timing diagrams show the behavior of a circuit with **progression of time**
- Input values are changed and the resultant outputs shown
- Consider an **AND** gate:
- A timing diagram can show any combination or order of input values
- The output at any point is calculated by looking at the input values at that instance

 

 Exercise 4

- The following waveform for inputs A, B and output X depicts



- ✓ A. 2-input AND gate
- B. 2-input OR gate
- C. 2-input XOR gate
- D. None of the above



1

Go to wooclap.com

2

Enter the event code in the top banner

Event code
ZLXOFA




Combinational Circuits

DESIGNING A DIGITAL CLOCK DISPLAY

Digital Clock Display

- Four seven segment displays
- One seven segment decoder
- One 4-bit 4x1 Multiplexer
- One 2-4 Decoder

 

SC1005

Digital Logic

Recap and Discussion

Lecture 14

Introduction to Verilog

Summary of Lecture 14

- Introduction to Verilog HDL
 - Module Declaration
 - Instantiating Gate-Level Primitives
 - Module Instantiation

Hardware Description Languages (HDLs)

- HDLs are **programming-like** languages that are used to describe hardware
- HDLs are synthesized (and optimized) to hardware primitives
- Sophisticated tools can then ensure the hardware generated from the description is efficient

```
void main()
{
    int i, nc;
    nc = 0;
    i = getchar();
    while (i != EOF) {
        nc = nc + 1;
        i = getchar();
    }
    printf("Chars = %d\n", nc);
}
```


Compiler

```
module counter (clk,
reset, enable, count);
    input clk, reset,
enable;
    output [3:0] count;
    reg [3:0] count;

    always @ (posedge clk)
    if (reset == 1'b1)
        count <= 0;
    else if (enable == 1'b1)
        count <= count + 1;

endmodule
```



Tools
(e.g. Logic
Synthesizer)

 

MODULES

Module

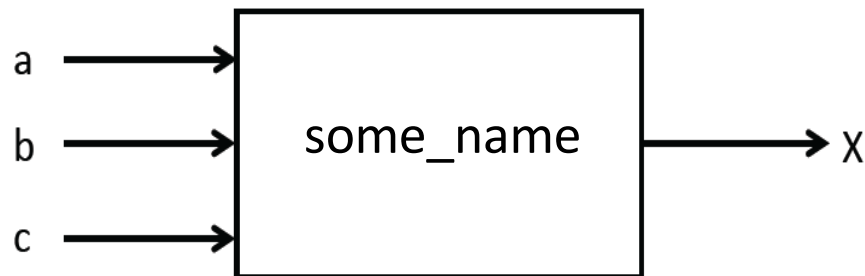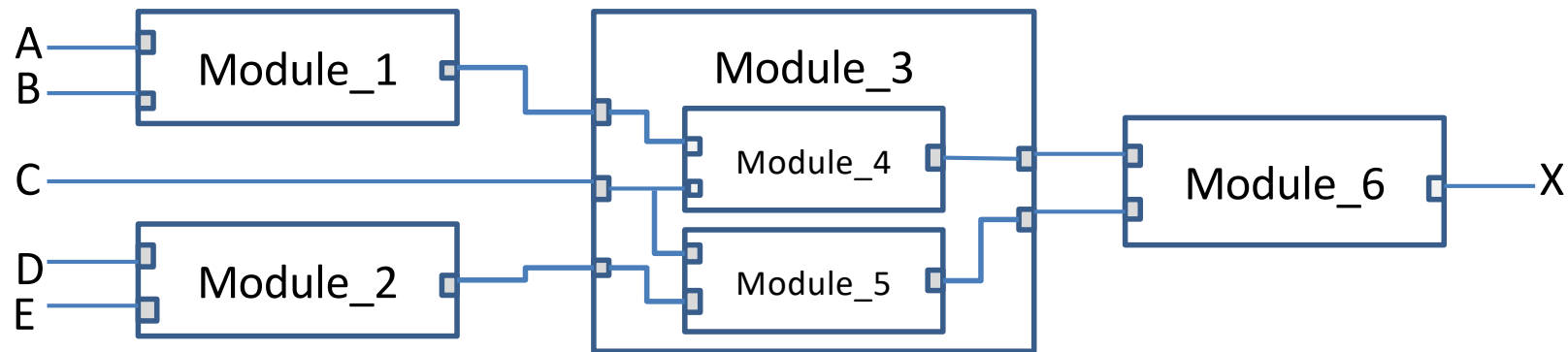- In Verilog, designs are broken down into **modules**
- At each level in the hierarchy, a module instance is treated as a “black-box” – the internals are unknown



```
module some_name (
    input a, b, c,
    output X);

    // Describe your circuit here


endmodule
```

INSTANTIATING GATE-LEVEL PRIMITIVES

Gate-Level Primitives


- Verilog provides us with basic **primitives** to model Boolean gates: **and**, **nand**, **or**, **nor**, **not**, **xor**, **xnor**

```
and (y, a, b);
```

 

- Represents an **and** gate with inputs connected to wires a and b, and output connected to wire y
- Gate primitives allow more than two inputs:


```
or (z, a, b, c, d);
```

 

- This represents an **or** gate with inputs a, b, and c, d and output z

 Exercise

- Implement a Verilog module using structural gate-level primitives for the following circuit:




```
module simple_circ (input A, B, C, D, output Y);
    wire int1, int2, int3, int4;

    and (Y, int1, int2);
    not (int1, int3);
    or (int3, A, D);
    and (int2, B, C, int4);
    not (int4, D);

endmodule
```

 Exercise

- Implement a Verilog module using structural gate-level primitives for the following circuit:



```
module simple_circ (input A, B, C, D,
                    output Y);
    wire int1, int2, int3, int4;

    and (Y, int1, int2);
    not (int1, int3);
    or (int3, A, D);
    and (int2, B, C, int4);
    not (int4, D);
endmodule
```

```
module simple_circ (input A, B, C, D,
                    output Y);
    wire int1, int2, int3, int4;



    not (int1, int3);
    not (int4, D);
    and (int2, B, C, int4);
    and (Y, int1, int2);
    or (int3, A, D);
endmodule
```

These two implementations will produce the same circuit

Exercise 5

- Which of the following is correct gate-level instantiation of a 2x1 multiplexer in Verilog:

1-bit 2x1 mux

  

```
module mux (input in0, in1, sel,
            output mxout);
    wire w1, w2, w3;

    or (muxout, w1, w2);
    and (w1, in0, w3);
    not (w3, sel);
    and (w2, in1, sel);
endmodule
```



- A. mux (mxout, in0, in1, sel);
- B. mux (in0, in1, sel, mxout);
- C. mux (mxout, sel, in0, in1);
- ✓ D. None of the above



1

Go to wooclap.com

2


Enter the event code in the top banner

Event code
ZLXOFA

MODULE INSTANTIATION


Module

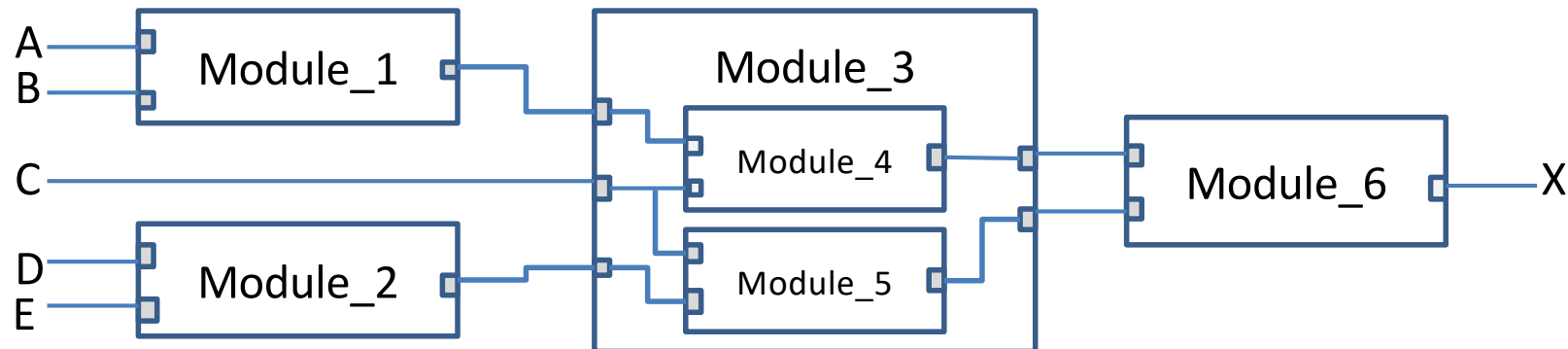- In Verilog, designs are broken down into *modules*
- Good designs consist of sufficient (but not excessive) *levels of hierarchy*, with modules containing instances of other modules
- At each level in the hierarchy, a module instance is treated as a “black-box” – the internals are unknown





Instantiation in Verilog

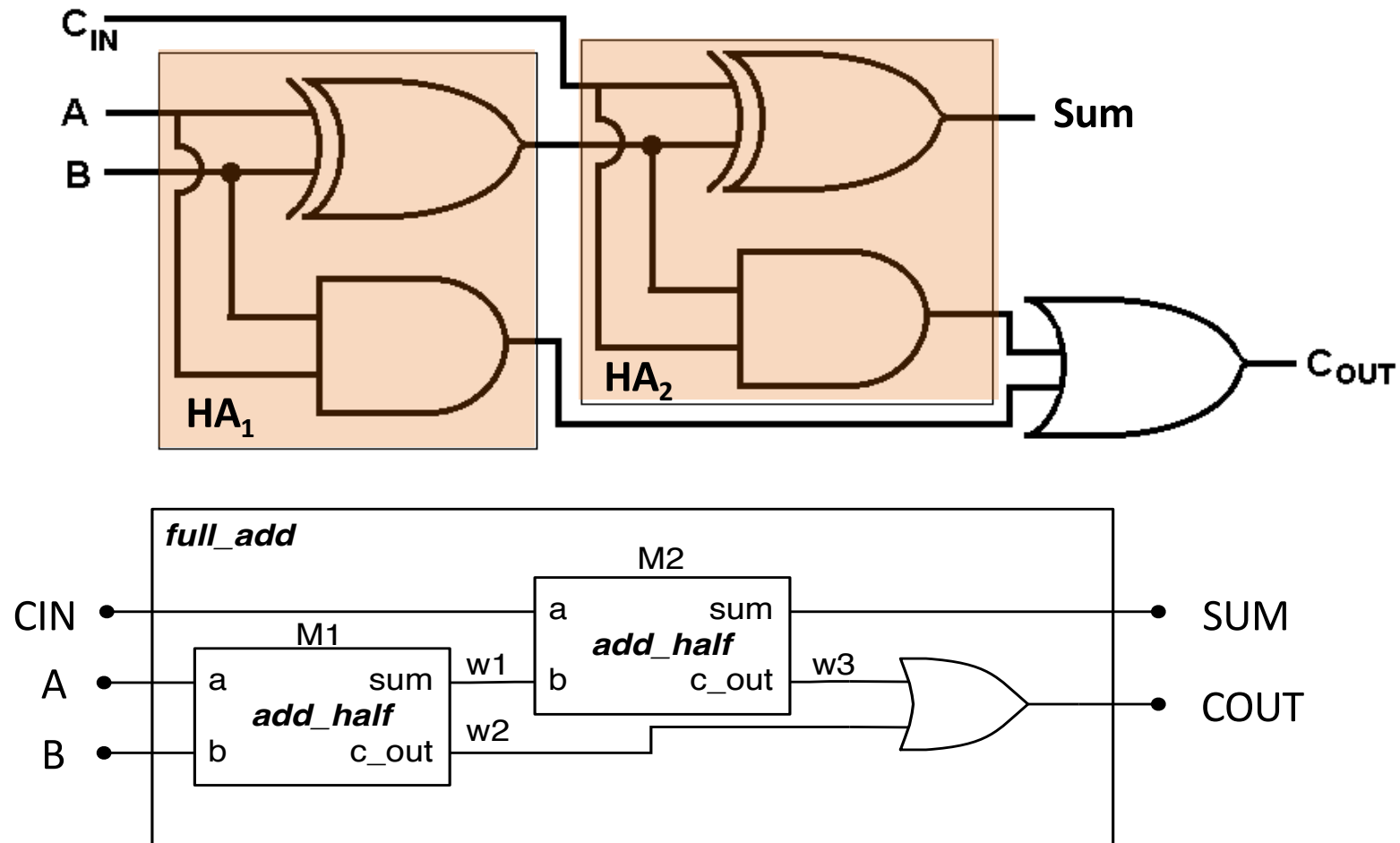- We can *instantiate* the half adder module twice to design a full adder



Instantiation in Verilog (Full Adder)
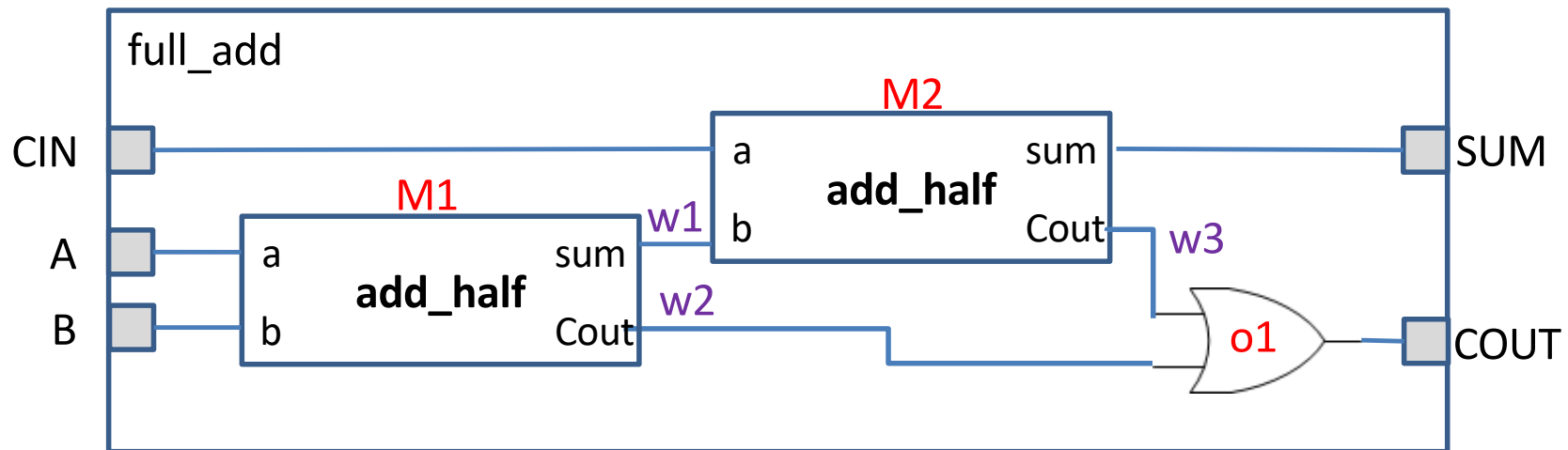 
```
module add_half (input a, b,  
                 output sum, Cout);  
  xor g1 (sum, a, b);  
  and g2 (Cout, a, b);  
endmodule
```




```
module full_add (input A, B, CIN,  
                output SUM, COUT);  
  wire w1, w2, w3;  
  
  add_half M1 (A, B, w1, w2);  
  add_half M2 (CIN, w1, SUM, w3);  
  or o1 (COUT, w3, w2);  
endmodule
```

Instantiation in Verilog

- We *instantiate* a module by invoking its name and giving an *instance* a name:



```
add_half M1 (A, B, w1, w2);
```

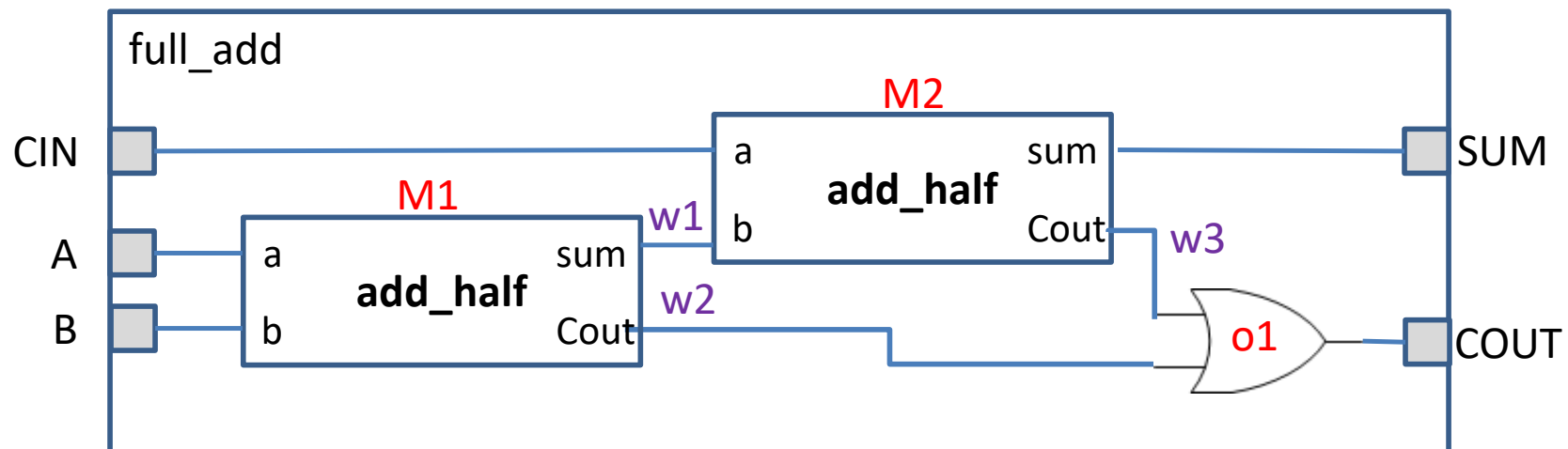- Creates an *instance* called **M1** of module **add_half**



Ordered Instantiation

- The **order** determines connections
- Looking at the original **add_half** module declaration:
- Its first port is its **a** input, the second its **b** input, the third its **sum** output and the fourth its **Cout** output
- Connects a wire called **A** in the outer module with the **a** port, **B** with the **b** port, the **w1** wire to its **sum** output and the **w2** wire to its **Cout** port

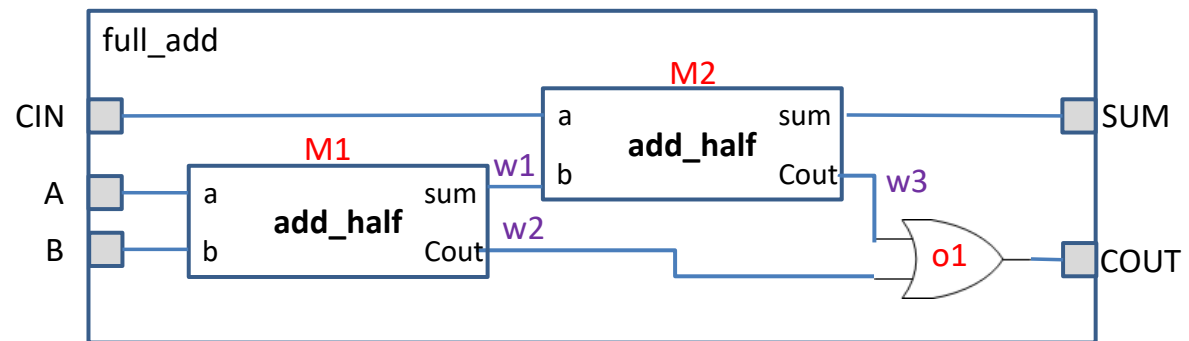 

```
module add_half (input a, b,
                 output sum, Cout);
    xor g1 (sum, a, b);
    and g2 (Cout, a, b);
endmodule
```

```
add_half M1 (A, B, w1, w2);
```

```
add_half M2 (CIN, w1, SUM, w3);
```


Named Instantiation

- Connecting instantiated modules to wires and ports in the manner just described can be **error-prone**:
- Hence, we generally use a ***named connection***:

```
add_half M1 (.a(A),
             .b(B),
             .sum(w1),
             .Cout(w2));
```

```
add_half M2 (.a(CIN),
             .b(w1),
             .sum(SUM),
             .Cout(w3));
```

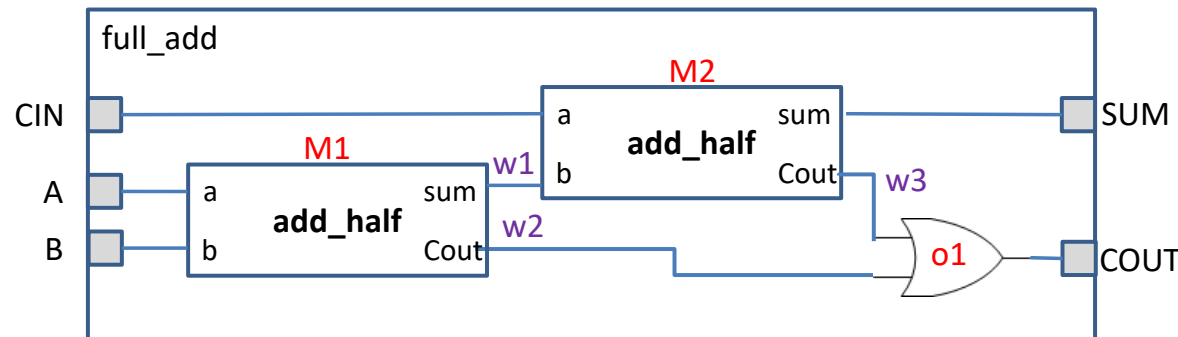The port name is preceded by a dot, and the connected signal is placed in the brackets



END OF L13,L14 SUMMARY