

# SC1005

## Digital Logic

Recap and Discussion

Lecture 19 and 20

Sequential Circuits in Verilog




# Summary of Lecture 19

- Sequential Circuits in Verilog
  - Registers in Verilog
  - Clock and Reset
  - Synchronous always block
  - Counters

# Summary of Lecture 20

- Sequential Circuits in Verilog
  - Shift Registers
  - Serial Data Transfer
  - Memory
  - What gets synthesized

# Recap: Registers in Verilog

   

```
module d_reg (input d, clk,  
              output reg q);
```

```
    always @ (posedge clk)  
        q <= d;
```

```
endmodule
```


Note the use of the non-blocking assignment. **e.g. <=**  
More on that later

```
module d_reg (input clk, input [7:0] d,  
              output reg [7:0] q);
```


```
    always @ (posedge clk)  
        q <= d;
```

```
endmodule
```

 
# Recap: Synchronous Reset vs. Asynchronous Reset



## Synchronous Reset

 

## Asynchronous Reset

 

```
module d_reg (input [7:0] d,
               input clk, rst,
               output reg [7:0] q);

always @ (posedge clk)
begin
    if (rst)          // same as (rst==1'b1)
        q <= 8'b0000_0000;
    else
        q <= d;
end

endmodule
```


```
module d_reg (input [7:0] d,
               input clk, rst,
               output reg [7:0] q);

always @ (posedge clk or posedge rst)
begin
    if (rst)
        q <= 8'b0000_0000;
    else
        q <= d;
end

endmodule
```


In FPGA Design we try to  
AVOID asynchronous reset.

# Recap

 

```
module multireg (input [7:0] a, b, c,  
                 input clk, rst,  
                 output reg [7:0] q, r, s);  
  
    always@(posedge clk)  
    begin  
        if(rst) begin  
            q <= 8'b0000_0000;  
            r <= 8'b0000_0000;  
            s <= 8'b0000_0000;  
        end else begin  
            q <= a;  
            r <= b;  
            s <= c;  
        end  
    end  
end  
endmodule
```

 - Each *assignment* in a synchronous always block results in a *register*
- All **synchronous always blocks** should use the same clock signal
- For **falling-edge triggered**, use `always@(negedge clk)`




# Recap: Assignments in Always Blocks

- For *combinational always blocks*, we *always* use a blocking assignment (**=**), and **order matters**
- For *synchronous always blocks*, we *always* use non-blocking assignments (**<=**), and **order does not matter**
 
## Combinational always block


```
reg x, y;  
  
always @ *  
begin  
    x = a & b;  
    y = x ^ c;  
end
```


 
## Synchronous always block

```
reg x, y;  
  
always@(posedge clk)  
begin  
    x <= a;  
    y <= x;  
end
```

Each non-blocking *assignment* in a synchronous always block results in a *register*



## Exercise 1

For the Verilog code shown, if Rst=0 and the current circuit state is  $ABC = 001$ , what is the next state?

- A. 111
- B. 001
- C. 100
- D. 010

```
module Ex1 (input Clk, Rst,
            output reg A, B, C);

    always@(posedge Clk)
    begin
        if (Rst) begin
            C <= 1'b1;
            B <= 1'b0;
            A <= 1'b0;
        end
        else begin
            C <= B;
            B <= A;
            A <= A ^ B ^ C;
        end
    end
endmodule
```

Ans: C. 100

A is shifted to B, B is shifted to C,  
and the new A is  $A \text{ XOR } B \text{ XOR } C = 1$ .

# Sequential Verilog

- While it is possible to describe general sequential blocks in Verilog, it is generally used to describe *synchronous* circuits, i.e. **edge-triggered components**
  - Counter
  - Shift Register
  - Serial to parallel converter
  - Parallel to serial converter
  - First-In-First-Out buffers
  - ...
- The Vivado Synthesis tool will generally convert designs to D-type flip-flops/registers



# Synchronous Counters: Binary Counters

- At each rising edge, we pass through the incremented value of the current count

0 0 0 ← Reset

0 0 1

0 1 0

0 1 1

1 0 0

1 0 1

1 1 0

1 1 1


0 0 0

0 0 1

⋮

```
module simplecnt (input clk, rst,
                  output reg [2:0] q);

 
    always @ (posedge clk)
    begin
        if (rst)
            q <= 3'b000;
        else
            q <= q + 1'b1;
    end
endmodule
```



 
# Synchronous Counters: Counter with load

```
module simplecnt (input clk, rst, load,
                  input [3:0] cnt_in,
                  output reg [3:0] q);

always @ (posedge clk)
begin
    if (rst)
        q <= 4'b0000;
    else
        if (load)
            q <= cnt_in;
        else
            q <= q + 1'b1;
end
endmodule
```




## Exercise 2

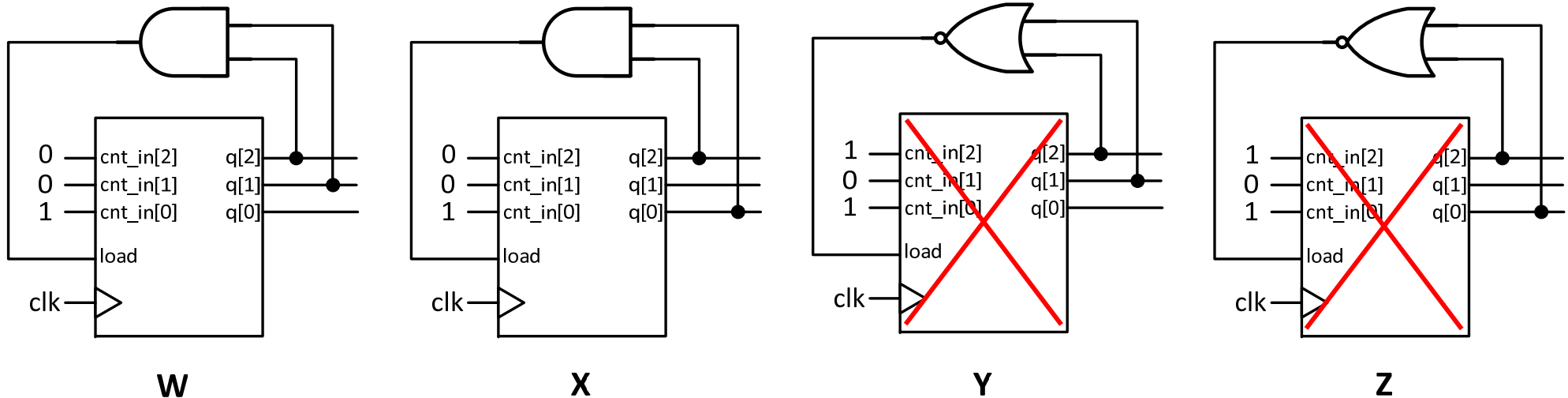

- Using an up-counter with load capabilities, which circuit will generate a counting sequence: 1, 2, 3, 4, 5, 6, 1, 2 ...?

You can assume that the initial state of the counter is  $001_2$ .

- A. W 
- B. X
- C. Y
- D. Z
- E. None of the above


Ans: Circuit W

A binary counter with initial state equal to 001 and with  $load = 0$ , will naturally count from 1 to 6.

At 6, the counter needs to roll over back to 1 so that the sequence will repeat. To achieve this we need to detect 6 and use it to load 1. Circuit W will do this by using  $q[2]=q[1]=1$  to generate the  $load$  signal which will load 001 back into the counter on the next  $clk$  edge.
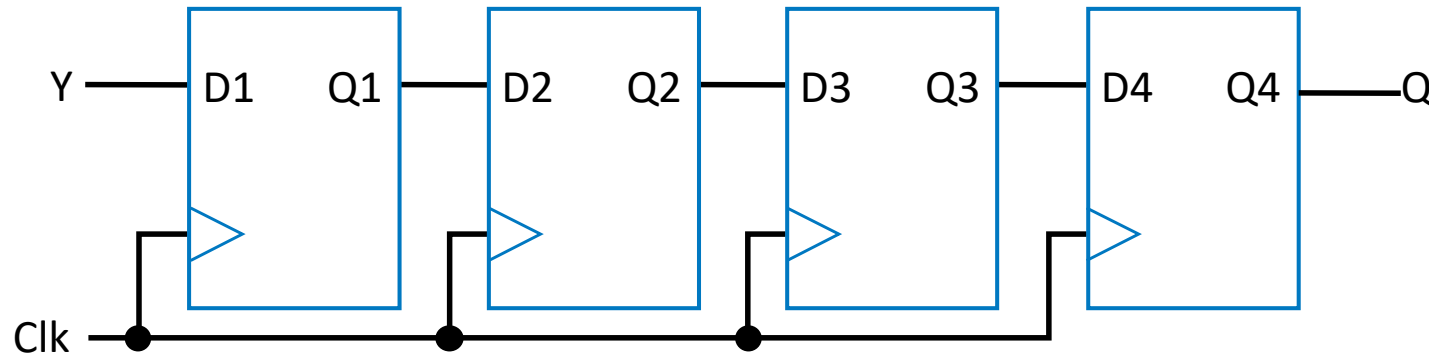
# Recap: Shift Registers in Verilog

- Shift registers pass a single input through a chain of flip-flops



```
module shiftreg (input clk, y,
                 output reg q);

    reg q1, q2, q3;

    always@(posedge clk)
    begin
        q1 <= y;
        q2 <= q1;
        q3 <= q2;
        q  <= q3;
    end

endmodule
```

**Order does not matter**

```
module shiftreg (input clk, y,
                 output reg q_out);


    reg [3:1] q;

    always@(posedge clk)
    begin
        q[1]    <= y;
        q[3:2] <= q[2:1];
        q_out   <= q[3];
    end

endmodule
```
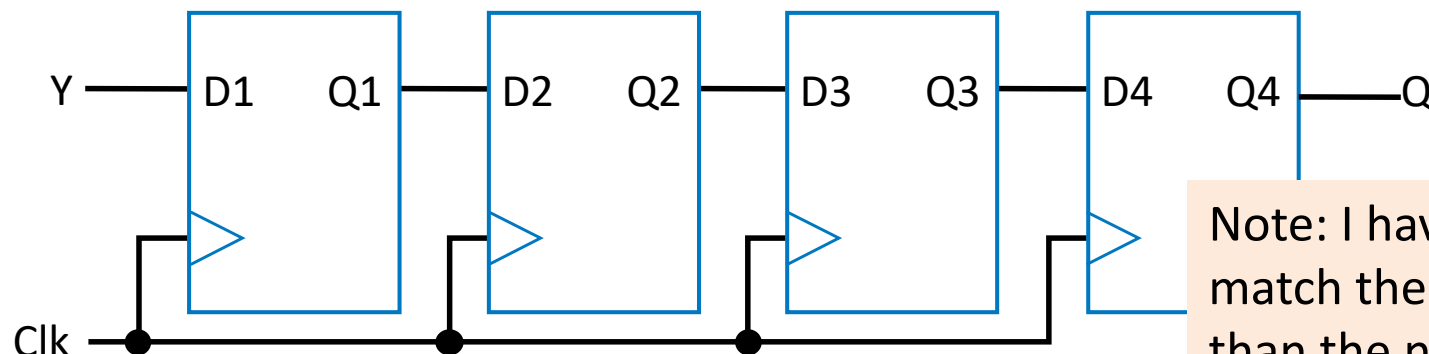
# Recap: Shift Registers in Verilog

- Shift registers pass a single input through a chain of flip-flops



Note: I have defined **q** to match the diagram, rather than the normal [3:0] q;.

```
module shiftreg (input clk, y,
                 output reg q);

    reg q1, q2, q3;

    always@(posedge clk)
    begin
        q1 <= y;
        q2 <= q1;
        q3 <= q2;
        q  <= q3;
    end

endmodule
```

Order does  
not matter

```
module shiftreg (input clk, y,
                 output q_out);

    reg [4:1] q;

    assign q_out = q[4];



    always @ (posedge clk)
    begin
        q[4:1] <= {q[3:1], y};
    end

endmodule
```



An even better way

# Shift Registers (Analogy)



## Serial-In Serial-Out

  

## Parallel-In Serial-Out

  

## Serial-In Parallel-Out

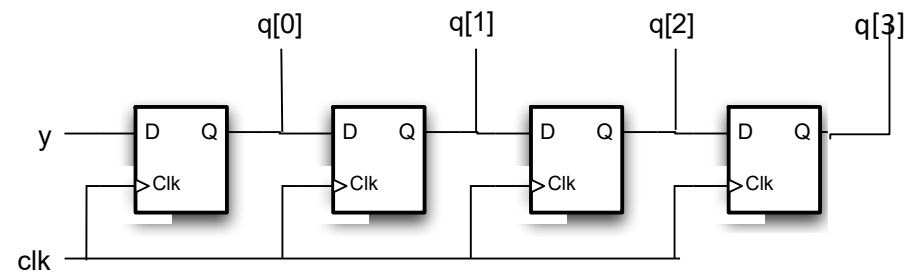 

**Source:** <http://www.allaboutcircuits.com/worksheets/shift-registers/>

# Shift Registers (Parallel-In Serial-Out)



- Whenever *ld* is high, the shift register is loaded with the value on *y*
- Can also be used as a conventional shift register when *ld* is always low.

```
module shiftreg ( input clk, ld,
                  input [3:0] y,
                  output q_out);

    reg [3:0] q;

    always @ (posedge clk)
    begin
        if (ld)
            q <= y;
        else
            q[3:0] <= {q[2:0], y[0]};
    end
    assign q_out = q[3];



endmodule
```

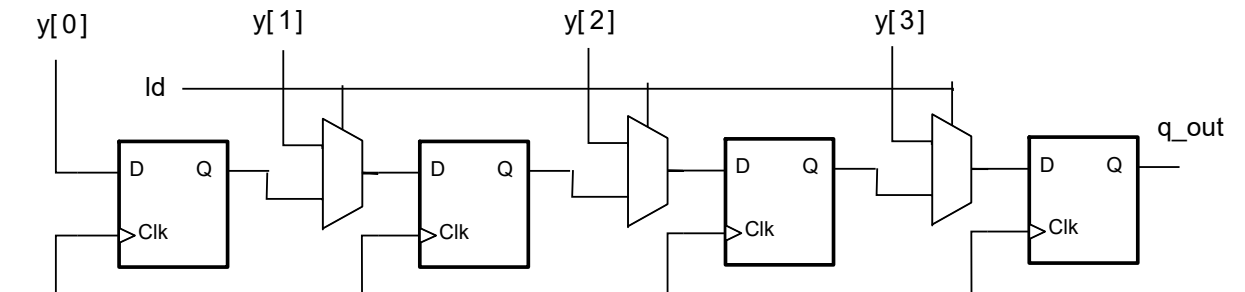 
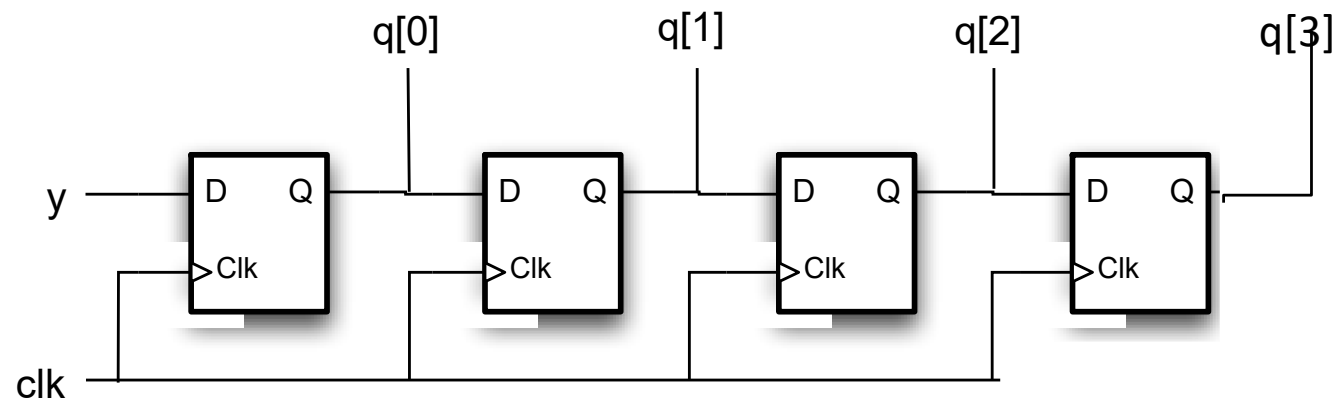 
# Shift Registers (Serial-In Parallel-Out)




- We can also access the outputs of the flip flop all at once

```
module shiftreg ( input clk, y,  
                  output reg [3:0] q);  
  
    always@(posedge clk)  
    begin  
        q[3:0] <= {q[2:0], y};  
    end  
  
endmodule
```





# Serial Data Transfer

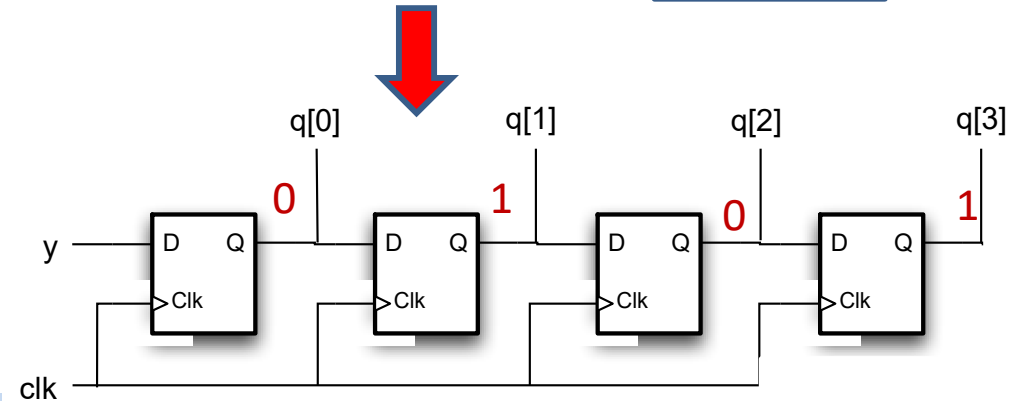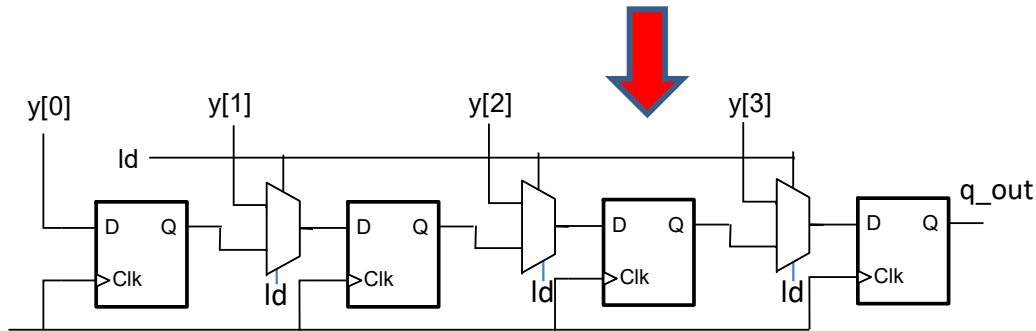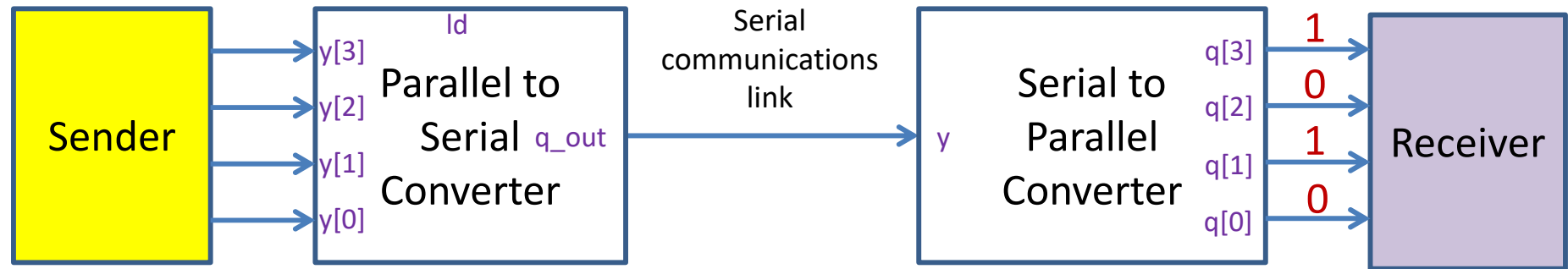

```
module piso4 (input clk, ld, input [3:0] y,
              output q_out);
    reg [3:0] q;

    always@(posedge clk)
    begin
        if (ld)
            q <= y;
        else
            q[3:0] <= {q[2:0], y[0]};
        end
        assign q_out = q[3];
    endmodule
```


```
module sipo4 (input clk, y,
              output reg [3:0] q);

    always@(posedge clk)
    begin
        q[3:0] <= {q[2:0], y};
    end

endmodule
```
 
# Memory

- Memory is an array of registers
  - Can access a single word
    - Need an *Address* signal
  - Can read from and write to
    - Need *Data in, Data out & Write enable*
    - May have other control signals



- Memories are defined as an array of type *reg*.

**An 8-bit x 1024 memory array**

```
reg [7:0] mem_array [0:1023];
```

**A 32-bit x 8K memory array**

```
reg [31:0] mem_array [0:8191];
```

- A simple 8-bit x 1024 single port RAM module in Verilog

```
module dmem #(parameter WORD_SIZE = 8, ADD_SIZE = 10) (input clk, we,  
    input [WORD_SIZE-1:0] din, input [ADD_SIZE-1:0] add,  
    output [WORD_SIZE-1:0] dout);
```

```
    reg [WORD_SIZE-1:0] RAM [0:(1<<ADD_SIZE)-1];    // Define mem array
```

```
    assign dout = RAM[add];                          // Combinational read
```

```
    always @ (posedge clk)
```

```
        if (we) RAM[add] <= din;                    // Synchronous write
```


```
endmodule
```

What does  $1 \ll \text{ADD\_SIZE}$  produce?

Ans:  $1 \ll 10 = 100\_0000\_0000 = 1024$
 
# What Gets Synthesized?


- Important to understand what is synthesized from a synchronous always block
- Each (non-blocking) assignment results in a register, with its input connected to a circuit based on the right hand side, and the output connected to the signal the left hand side
- **Every assignment is a register (i.e. synchronous)**



```
module shiftreg (input clk, y,  
                 output reg q);  
    reg q1, q2, q3;  
    always@(posedge clk) begin  
        q1 <= y;  
        q2 <= q1;  
        q3 <= q2;  
        q  <= q3;  
    end  
endmodule
```
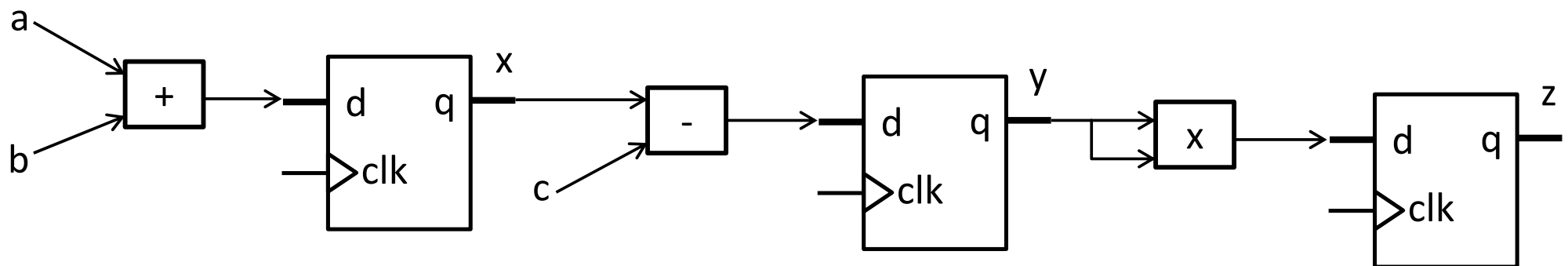
# What Gets Synthesized?

```
always@(posedge clk)
begin
    x <= a + b;
    y <= x - c;
    z <= y * y;
end
```




# What Gets Synthesized?

- It is also possible to separate the combinational and synchronous parts

```
always @ (posedge clk)
begin
    x <= a + b;
    y <= x - c;
    z <= y * y;
end
```

```
always @ (posedge clk)
begin
    x <= xt;
    y <= yt;
    z <= zt;
end
```

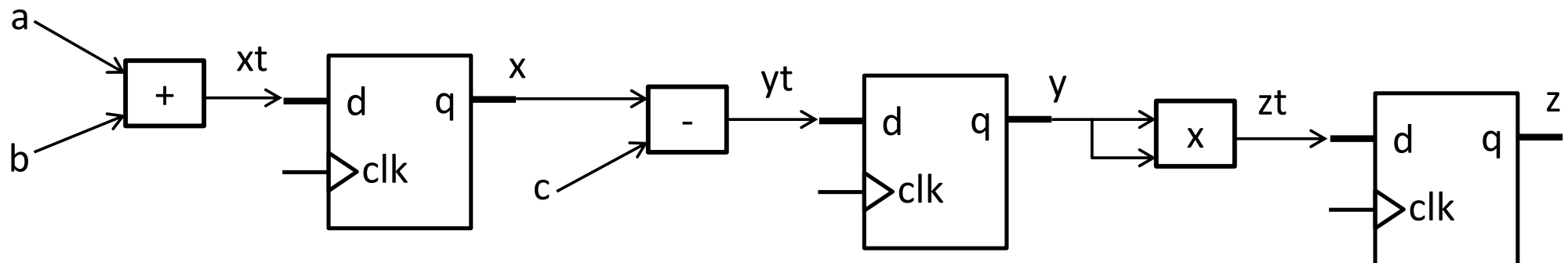
```
always@*
begin
    xt = a + b;
    yt = x - c;
    zt = y * y;
end
```



## Exercise 3

Which of the following is the correct Verilog description of the circuit?

- a. X
- b. Y
- c. Z

 

X

```
always@(posedge Clk)
begin
  if (rst) begin
    Q1 <= 1'b0;
    Q0 <= 1'b0;
  end
  else begin
    Q1 <= ~(Q1);
    Q0 <= ~(Q0) ^ Q1;
  end
end
endmodule
```

Y



```
always@(posedge Clk)
begin
  if (rst) begin
    Q1 <= 1'b0;
    Q0 <= 1'b0;
  end
  else begin
    Q1 <= ~(Q1);
    Q0 <= ~(Q1) ^ Q0;
  end
end
endmodule
```

Z

```
always@(posedge Clk)
begin
  if (rst) begin
    Q1 <= 1'b0;
    Q0 <= 1'b0;
  end
  else begin
    Q1 <= ~(Q0);
    Q0 <= ~(Q0) ^ Q1;
  end
end
endmodule
```
  
## Exercise 4

What is the correct output sequence of Q1 and Q0 observed at the dash lines?



- A. Q1: 1010; Q0: 0011
- B. Q1: 0101; Q0: 1010
- C. Q1: 1010; Q0: 1100
- D. None of the above

Ans: C  
Q1 will just toggle



# Selected Past Exam Questions

## CE/CZ1005 2018-2019 Semester 1 (Nov/Dec 2018)

Q4(a) Write the Verilog code for an 8-bit up/down counter (controlled by a single bit *up* input). Use a ***parameter*** statement to define the counter width (e.g. 8 bits). (8 marks)

ANS:

```
module cnt8bit #(parameter SIZE=8) (input clk, rst,
                                     up, output reg [SIZE-1:0] count);

    always @ (posedge clk)
    begin
        if (rst)
            count <= 0;                //or 8'h00;
        else if (up)
            count <= count + 1'b1;    //or count+1;
        else
            count <= count - 1'b1;
    end
endmodule
```

# Selected Past Exam Questions


## CE/CZ1005 2018-2019 Semester 2 (Apr/May 2019)

Q4(a) Fig Q4a shows a sequential Verilog module.

- (i) Draw the circuit described by the Verilog module in Figure Q4a with D-type flip-flops and logic gates.

5 marks

```
module mod1 (input clk, rst, output reg A, B, C);  
  
    always@(posedge clk)  
    begin  
        if (rst) begin  
            A <= 1'b0;  
            B <= 1'b0;  
            C <= 1'b0;  
        end  
        else begin  
            C <= B;  
            B <= A;  
            A <= A ^ ~(B ^ C);  
        end  
    end  
endmodule
```

 



**Figure Q4a**

# Selected Past Exam Questions

## CE/CZ1005 2018-2019 Semester 2 (Apr/May 2019)

Q4(a) Fig Q4a shows a sequential Verilog module. 8 marks

- (ii) Complete the timing diagram shown in Figure Q4b for the Verilog module in Figure Q4a by drawing the waveforms for  $A$ ,  $B$  and  $C$ . Assume that  $rst = 0$ .

  


**Figure Q4b**

# Selected Past Exam Questions


## CE/CZ1005 2017-2018 Semester 1 (Nov/Dec 2017)

Q4(b) Figure Q4a shows a binary ripple counter. Sketch the timing diagram of each of the outputs  $Q_0$ ,  $Q_1$  and  $Q_2$  for six clock cycles. Assume the initial state of  $Q_2 Q_1 Q_0 = 000$ .

(7 marks)

 

 ANS: Firstly, the counter is negative edge triggered. Second, for a JK FF, when  $J=K=1$ , the Q output toggles.



# Selected Past Exam Questions

## CE/CZ1005 2016-2017 Semester 2 (Apr/May 2017)

Q4(b) Write the Verilog module *PISO* which is a parallel-in/serial-out register. The inputs to the module are *IN*[3:0], *CLK* and *LOAD*. When *LOAD* is high, the register is loaded with the value of *IN*. The output of this module is *OUT*.

YUK. Upper case!!!!

(7 marks)

ANS:

```
module PISO (input CLK, LOAD, input [3:0] IN,
             output OUT);
    reg [3:0] q;
    always @ (posedge CLK)
    begin
        if (LOAD)
            q <= IN;
        else
            q[3:0] <= {q[2:0], 1'b0};
    end
    assign OUT = q[3];
endmodule
```

Also Note that there is no real need for reset. Adding a reset is OK.

Note: There is no need to feed IN[0] into the LSB. Zero is fine.

