

Course contents

Design with Hardware Description Language: Structural and behavioural Verilog

Combinational logic circuits

Encoder, decoder, multiplexer

Sequential logic circuits

Counter, register, finite state
machine

Digital circuits

Flip-flops

Number
systems
and codes

Logic
gates

Boolean
algebra

Digital
arithmetic

Boolean
expression
simplification

Lecture 11 key concepts

- **Digital circuits transfer characteristic**
- **Voltage parameters and noise margins**
- **Current parameters and fan-out**
- **Power dissipation, switching speed and propagation delay**
- **Rise time and fall time**
- **Tri-state output**
- **Open-drain output**

Which concepts are unclear to you after viewing L11?

- A. Voltage/current parameters
- B. Noise margin and fan-out
- C. Power dissipation
- D. Timing parameters
- E. Tristate output
- F. Open drain output
- G. none

Static characteristics

Static

- When outputs are not changing


Voltage/current parameters

DC noise margin =

$$\min \{ V_{OH}(\min) - V_{IH}(\min), \\ V_{IL}(\max) - V_{OL}(\max) \}$$

$$\text{DC fan-out} = \min \{ I_{OH} / I_{IH}, I_{OL} / I_{IL} \}$$

VOH, IOH, VIH, IIH

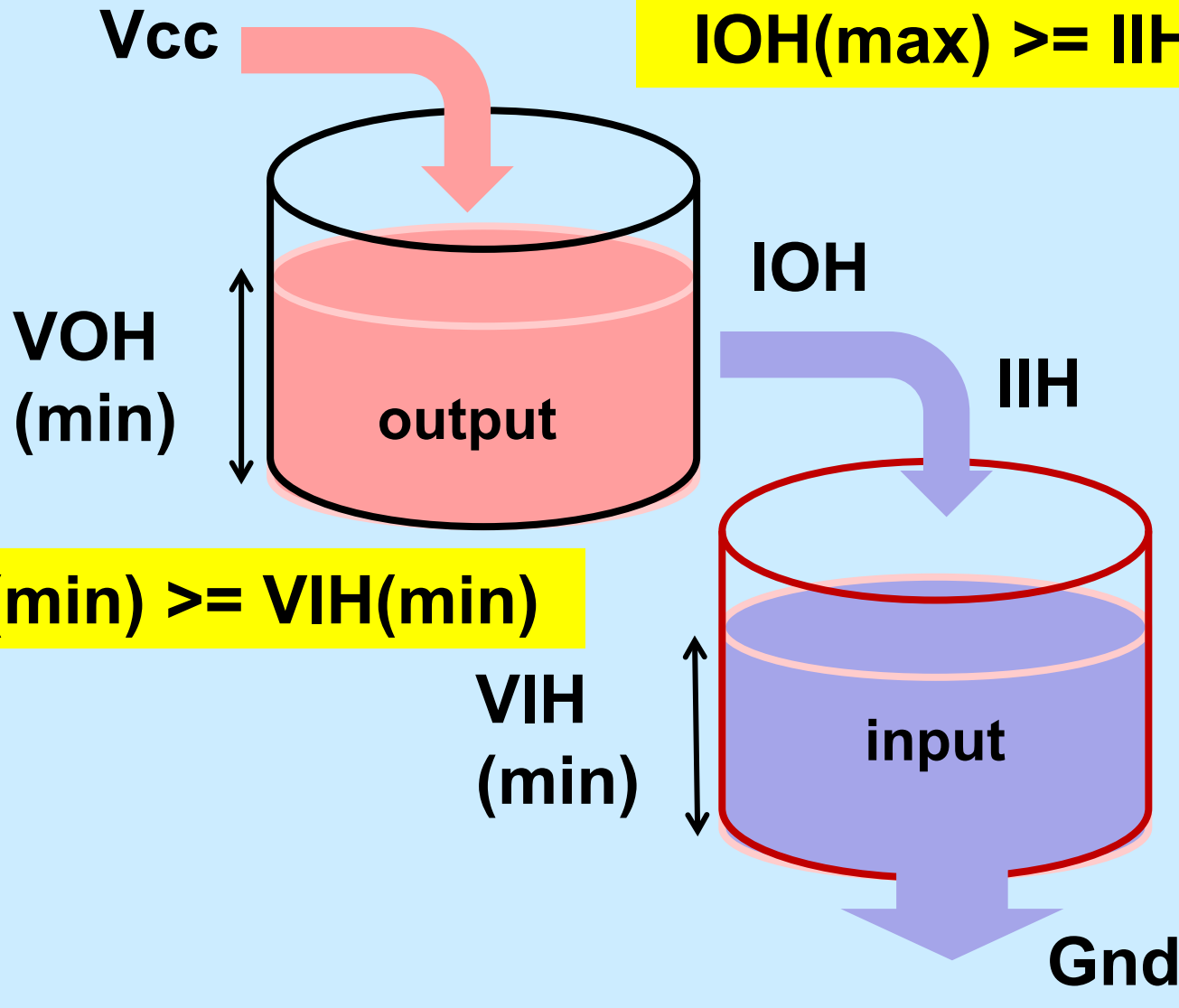


$$IOH(max) \geq IIH(max)$$

$$VOH(min) \geq VIH(min)$$

VOL, IOL, VIL, IIL

$$IOL(max) \geq IIL(max)$$

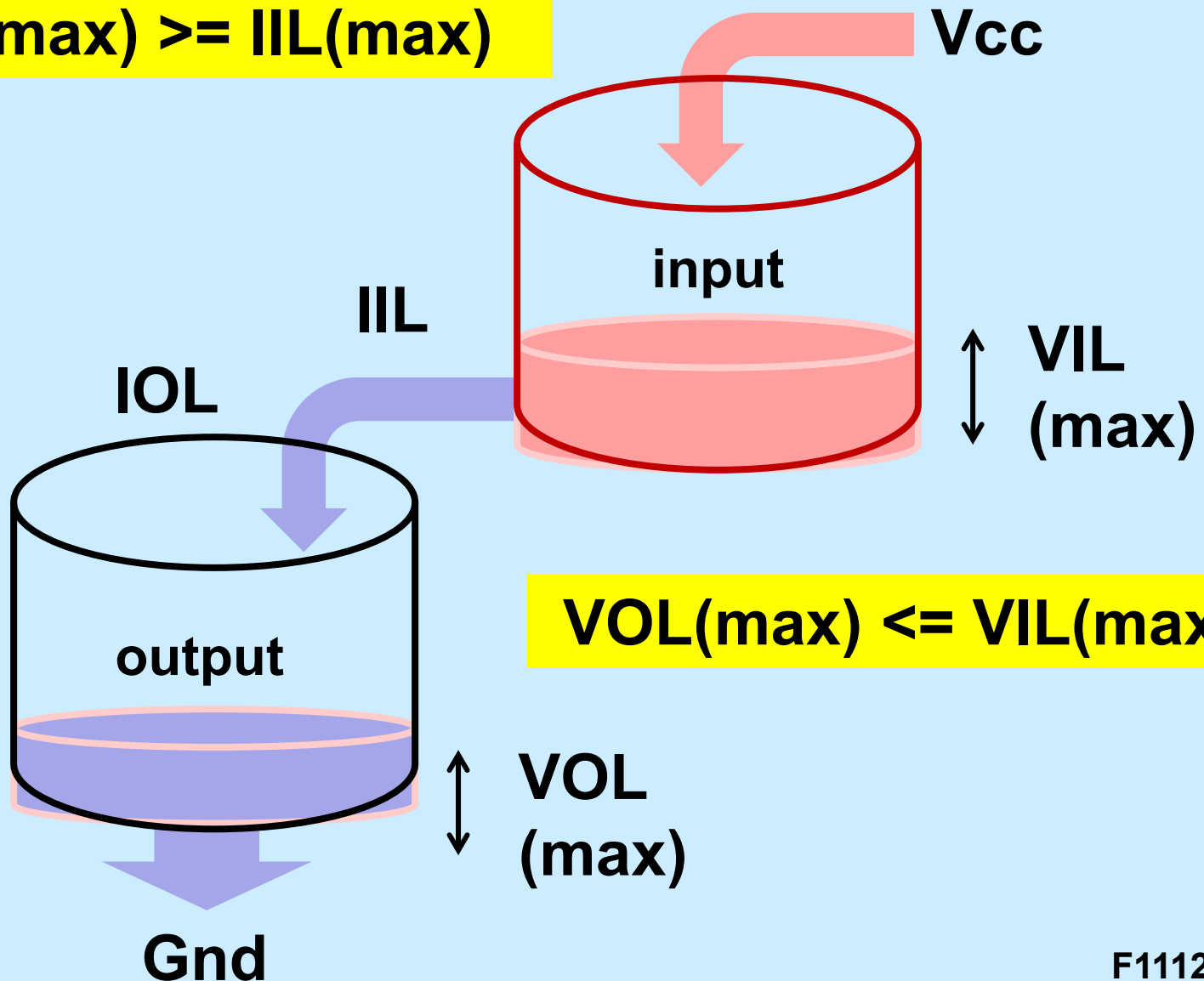

Requirements for device A to drive device B:

A's output provides	$\leq / \geq ?$	B's input requires
$V_{OH}(\text{min})$		$V_{IH}(\text{min})$
$I_{OH}(\text{max})$		$I_{IH}(\text{max})$
$V_{OL}(\text{max})$		$V_{IL}(\text{max})$
$I_{OL}(\text{max})$		$I_{IL}(\text{max})$

DC noise margin = min(Difference in input/output voltages)

DC fan-out = min(Ratio of output/input currents)

Dynamic characteristics

Dynamic

- When outputs are changing

Low is better:

Power dissipation, propagation delay,
rise time and fall time

High is better:

Switching speed

Tristate output

Enabled output: 0, 1

Disable output: H-Z (High-impedance)


Connected tristate outputs:


Why not more than one output can be enabled?

Question: which is which?

(a)	(b)
Outputs can be connected together	
Does not require external pull-up resistor	Requires external pull-up resistor
Has enable input	Does not have enable input
At most one individual output can produce High or Low (i.e. enabled) at any time. The rest must be Hi-Z.	Each individual output can produce High or Low at any time.
Common output follows enabled output; Hi-Z when all outputs are disabled	Common output is wire-AND of individual outputs


Connected open-drain outputs

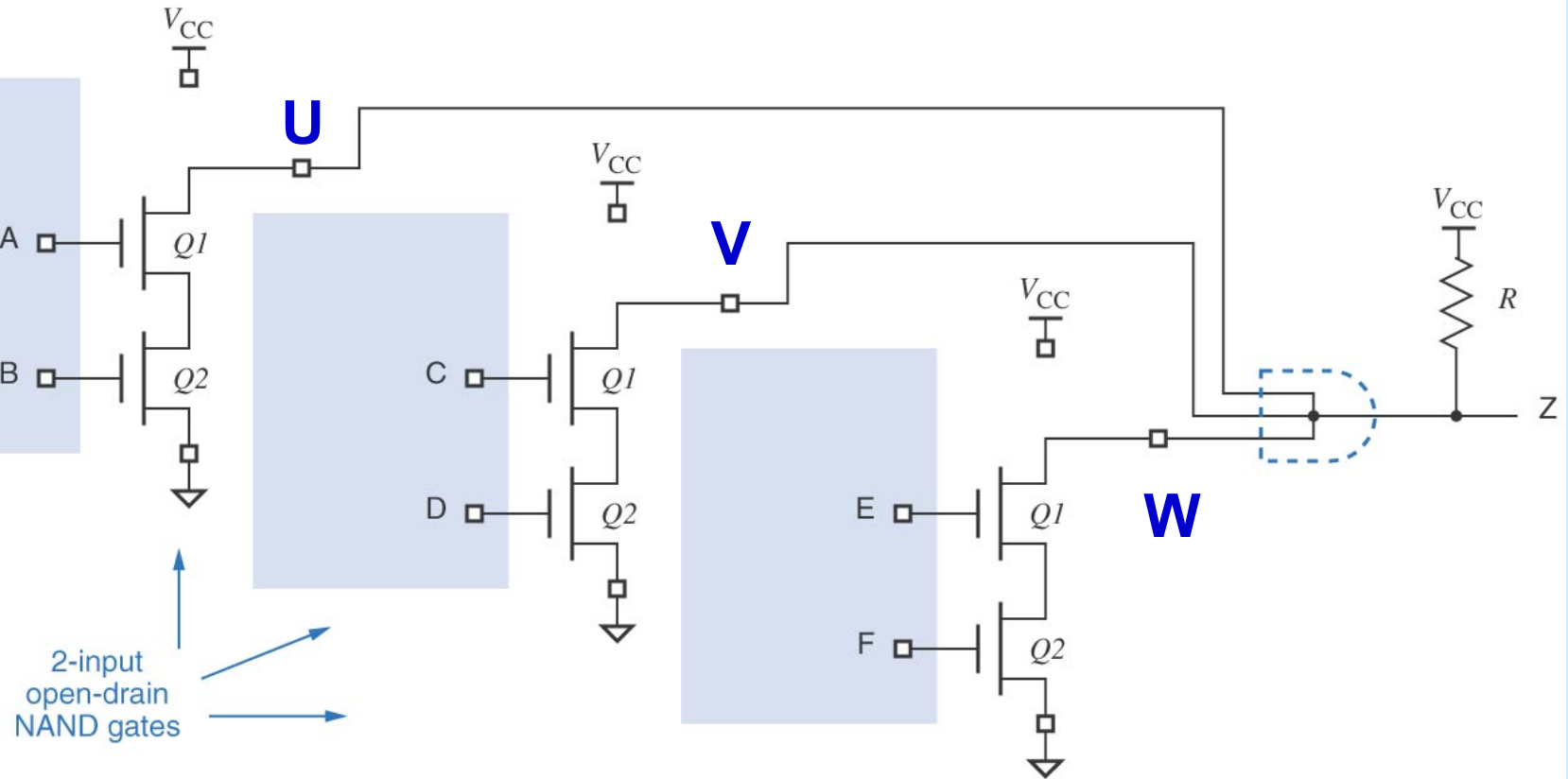

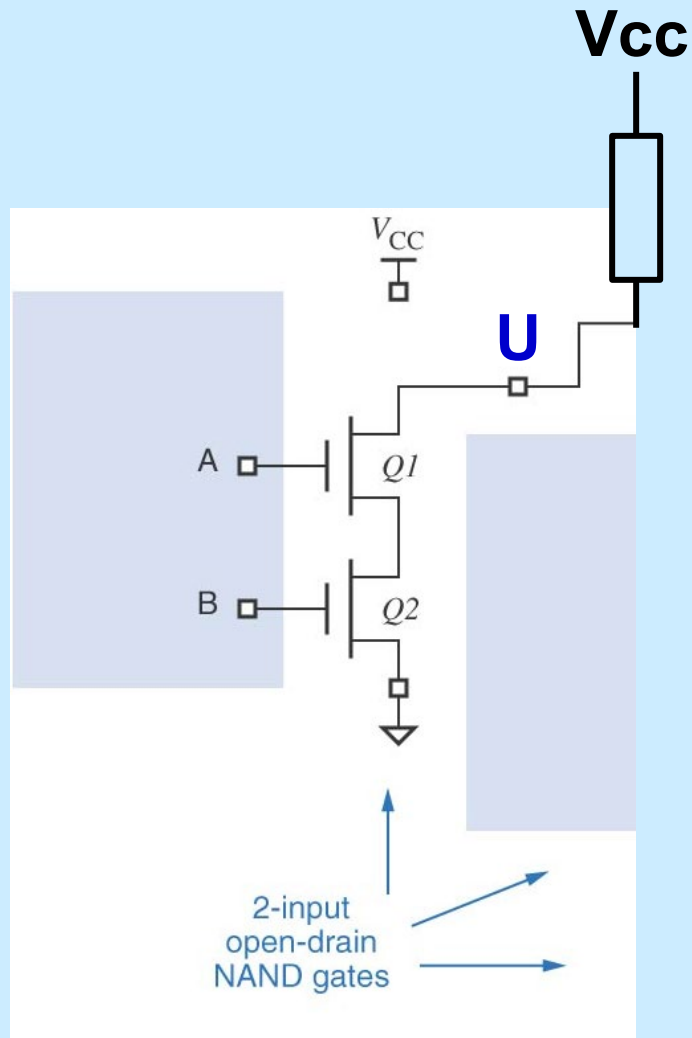

$$U = (AB)'$$

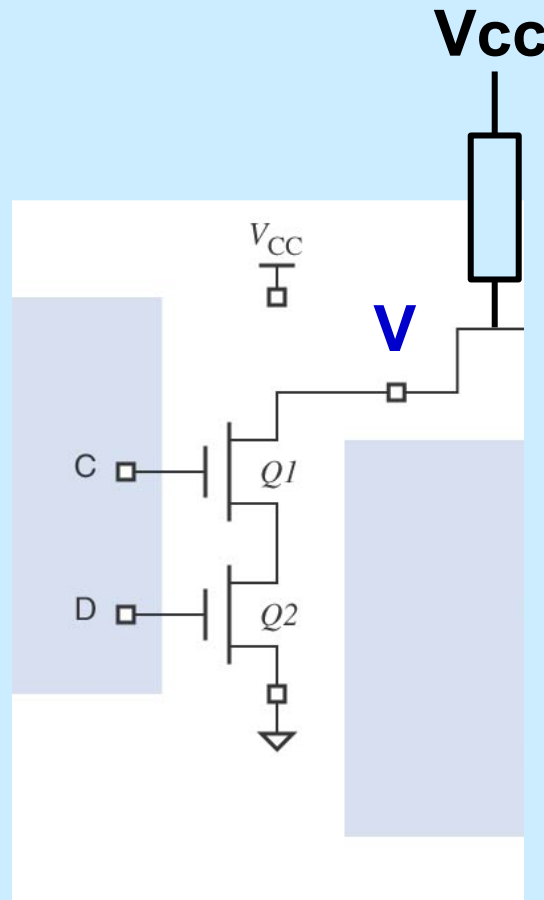
Each NAND gate can work on its own **with a pull-up resistor**



$$V = (CD)'$$


Each NAND gate can work on its own **with a pull-up resistor**

$$W = (EF)'$$

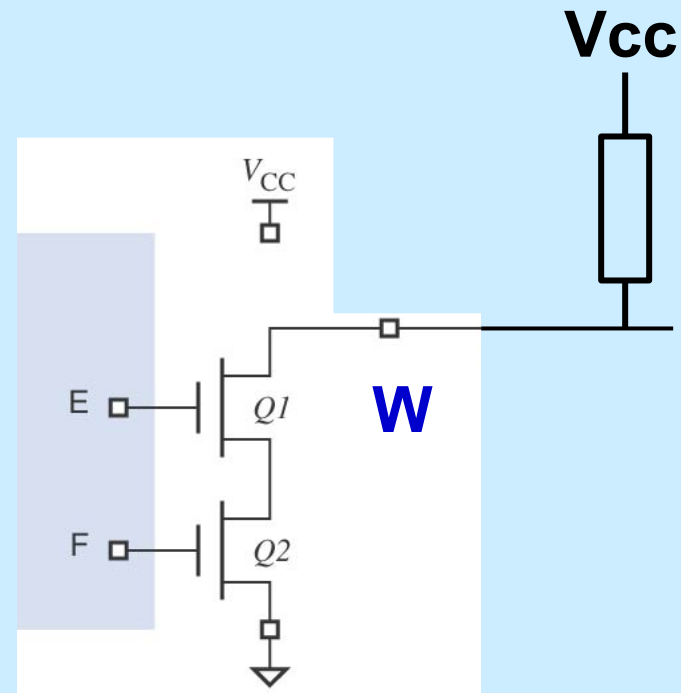

Each NAND gate can work on its own **with a pull-up resistor**

Wired-AND output

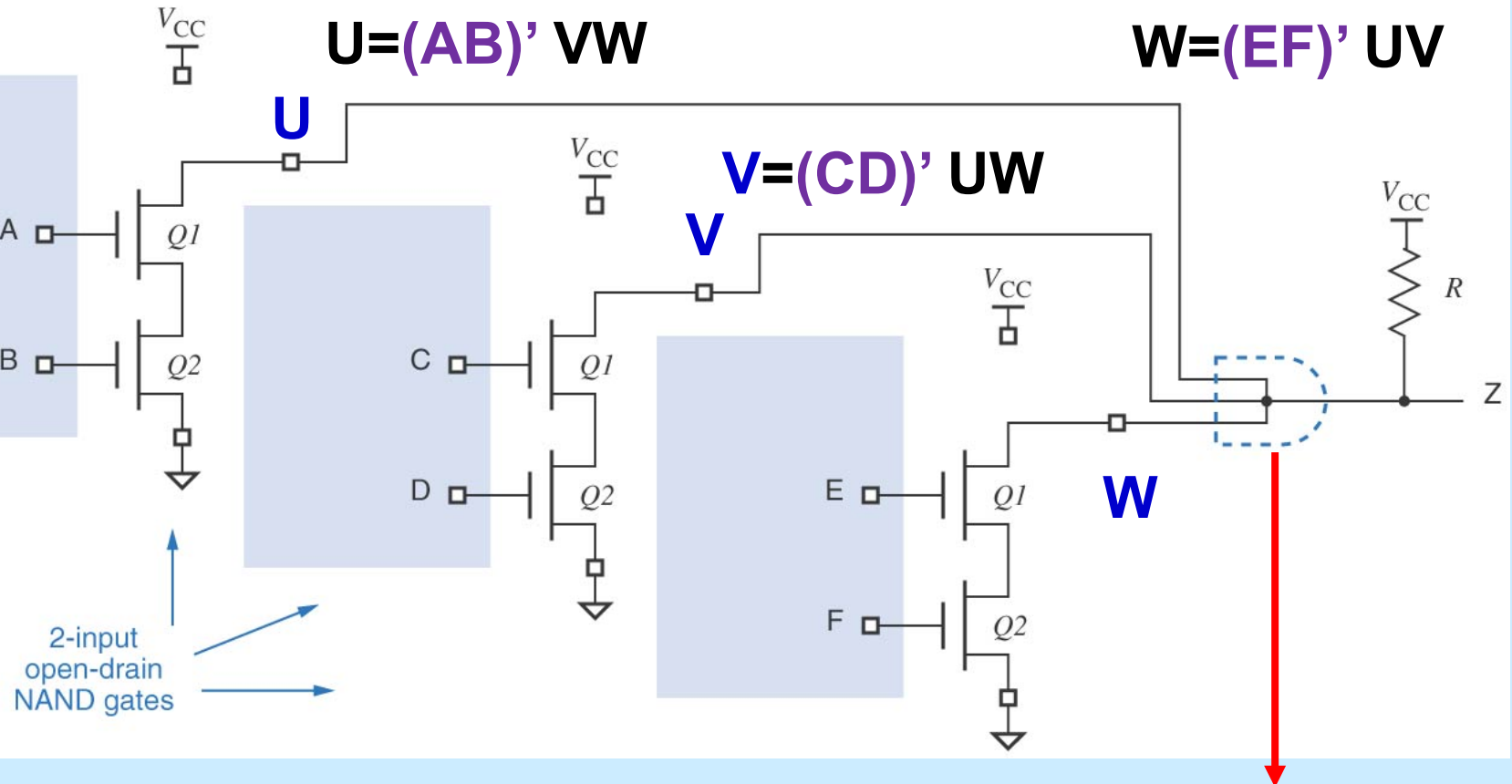

Wired-And: is a behavior, not an AND gate

$Z = 0$ if $U=0$, or $V=0$ or $W=0$

End of L11 summary

Lecture 12 key concepts

- **Schmitt-trigger inputs**

Key parameters: V_{T-} , V_{T+}

- **Programmable Logic Arrays**


Implement SOP with some flexibility

- **Fixed point and floating point numbers -**
Pros and cons


Which concepts are unclear to you after viewing L12?

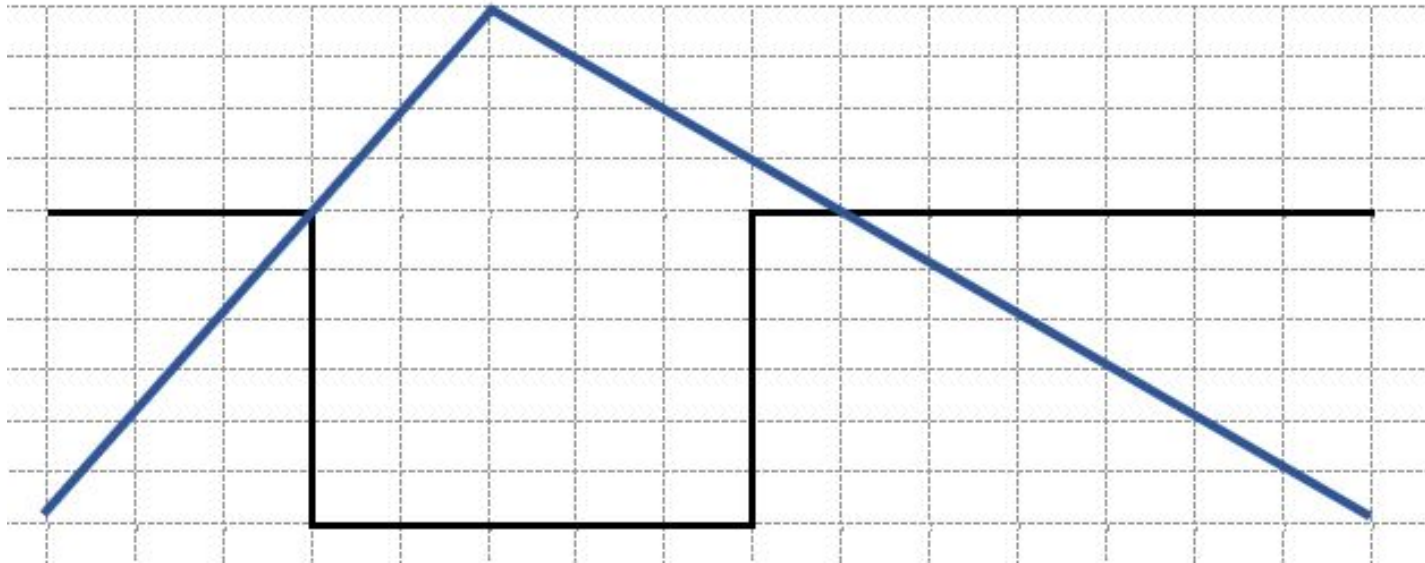- A. Schmitt-trigger input
- B. Programmable logic array
- C. Floating point number
- D. none

Are these input/output waveforms of a Schmitt-trigger buffer or inverter?




Programmable Logic Devices

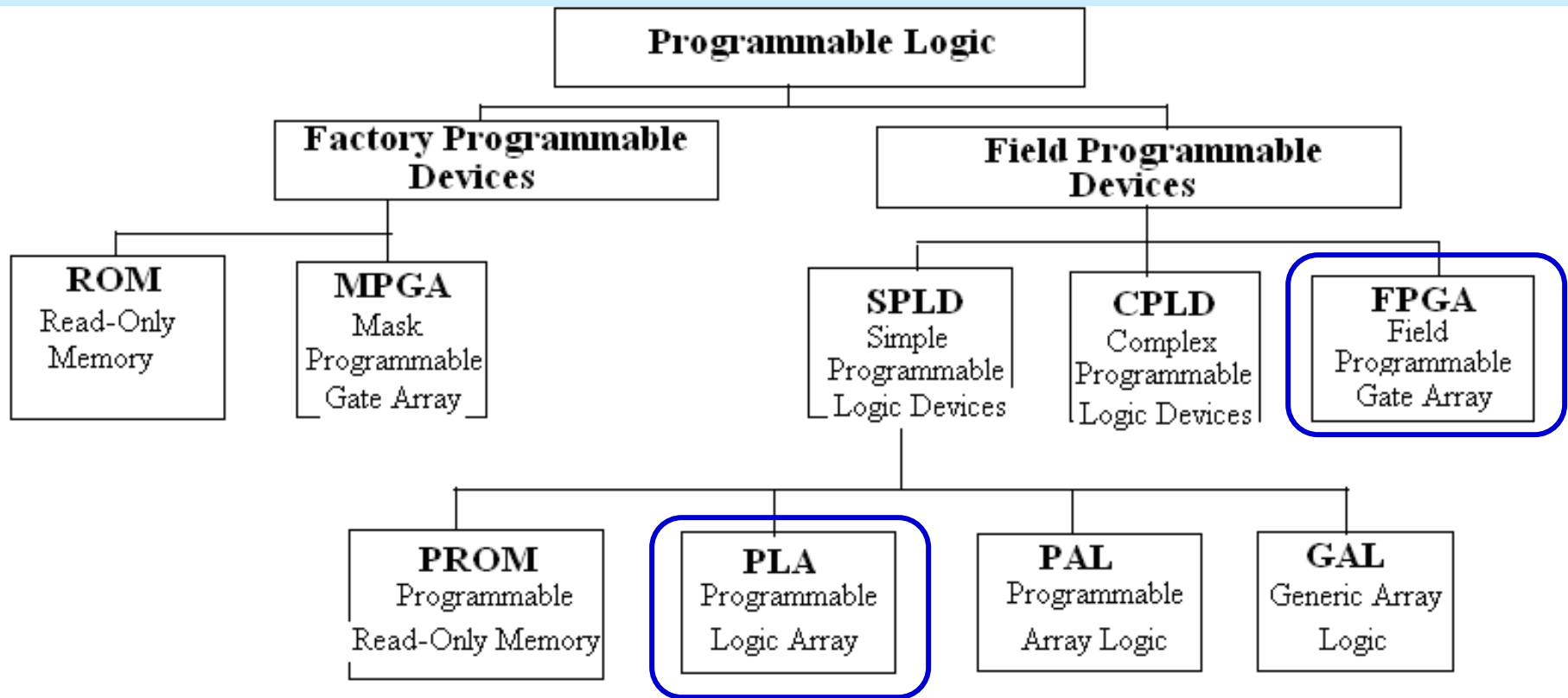

Digital Systems Design Using Verilog, Roth, John, Lee.
Cengage 2016.

Programmable Logic Arrays

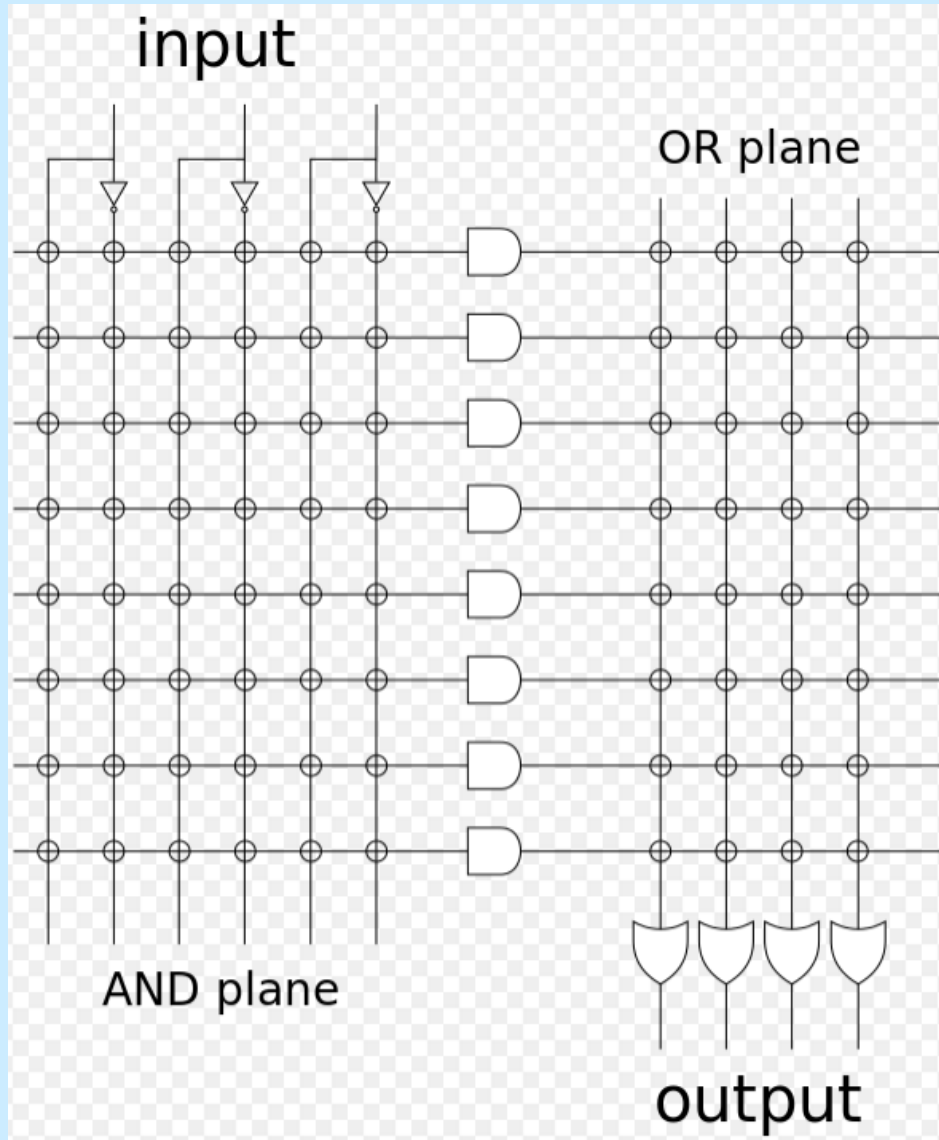

**Both AND
plane and OR
plane are
programmable**

What circuit is implemented?

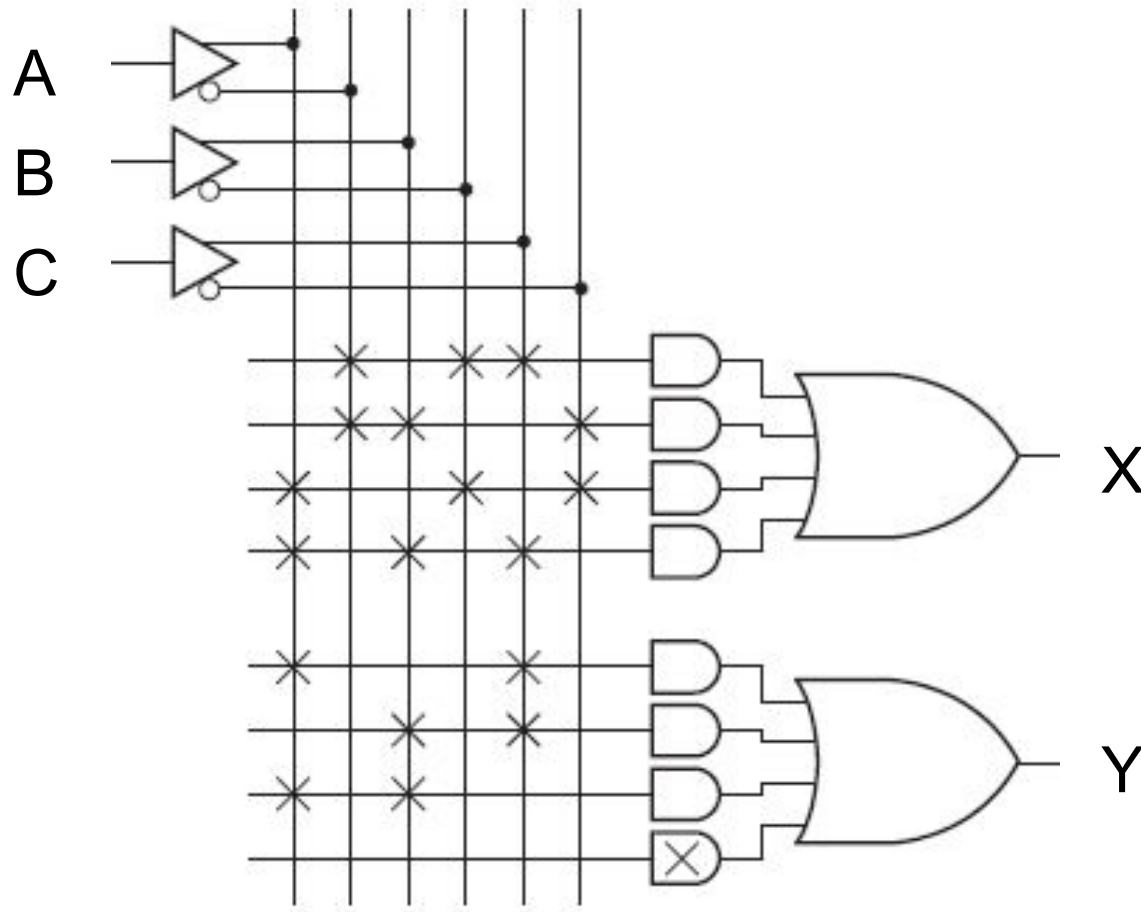


Fig. 9.33 from Fundamentals of Logic Design by Roth and Kinney

Fixed/floating point example

Store the unsigned decimal value 15.9375

15.9375(dec) = 1111.1111(bin)

Fixed point:

1111 1111



is not stored

Floating point:

0011 1111

1111.1111 = 1.1111111x2³

4-bit significand=1111

4-bit exponent=0011

1. is not stored

Range of values

Compare largest value represented

Fixed point:

1111 . 1111

= 15.9375(dec)

Floating point:

0111 1111

= 1.1111 x 2⁽⁺⁷⁾

= 1111 1000(bin)

= 248(dec)

Given the same number of bits, floating point can represent a much wider range of values than fixed point but is more complex.

Disadvantage of fixed point

e.g. Multiply 0.0010 with 0.0011 = 0.0000011

Fixed point result:

0000 . 0000


Floating point
result:

1010 1000

= 1.1000 x 2⁽⁻⁶⁾

Fixed-point arithmetic such as multiplication may result in a loss of significant bits.

Disadvantage of floating point

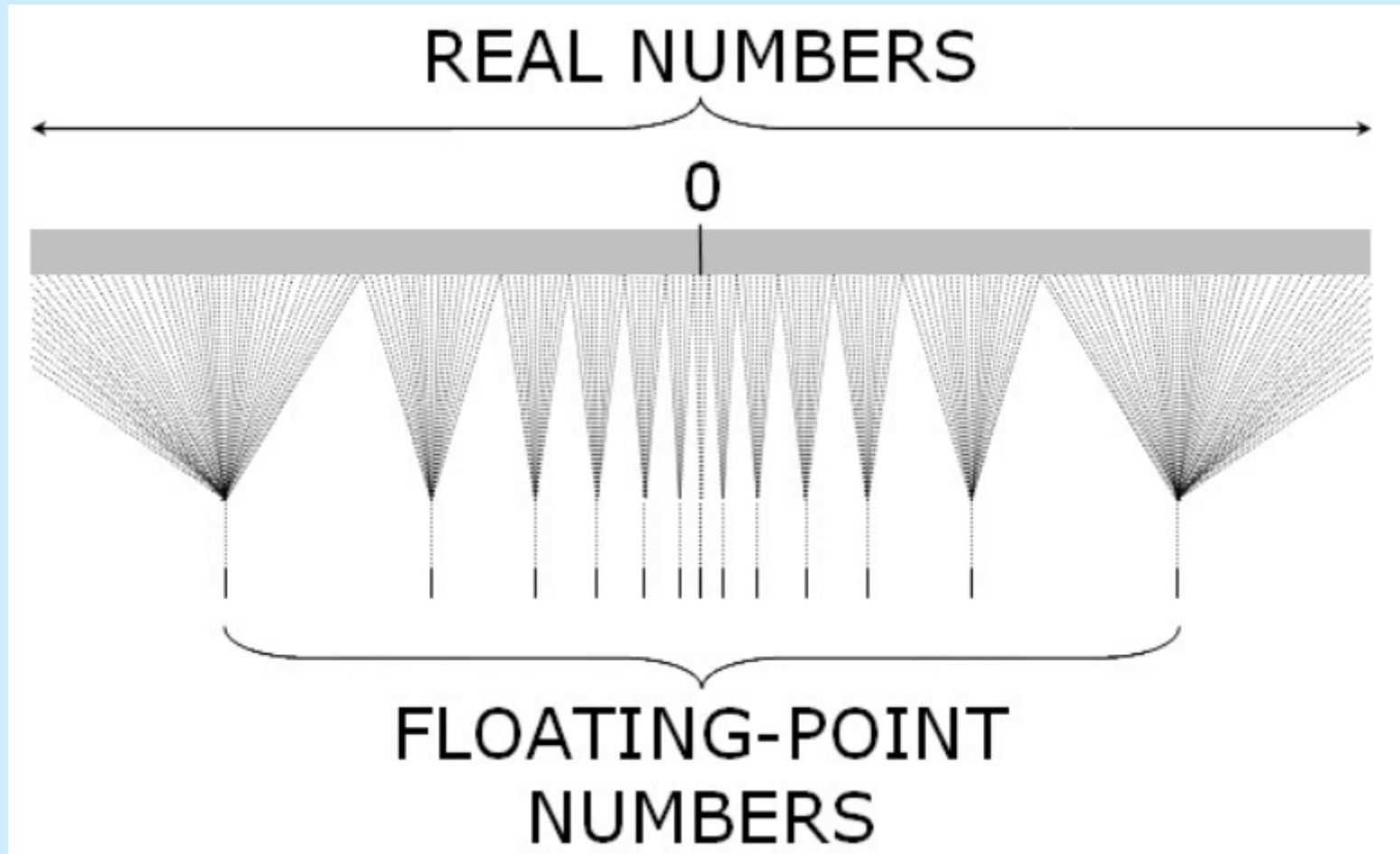

<http://jasss.soc.surrey.ac.uk/9/4/4.html>

End of L12 summary