

L4 (4.1 – 4.22)

- Half adder and full adder
- Parallel adder
- Carry propagation
- Sign-magnitude representation of signed numbers
- 2's complement representation of signed numbers

4. Digital Arithmetic

In digital circuits, e.g. digital computers and electronic calculators, arithmetic operations are carried out on binary numbers:

- **Addition, subtraction, multiplication and division**

Binary Addition and Subtraction both begin with the **LSB (least significant bit)**

Decimal Addition and Subtraction both begin with the **LSD**:

carry

$$\begin{array}{r} 1764_{10} \\ + 583_{10} \\ \hline 1347_{10} \end{array}$$

borrow

$$\begin{array}{r} 6\cancel{7}^164_{10} \\ - 583_{10} \\ \hline 181_{10} \end{array}$$

Binary addition example:

$$10111_2 + 1010_2 = ?$$

$$(23_{10} + 10_{10} = 33_{10})$$

$$\begin{array}{r} 10111_2 \\ + 1010_2 \\ \hline \\ \hline \end{array}$$

Adder

Half adder (HA)

- combination logic circuit that performs addition of **2 bits**

$$\text{Carry} = A \cdot B$$

$$\text{Sum} = A \oplus B$$

Inputs		Outputs	
A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Full adder (**FA**)

- combination logic circuit that performs addition of **3 bits**

Inputs			Outputs	
A	B	Cin	Cout	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Since the truth table is rather simple, we can obtain the Boolean expressions by observation,

$$\text{Sum} = \mathbf{A \oplus B \oplus Cin}$$

$$\text{Cout} = \mathbf{A \bullet B + B \bullet Cin + A \bullet Cin}$$

Fig 6.81 shows the circuit implementation.

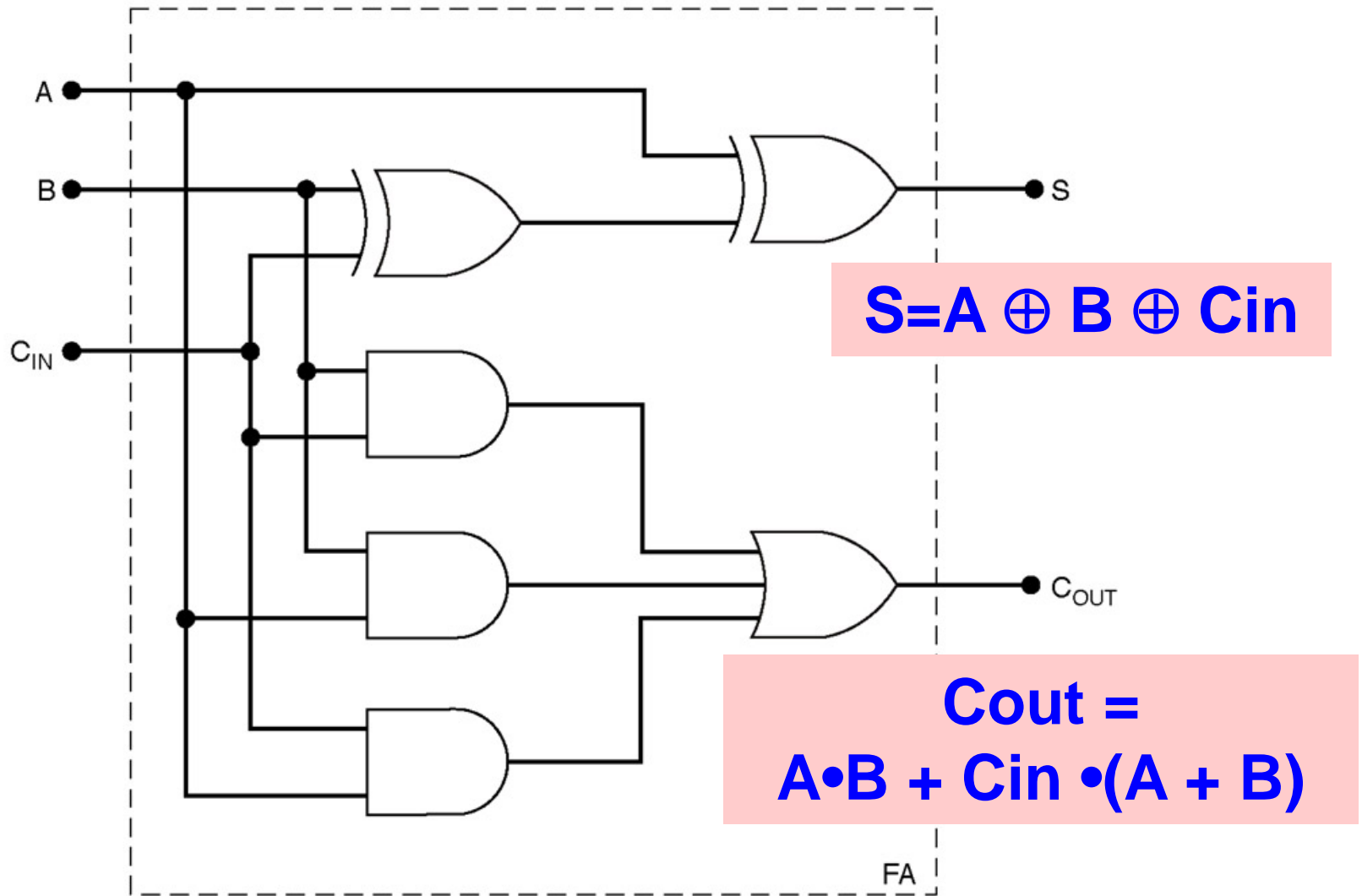


Fig. 6-81 Full adder circuit

If we re-arrange the Boolean expression,

$$\text{Cout} = A \bullet B + B \bullet \text{Cin} + A \bullet \text{Cin}$$


$$= A \bullet B + \text{Cin} (A' B + AB) + \text{Cin} (AB' + AB)$$

$$= A \bullet B + \text{Cin} (AB) + \text{Cin} (A' B + AB')$$

$$= \underbrace{A \bullet B}_{\text{red}} + \text{Cin} \bullet (A \oplus B)$$

- An alternate circuit implementation using Half-adders is obtained

 Full adder circuit implemented using 2 half-adders and an OR gate



$$S1 = A \oplus B$$

$$C1 = A \cdot B$$


$$S2 = (A \oplus B) \oplus Cin$$

$$C2 = Cin \cdot (A \oplus B)$$

$$Cout = A \cdot B + Cin \cdot (A \oplus B)$$

Binary addition example: $0101_2 + 0111_2 = ?$

Need 4 FAs

 

Parallel Adder

- N full-adders can be **cascaded** to form an N-bit parallel adder
- also known as ripple adder
- all the bits of the augend and addend are fed into the adder circuits simultaneously
- addition is very fast
- addition speed is limited by propagation delays of FAs - **carry propagation**
- Fig. 6-82 shows a 4-bit adder

Example: $0011_2 + 0001_2 = 0100_2$

(In decimal: $3 + 1 = 4$)

 


Fig. 6-82 : 4-bit ripple adder

Representing Signed Numbers

Signed-Magnitude system

- sign bit = MSB : 0 for positive numbers
- sign bit = MSB: 1 for negative numbers

$$14_{10} = 1\ 1\ 1\ 0_2$$

	sign	magnitude
+14	0	1 1 1 0
-14	1	1 1 1 0

Signed-Magnitude system

- There are equal numbers of positive and negative values
- An N-bit value lies in the range
 $\{ -(2^{N-1} - 1) \text{ to } +(2^{N-1} - 1) \}$

Examples:

$$0101\ 0101_2 = +85_{10}$$

$$1101\ 0101_2 = -85_{10}$$

$$0000\ 0000_2 = +0_{10}$$

$$1000\ 0000_2 = -0_{10}$$

2's complement system

- sign bit = MSB: 0 for zero and positive numbers
- sign bit = MSB: 1 for negative numbers

$$14_{10} = 1\ 1\ 1\ 0_2$$

	sign	
+14	0	1 1 1 0
-14	1	???

2's complement operation:

Step 1: invert every bit of a binary number
(i.e. perform **1's complement**)

$$\begin{array}{|c|c|c|c|} \hline 1 & 1 & 1 & 0 \\ \hline \end{array} \longrightarrow \begin{array}{|c|c|c|c|} \hline 0 & 0 & 0 & 1 \\ \hline \end{array}$$

Step 2: add (arithmetic addition) **1** to it

$$\begin{array}{|c|c|c|c|} \hline & 0 & 0 & 0 & 1 \\ \hline + & & & & 1 \\ \hline 0 & 0 & 1 & 0 \\ \hline \end{array}$$

The 2's complement of 1110 is 0010

2's complement system

$$14_{10} = 1\ 1\ 1\ 0_2$$

	sign	
+14	0	1 1 1 0
-14	1	0 0 1 0

A short-cut method for 2's complement operation:

- **starting from LSB, copy the bit if it is '0' and repeat process with remaining bits**
- **copy the bit if it is the first '1', then invert all the remaining bits**
- **a sequential process**

This method works on all binary bit patterns

Examples:


$$0\ 1\ 0\ 1\ 0\ 1\ 0\ 1_2 = +85_{10}$$



$$1\ 0\ 1\ 0\ 1\ 0\ 1\ 1_2 = -85_{10}$$

**Invert the
remaining
bits**

$$0\ 1\ 0\ 0\ 0\ 0\ 0\ 0_2 = +64_{10}$$

 

$$1\ 1\ 0\ 0\ 0\ 0\ 0\ 0_2 = -64_{10}$$

**Copy the
bits from
the right
until it
reaches
the first 1**

2's complement system

- There is 1 more negative value than positive ones
- An N-bit value lies in the range
 $\{ -(2^{N-1}) \text{ to } +(2^{N-1} - 1) \}$
- Eg. 4 bits: $\{-8, 7\}$
- 8 bits: $\{-128, 127\}$

Summary: representing signed numbers in 2's complement system:

If the number is **zero or positive**

- represent its magnitude in binary
- append a sign bit (0) in front of the MSB if the MSB is 1

If the number is **negative**

- represent its magnitude in binary
- obtain the 2's complement
- append a sign bit (1) in front of the MSB if the MSB is 0

Examples: Represent the following signed decimal numbers in 2's complement

(a) 5

- binary of 5 is 101
- Positive 5 is **0101**

(b) -7

- binary of 7 is 111
- 2's complement of 111 is 001
- Negative 7 is **1001**

L5 (4.23 – 4.41)

- Sign-extension for 2's complement numbers
- 2's complement add/subtract
- Arithmetic overflow

E.g. A 4-bit 2's complement number system:

Decimal	Binary	
	magnitude	2's comp
-8	1000	1000
-7	0111	1001
-6	0110	1010
-5	0101	1011
-4	0100	1100
-3	0011	1101
-2	0010	1110
-1	0001	1111
0	0000	0000
1	0001	0001
2	0010	0010
3	0011	0011
4	0100	0100
5	0101	0101
6	0110	0110
7	0111	0111

Generalised to an N-bit 2's complement number system:

Decimal	2's comp	
$-(2^{N-1})$	$1000\dots00$	← Most negative
$-(2^{N-1}) + 1$	$1000\dots01$	
$-(2^{N-1}) + 2$	$1000\dots10$	
.	.	
.	.	
-1	$1111\dots11$	← -1
0	$0000\dots00$	← zero
1	$0000\dots01$	
2	$0000\dots10$	
.	.	
.	.	
$(2^{N-1}) - 2$	$0111\dots10$	
$(2^{N-1}) - 1$	$0111\dots11$	← Most positive

Some special bit patterns:

- **100....000 (with N-1 zeros)**

the decimal value is $-(2^{N-1})$

- **111....111 (all ones)**

the decimal value is -1

- **000....000 (all zeroes)**

the decimal value is 0

- **011....111 (with N-1 ones)**

the decimal value is $(2^{N-1}-1)$

Obtaining the decimal value of a 2's complement number

If the number is **positive**:

- perform a binary-to-decimal conversion on the number

If the number is **negative**:

- First perform 2's complement to convert it to **positive**
- Next perform a binary-to-decimal conversion on the **positive** number

Examples: Obtain the decimal equivalent of the following 2's complement numbers

(a) 01001

- The magnitude 1001 is 9 in decimal
- 01001 is **positive 9** in decimal

(b) 10011

- 2's complement of 10011 is 01101
- The magnitude 1101 is 13 in decimal
- 10011 is **negative 13** in decimal

Some observations on the 2's complement number system

- The 2's complement of an N -bit binary number is also of N bits.
- To represent a binary number with N significant bits in its magnitude using the 2's complement system, we need $(N+1)$ bits. The extra bit is the sign bit. *

* note exception

- If there are more bits than necessary to represent a binary number in the 2's complement system, the more significant bits are filled with the sign bit, which is 0 for positive and 1 for negative – known as **sign extension**

$$101 = 1101 = 11101$$

$$011 = 0011 = 00011$$

- A 2's complement operation will change a positive number to negative and vice-versa, with no change in the magnitude. *

*** note exception**

*** Exception arises when dealing with the most negative number that can be represented given a number of bits.**

e.g.

-8 in a 4-bit system,

-16 in a 5-bit system

-128 in an 8-bit system

$-(2^{N-1})$ in an N-bit system

Reasons for using the 2's complement system:

- **Using the 2's complement representation for signed numbers, subtraction of numbers can be carried out in the same way as addition**
- **Therefore, the same set of hardware circuits can be used for both subtraction and addition**


Addition in the 2's complement system

two positive numbers

+10	0	1	0	1	0	(augend)
+3	0	0	0	1	1	(addend)
<hr/>						
+13	0	1	1	0	1	(sum)
<hr/>						

↑
sign bit

 The sign bits are added like the other bits
positive number and smaller
negative number




positive number and larger negative number

-10	1	0	1	1	0
+3	0	0	0	1	1
<hr/>					
-7	1	1	0	0	1
<hr/>					

↑

sign bit

two negative numbers

 

Subtraction in the 2's complement system

Subtraction can be carried out using 2's complement and addition

$$A - B = A + (-B)$$

-B = 2's complement of B

B may be positive or negative

Examples:

$$10 - 3 = 10 + (-3) = 7$$

-3 is 2's complement of 3

Ignore
carry out



	1	0	1	0	1	0
+	1	1	1	0	1	
<hr/>						
1	0	0	1	1	1	
<hr/>						

$$-10 - (-3) = -10 + 3 = -7$$


3 is 2's complement of -3

	1	1	0	1	1	1	0
+	0	0	0	1	1		
<hr/>							
1	1	0	0	1			
<hr/>							

Remember:


The pair of numbers to be added/subtracted must have the same size, i.e. same number of bits. This ensures that the sign bits are aligned. The resulting sum must also be of the same size.

 Addition and Subtraction in the 2's complement system



Arithmetic Overflow

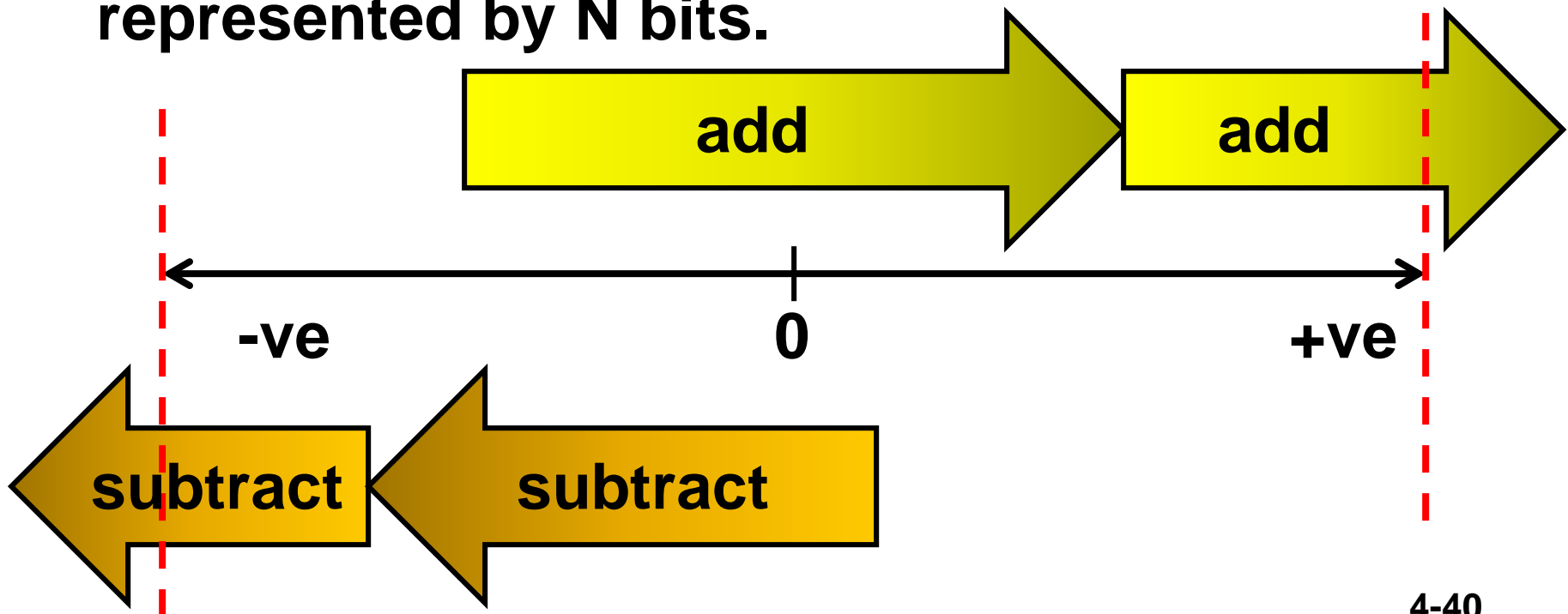
It occurs when an arithmetic operation between two N-bit operands produces a result that cannot be sufficiently represented by N bits.



Rules to detect overflow in 2's complement addition:

No overflow occurs if the operands have opposite signs.

 Overflow is detected when operands have the **same sign**, but the arithmetic sum has an **opposite sign**.



	1	0	1	0	1	0
	0	1	0	0	0	0
<hr/>						
	1	0	0	1	0	0
<hr/>						

10+8=-14?

For **subtraction**, no overflow occurs if the operands have the same sign.

L6 (4.42 – 4.58)

- Circuit for 2's complement add/subtract
- Parallel addition with registers
- Multiplication
- BCD addition

Combined circuit for addition and subtraction

Fig 6-12 (**X0 and Y0 are LSB**)

- To perform the addition: $X + Y$
- Make inputs Add/Sub = 0, $C0 = 0$
- XOR gates do not invert Y
- Inputs to FAs are X and Y, with $C0 = 0$
- E.g. $0001 + 0011 = 0100$
- i.e. $1 + 3 = 4$ (in decimal)

Combined circuit for addition and subtraction

 


Fig 6-12 (add)

Fig 6-12 (subtraction)

- To perform the subtraction: $X - Y$
- Recall: $-Y$ is 2's complement of Y
- Make inputs Add/Sub = 1, $C0 = 1$
- XOR gates invert Y to give Y'
- Inputs to FAs are X and Y' , with $C0 = 1$
- E.g. $0001 - 0100 = 0001 + 1011 + 1 = 1101$
- i.e. $1 - 4 = -3$ (in decimal)

Combined circuit for addition and subtraction

 


Fig 6-12 (subtract)

Fig. 6-9: Complete 4-bit Parallel Adder with Registers

t1: CLEAR* clears the contents of A register to 0's

t2: PGT of first LOAD pulse transfers operand X from memory into B register

t3: PGT of first TRANSFER pulse transfers FA output (=X) into A register

t4: PGT of second LOAD pulse transfers operand Y from memory into B register

t5: PGT of second TRANSFER pulse transfers FA output ($=X+Y$) into A register

- **Note that sufficient time (between load and transfer) must be given to FAs to complete addition**

- **E.g. $0001 + 0010 = 0011$**

Thus A register holds the result of $X+Y$

 
 


Fig.6-9

Carry propagation can be reduced (hence increasing speed of addition) by a special-purposed logic circuit

- **carry-look-ahead circuit**

Many IC parallel adders have built-in carry look-ahead circuit to speed up the addition.

Binary Multiplication

Unsigned multiplication:

similar to decimal multiplication

$$\begin{array}{r} 0111 \quad (7) \\ \times 1100 \quad (12) \\ \hline \end{array}$$


2's complement multiplication:

- **If the multiplier is positive, same as unsigned multiplication**
- **If the multiplier is negative, need to take care of negative weight of MSB (i.e. the sign bit)**
- **Treat multiplier as a sum of 2 parts:**
 - **MSB – negative part**
 - **Remaining bits – positive part**

Example of 2's complement multiplication:

$$\begin{array}{r} -5 \\ x -3 \\ \hline 15 \\ \hline \end{array}$$

Explanation:

$$\begin{aligned} 1011 \times 1101 &= 1011 \times (1000 + 0101) \\ &= (1011 \times 1000) + (1011 \times 0101) \end{aligned}$$


This is done by
shift and
2's complement

This is done by
shift and sign-
extension

Binary Division

Unsigned division:

similar to the long division method in decimal arithmetic

$$9 \div 3 = 3$$

Signed division:

convert the signed numbers to unsigned, divide them as above, then convert the result using the appropriate sign representation

BCD addition

When the sum of two BCD digits does not exceed 9_{10} , the operation is the same as binary addition

If the sum of two BCD digits is more than 9_{10} , a **correction** needs to be made by adding 6 (0110) to skip over the six invalid codes

The correction involves two steps:

- **a carry of decimal value 1 is brought forward and added to the next higher digit**
- **the decimal value 6 is added to the sum to obtain the correct BCD digit**

Example:

$$24_{10} + 47_{10} = 71_{10}$$